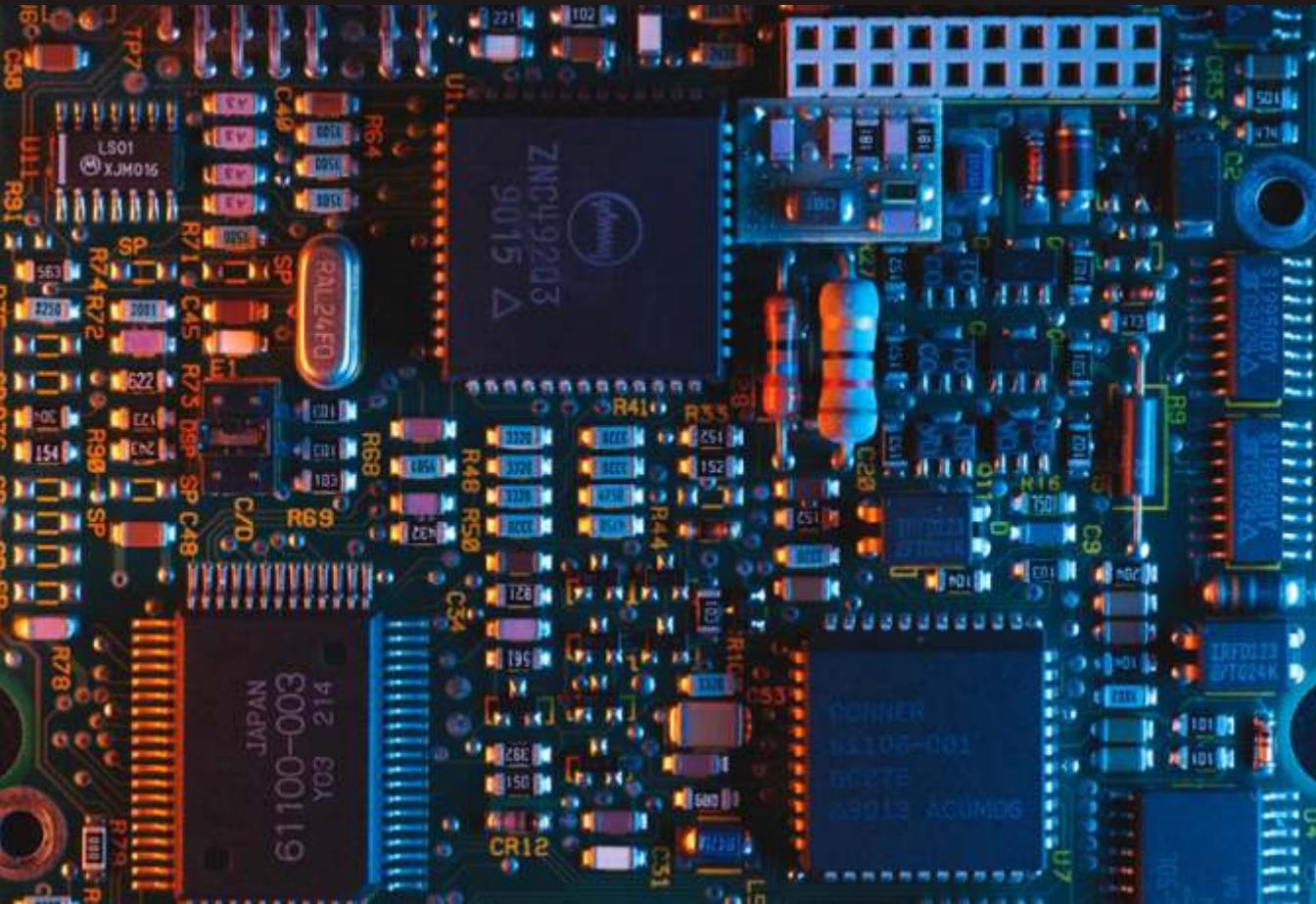


# Basic Electronics FOR SEAFARERS

Includes Relevant Topics for IMO Model Courses  
7.02, 7.04 and 7.08

Elstan A. Fernandez | Divyam Verma | Swarup Hati | Yadukrishnan KM





# **Basic Electronics for Seafarers**

*A Free Compilation*

*As per IMO Model Courses 7.02, 7.04 and 7.08*



# **Basic Electronics for Seafarers**

*A Free Compilation*

*As per IMO Model Courses 7.02, 7.04, 7.08*

*Elstan A. Fernandez*

*Divyam Verma*

*Swarup Hati*

*Yadukrishnan KM*

**Basic Electronics for Seafarers**

*By Elstan A. Fernandez, Divyam Verma, Swarup Hati, Yadukrishnan KM*

First Edition: August 2021



*To Our Fellow Seafarers  
and Would Be Seafarers Too*

## Preface

---

No matter where we go or what we do in this world today, Electronics plays a pivotal role. It is befitting to note that at the very beginning of the vast syllabus for the IMO Model Courses 7.02 and 7.04 for Engineers at the Management and Operational Levels and also 7.08 for ETOs, great stress has been laid on the knowledge and understanding of Basic Electronics.

This little book has been compiled from various sources and hence is not for commercial benefits but purely to help those who are interested to learn the subject. It thus aims at helping engineers recap their fundamentals and also apply the same in their work lives at sea and on land.

# Acknowledgements

---

This book has been compiled from various resources, without which, it would not have been possible. The following are the sources of our informations to whom we are grateful and sure that our readers would be grateful too!

## Sources for Chapter 1:

- <https://brilliant.org/>
- <https://en.wikipedia.org/>
- <https://manoa.hawaii.edu/>
- <https://www.britannica.com/>
- <https://www.codrey.com/>

## Sources for Chapter 2:

- <https://www.electronics-tutorials.ws>
- <https://byjus.com/physics/bridge-rectifier>
- Basic Electronics and Linear Circuits by N N Bhargava
- <https://www.engineeringprojects.com>
- Wikipedia

## Sources for Chapter 3:

- [circuitdigest.com](http://circuitdigest.com)
- [Wikipedia.com](https://en.wikipedia.org)
- [electronicshub.com](http://electronicshub.com)
- [electronicsslabs.com](http://electronicsslabs.com)
- [elprocus.com](http://elprocus.com)
- [electricalfundablog.com](http://electricalfundablog.com)

## Sources for Chapter 4:

- <https://www.circuitstoday.com/>
- <https://en.wikipedia.org/>
- <https://www.electronics-notes.com/>
- <https://www.electrical4u.com/>
- <https://instrumentationtools.com/>
- <https://www.electronics-tutorials.ws/>

## Sources for Chapter 4 (Continued)

- <https://industrialcircuits.wordpress.com/>
- <https://www.circuitstoday.com/>
- <https://www.electronicshub.org/>
- <https://news.energysage.com/>
- <https://www.differencebetween.com/>

## Sources for Chapter 5:

- [www.daenotes.com/](http://www.daenotes.com/)
- [www.elprocus.com/](http://www.elprocus.com/)
- [www.wikipedia.org/](http://www.wikipedia.org/)
- [http://wakerly.org/DDPP/DDPP4student/Supplementary\\_sections/ECL.pdf](http://wakerly.org/DDPP/DDPP4student/Supplementary_sections/ECL.pdf)

## Sources for Chapter 6:

- [www.elprocus.com/](http://www.elprocus.com/)
- [www.electronics-tutorials.ws](http://www.electronics-tutorials.ws)
- <https://www.electronics-notes.com/>
- [www.techwalla.com](http://www.techwalla.com)
- [www.geeksforgeeks.org](http://www.geeksforgeeks.org)
- <https://www.tutorialspoint.com>
- <http://www.pvpsiddhartha.ac.in/>
- Marine Control Practice by DA Taylor
- [www.marineeto.we.bs](http://www.marineeto.we.bs)
- [www.fierceelectronics.com](http://www.fierceelectronics.com)
- <https://www.electronics-tutorials.ws>
- <https://www.omega.com/>

# **Contents**

---

<b>Chapter No.</b>	<b>Title</b>	<b>Page No.</b>
1	Electron Theory	1
2	Semiconductors	21
3	Silicon Controlled Rectifiers	43
4	Power Electronics	61
5	ICs and LSI	127
6	Digital Techniques	143

---

<b>Chapter 1 – Electrical Theory</b>		
<b>Article No.</b>	<b>Article</b>	<b>Page No.</b>
1.1	Introduction	2
1.2	Atom	2
1.3	Molecules	3
1.4	Bonding	5
1.5	Element	6
1.6	Isotopes	7
1.7	Compound	7
1.8	Parts of Atoms	10
1.9	Orbits and Energy Levels	12
1.10	Orbitals	12
1.11	Applying Energy to an Atom	14
1.12	Flow of Current in a Conductor	15
1.13	Conventional Current and Electron Current	16
1.14	Electron Configurations	18

# Contents

<b>Chapter 2 – Semiconductors</b>		
<b>Article No.</b>	<b>Article</b>	<b>Page No.</b>
2.1	Introduction	22
2.2	Speciality of Semiconductor Materials	22
2.3	Atomic Structure and Free Electron	23
2.4	Energy Bands of Metals, Insulators and Semiconductors	23
2.5	Types of Semiconductors	25
2.6	Photoelectric Effect	28
2.7	Thermoelectric Effect	29
2.8	Hall Effect	29
2.9	The P-N Junction Diode	30
2.10	The Transistor	37

<b>Chapter 3 – Silicon Controlled Rectifiers</b>		
<b>Article No.</b>	<b>Article</b>	<b>Page No.</b>
3.1	Introduction	44
3.2	The Working Principle of a Thyristor	46
3.3	Function of the Gate Terminal	47
3.4	Switching Characteristics	48
3.5	Types of Transistors -Their Actions and Characteristics	50
3.6	Differences Between a DIAC and a TRIAC	52
3.7	Basic Applications of Thyristors:	55

<b>Chapter 4 – Power Electronics</b>		
<b>Article No.</b>	<b>Article</b>	<b>Page No.</b>
4.1	The Unijunction Transistor (UJT)	62
4.2	The Field Effect Transistor (FET)	64
4.3	The Insulated Gate Bipolar Transistor (IGBT)	68
4.4	The Gate Turn-off Thyristor (GTO)	73
4.5	The Integrated Gate-Commutated Thyristor (IGCT)	76
4.6	Power Electronic Converters	78
4.7	AC to DC Converters or Rectifiers	79
4.8	DC to DC Converters	89
4.9	AC to AC Converters	92

# Contents

<b>Chapter 4 – Power Electronics</b>		
<b>Article No.</b>	<b>Article</b>	<b>Page No.</b>
4.10	DC to AC Converters or Inverters	102
4.11	Multi String Inverters (MSI)	103
4.12	Linear Regulated Power Supply (Analog Power Supply)	105
4.13	Switched Mode Power-supply (SMPS) - Impulse Power Supply	105
4.14	The Snubber Circuit	107
4.15	The Operational Amplifier (Op-amp)	109
4.16	The Instrumentation Amplifier	119
4.17	The Multivibrator	121
4.18	Series Voltage Regulator Using an Op-Amp	123
4.19	The 4-20 mA Current Loop Transmitter Using an Op-Amp	124

<b>Chapter 5 – ICs and LSI</b>		
<b>Article No.</b>	<b>Article</b>	<b>Page No.</b>
5.1	Introduction	128
5.2	Fabrication	129
5.3	Large Scale Integration (LSI)	130
5.4	Logic Gate Families	130
5.5	TTL (Transistor-Transistor Logic)	130
5.6	Two-input ECL OR / NOR gate	135
5.7	TTL Comparison with ECL	136
5.8	Semiconductor Memories	136
5.9	Central Processing Unit (CPU)	138

<b>Chapter 6 – Digital Techniques</b>		
<b>Article No.</b>	<b>Article</b>	<b>Page No.</b>
6.1	Introduction	144
6.2	What are Basic Logic Gates?	144
6.3	What are the 7 Basic Logic Gates?	144
6.4	Why we use Basic Logic Gates?	145
6.5	Types of Logic Gates	146
6.6	De Morgan's Theorem	150
6.7	The Conversion of the NAND Gate	151

# **Contents**


---

<b>Chapter 6 – Digital Techniques</b>		
<b>Article No.</b>	<b>Article</b>	<b>Page No.</b>
6.8	Ex-OR Gate Conversion	152
6.9	Ex-NOR Gate Conversion	152
6.11	Basic Logic Gates using Universal Gates	153
6.12	Laws of Boolean Algebra	156
6.13	Transistor-Transistor Logic (TTL)	161
6.14	CMOS (Complementary Metal Oxide Semiconductor)	162
6.15	Binary Adder- Subtractor	164
6.16	Flip-Flops	166
6.17	Register	167
6.18	Counter	168
6.19	Encoder and Decoder	169
6.20	Basic 4x1 Multiplexer	171
6.21	Semiconductor Memory Technologies	172
6.22	Microprocessor	178
6.23	Application In Marine Control Systems	181
6.24	The 8085 Microprocessor	183
6.25	One-Time-Programmable Memory (OTP)	187
6.26	NOR Flash Memory	187
6.27	GPIO	188
6.28	3-bit Analogue-to-Digital Converter	190
6.29	3-bit Analogue to Digital Converter Circuit (Flash Type)	191
6.30	ADC0808 (A to D converter IC)	192

# 🚢 Chapter 1 🚦

## Electron Theory

---

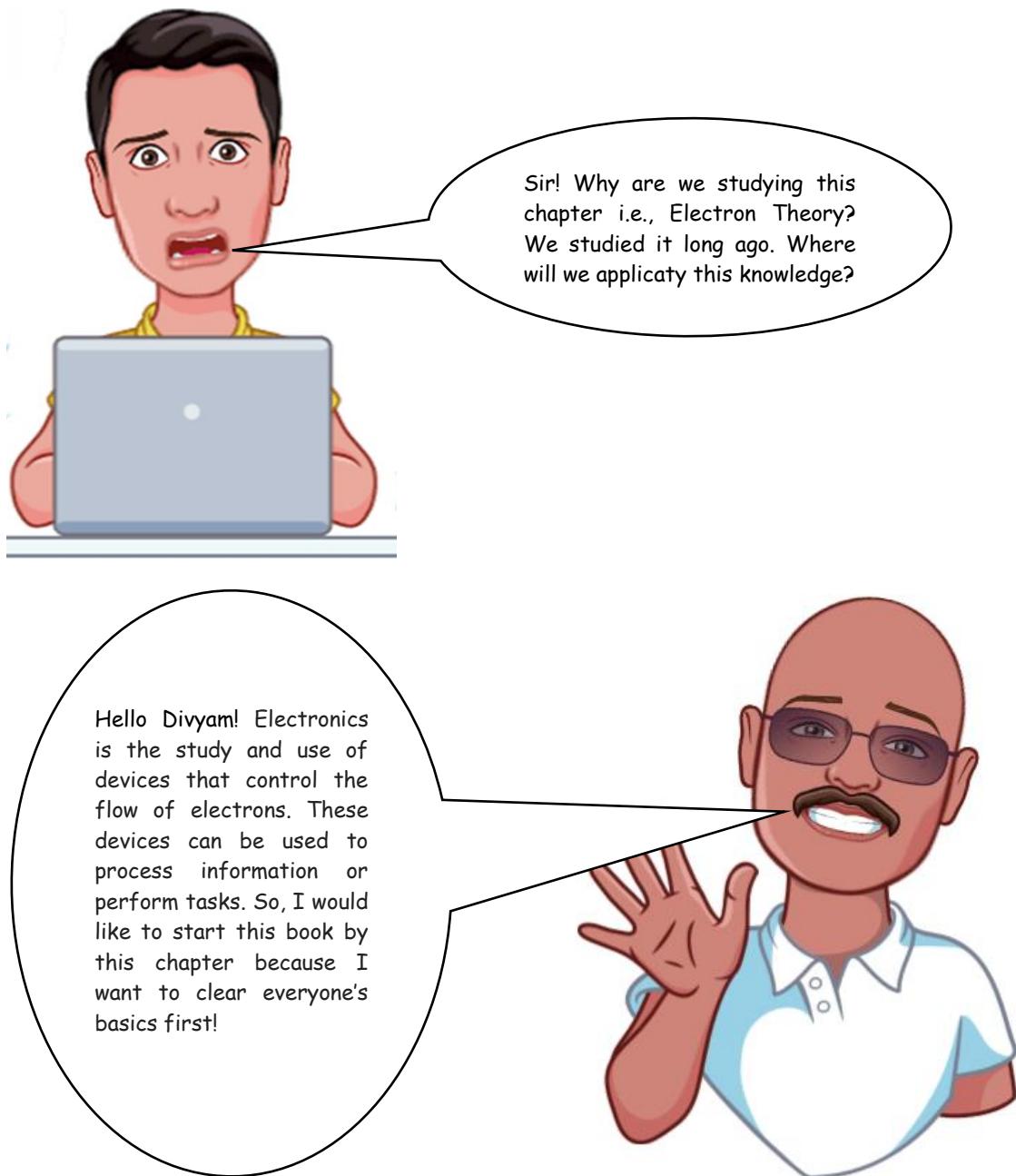

## Chapter 1

### 1.1 Introduction

Atoms are the building blocks of everything you see around: the screen you are looking at, your study table, your books, etc. Such is the amazing power of nature and also the fundamental nature of these particles. Despite the discovery of sub-particles like electrons, protons and neutrons, an atom continues to remain the fundamental particle because of the fact that it is the smallest unit humans can calculate and model and that which exhibits the chemical properties of an element.

### 1.2 Atom

The word “atom” has a Greek origin from the words “a” meaning not “temnein” meaning “to cut” combined to form “atomos” meaning “indivisible.” When Dalton divulged his atomic theory, it was believed that the atom was indivisible and hence the name. But later it was found that atoms could be subdivided into smaller parts; these are called the subatomic particles. As mentioned in the Introduction, an atom is the smallest constituent particle of an element which exhibits the chemical properties of an element and also can take part in a chemical reaction. Atoms are extremely small and their sizes are about an angstrom ( $1 \text{ Angstrom} = 1 \times 10^{-10} \text{ meters}$ ). The recent quantum mechanical model, suggests that it does not have a fixed shape or structure (For representative purposes and convenience, we however assume it to be spherical). This is due to the uncertainty principle, as proven by Werner Von Heisenberg, popularly known as Heisenberg’s uncertainty principle.

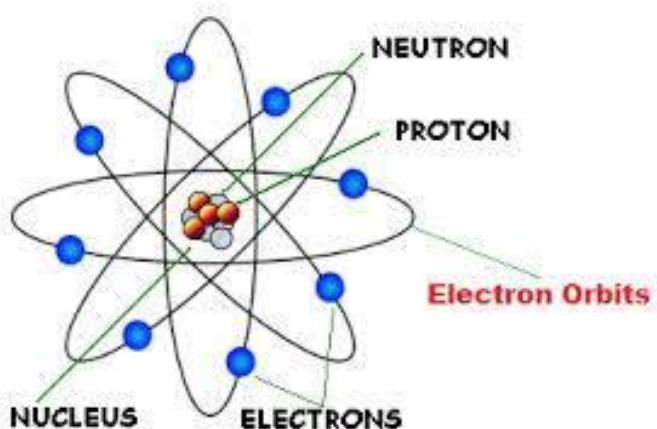


Figure 1.1 – The Atom

## **Electron Theory**

---

Every atom is composed of a nucleus and one or more electrons bound to the nucleus. The nucleus is made of one or more protons and a number of neutrons. Only the most common variety of hydrogen has no neutrons.

More than 99.94% of an atom's mass is in the nucleus. The protons have a positive electric charge, the electrons have a negative electric charge, and the neutrons have no electric charge. If the number of protons and electrons are equal, then the atom is electrically neutral. If an atom has more or fewer electrons than protons, then it has an overall negative or positive charge, respectively – such atoms are called ions.

The electrons of an atom are attracted to the protons in an atomic nucleus by the electromagnetic force. The protons and neutrons in the nucleus are attracted to each other by the nuclear force. This force is usually stronger than the electromagnetic force that repels the positively charged protons from one another. Under certain circumstances, the repelling electromagnetic force becomes stronger than the nuclear force. In this case, the nucleus splits and leaves behind different elements. This is a form of nuclear decay. The number of protons in the nucleus is the atomic number and it defines to which chemical element the atom belongs. For example, any atom that contains 29 protons, 35 neutrons and 29 electrons is copper (Cu). The number of neutrons defines the isotope of the element. Atoms can attach to one or more other atoms by chemical bonds to form chemical compounds such as molecules or crystals. The ability of atoms to associate and dissociate is responsible for most of the physical changes observed in nature. Chemistry is the discipline that studies these changes. There were many theories on the structure of an atom. Some of the most important ones are J.J. Thomson's Model, Rutherford's Model and Bohr's Model.


### **1.3 Molecules**

Atoms, in general, seem to be extroverts. They can easily combine with one another and form more complex particles called molecules as mentioned above. Thus, molecules are groups of atoms held together by chemical bonds and possess no net charge. Molecules can simply be defined as the way atoms exist in nature. Molecules, in general, are the smallest entities that can represent the chemical properties of a compound. It is strange to define a molecule using a compound, and then a compound using the idea of molecules, but they are so interconnected that it is difficult to find independent definitions. So, molecules are the basic units of everything that you see around. Molecules are formed when two or more atoms react and chemically combine under certain conditions. Molecules can be categorized as homo-nuclear and hetero-nuclear. It is pretty much evident from the names itself.

## Chapter 1

---

A homo-nuclear molecule is formed when the combining atoms are of the same element. For example, two hydrogen atoms combine together and form a stable homo-nuclear molecule, di-hydrogen ( $H_2$ ). It is the smallest molecule with a bond length of 0.74 Å where the Angstrom (Å), is the unit of length, equal to  $10^{-10}$  metre, or 0.1 nanometre. A hetero-nuclear molecule consists of atoms of different elements. For example, when two atoms of hydrogen and an atom of oxygen chemically combine, they form stable hetero-nuclear compound, water ( $H_2O$ ).

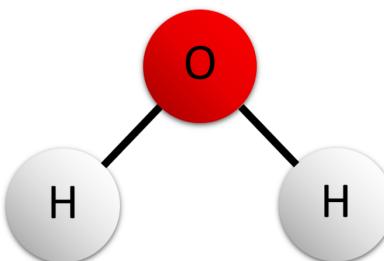

**Figure 1.2 – A Water Molecule**

Molecules can react with one another to form different molecules and thus different compounds. It is thus molecules that are in general involved in chemistry and chemical reactions, much more than atoms. Molecules as components of matter are common. They also make up most of the oceans and atmosphere. Most organic substances are molecules. The substances of life are molecules, e.g., proteins, the amino acids they are made of, the nucleic acids (DNA and RNA), sugars, carbohydrates, fats, and vitamins. The nutrient minerals ordinarily are not molecules, e.g., iron sulfate. However, the majority of familiar solid substances on Earth are not made of molecules. These include all of the minerals that make up the substance of the Earth, soil, dirt, sand, clay, pebbles, rocks, boulders, bedrock, the molten interior, and the core of the Earth. All of these contain many chemical bonds, but are not made of identifiable molecules.

Molecules can also be classified on the basis of the interaction between the atoms, i.e., the nature of the bond between the atoms. It can be covalent, i.e., there is an overlap of electron cloud of the two interacting atoms and the increased interaction between the overlapping electrons reduces the energy of the system keeping it intact.

It can also be ionic wherein one of the atoms loses an electron to become a positively charged ion while the other interacting ion gains an electron to become a negatively charged ion and these ions are held together by electrostatic forces.

### 1.4 Bonding

Molecules are held together by either covalent bonding or ionic bonding. Several types of non-metal elements exist only as molecules in the environment. For example, hydrogen only exists as hydrogen molecule. A molecule of a compound is made out of two or more elements. A homo-nuclear molecule is made out of two or more atoms of a single element.

#### 1.4.1 Covalent Bond

A covalent bond forming  $H_2$  where two hydrogen atoms share the two electrons. A covalent bond is a chemical bond that involves the sharing of electron pairs between atoms. These electron pairs are termed shared pairs or bonding pairs, and the stable balance of attractive and repulsive forces between atoms, when they share electrons, is termed *covalent bonding*.

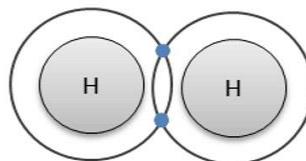


Figure 1.3 – A Covalent Bond

#### 1.4.2 Ionic Bond

Ionic bonding is a type of chemical bond that involves the electrostatic attraction between oppositely charged ions, and is the primary interaction occurring in ionic compounds. The ions are atoms that have lost one or more electrons (cations) and atoms that have gained one or more electrons (anions). This transfer of electrons is termed electrovalence in contrast to covalence. In the simplest case, the cation is a metal atom and the anion is a non-metal atom, but these ions can be of a more complicated nature, e.g., molecular ions like  $NH_4^+$  or  $SO_4^{2-}$ .

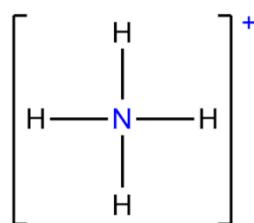


Figure 1.4 – An Ionic Bond

## Chapter 1

---

### 1.5 Element

In chemistry, an element is a pure substance consisting only of atoms that all have the same number of protons in their atomic nuclei. Unlike chemical compounds, chemical elements cannot be broken down into simpler substances by chemical means. The number of protons in the nucleus is the defining property of an element, and is referred to as its atomic number (represented by the symbol Z) – all atoms with the same atomic number are atoms of the same element. All of the baryonic matter of the universe is composed of chemical elements. When different elements undergo chemical reactions, atoms are rearranged into new compounds held together by chemical bonds. Only a minority of elements, such as silver and gold, are found uncombined as relatively pure native element minerals. Nearly all other naturally-occurring elements occur in the Earth as compounds or mixtures. Air is primarily a mixture of the elements namely nitrogen, oxygen, and argon, though it does contain compounds including carbon dioxide and water.

The history of the discovery and use of the elements began with primitive human societies that discovered native minerals like carbon, sulfur, copper and gold. Attempts to classify materials such as these resulted in the concepts of classical elements, alchemy, and various similar theories throughout human history.

Much of the modern understanding of elements developed from the work of Dmitri Mendeleev, a Russian chemist who published the first recognizable Periodic Table in 1869. This table organizes the elements by increasing atomic number into rows (“periods”) in which the columns (“groups”) share recurring (“periodic”) physical and chemical properties. The periodic table summarizes various properties of the elements, allowing chemists to derive relationships between them and to make predictions about compounds and potential new ones. By November 2016, the International Union of Pure and Applied Chemistry had recognized a total of 118 elements in the periodic table. The first 94 occur naturally on earth, and the remaining 24 are synthetic elements produced in nuclear reactions. Except for unstable radioactive elements (radionuclides) which decay quickly, nearly all of the elements are available industrially in varying amounts. The discovery and synthesis of further new elements is an on-going area of scientific study.

## Electron Theory

Group Period	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	
1	1 H																2 He		
2	3 Li	4 Be												5 B	6 C	7 N	8 O	9 F	10 Ne
3	11 Na	12 Mg												13 Al	14 Si	15 P	16 S	17 Cl	18 Ar
4	19 K	20 Ca	21 Sc	22 Ti	23 V	24 Cr	25 Mn	26 Fe	27 Co	28 Ni	29 Cu	30 Zn	31 Ga	32 Ge	33 As	34 Se	35 Br	36 Kr	
5	37 Rb	38 Sr	39 Y	40 Zr	41 Nb	42 Mo	43 Tc	44 Ru	45 Rh	46 Pd	47 Ag	48 Cd	49 In	50 Sn	51 Sb	52 Te	53 I	54 Xe	
6	55 Cs	56 Ba	*	71 Lu	72 Hf	73 Ta	74 W	75 Re	76 Os	77 Ir	78 Pt	79 Au	80 Hg	81 Tl	82 Pb	83 Bi	84 Po	85 At	86 Rn
7	87 Fr	88 Ra	*	103 Lr	104 Rf	105 Db	106 Sg	107 Bh	108 Hs	109 Mt	110 Ds	111 Rg	112 Cn	113 Nh	114 Fl	115 Mc	116 Lv	117 Ts	118 Og
	*	57 La	58 Ce	59 Pr	60 Nd	61 Pm	62 Sm	63 Eu	64 Gd	65 Tb	66 Dy	67 Ho	68 Er	69 Tm	70 Yb				
	*	89 Ac	90 Th	91 Pa	92 U	93 Np	94 Pu	95 Am	96 Cm	97 Bk	98 Cf	99 Es	100 Fm	101 Md	102 No				

Figure 1.5 – The Periodic Table

### 1.6 Isotopes

Isotopes are atoms of the same element (that is, with the same number of protons in their atomic nucleus), but having different numbers of neutrons. Thus, for example, there are three main isotopes of carbon. All carbon atoms have 6 protons in the nucleus, but they can have either 6, 7, or 8 neutrons.

Since the mass numbers of these are 12, 13 and 14 respectively, the three isotopes of carbon are known as carbon-12, carbon-13, and carbon-14, often abbreviated to  $^{12}\text{C}$ ,  $^{13}\text{C}$ , and  $^{14}\text{C}$ . Carbon in everyday life and in chemistry is a mixture of  $^{12}\text{C}$  (about 98.9%),  $^{13}\text{C}$  (about 1.1%) and about 1 atom per trillion of  $^{14}\text{C}$ . Most (66 of 94) naturally occurring elements have more than one stable isotope. Except for the isotopes of hydrogen (which differ greatly from each other in relative mass—enough to cause chemical effects), the isotopes of a given element are chemically nearly indistinguishable.


### 1.7 Compound

A chemical compound is a chemical substance composed of many identical molecules (or molecular entities) composed of atoms from more than one element held together by chemical bonds. A molecule consisting of atoms of only one element is therefore not a compound.

## Chapter 1

---

A compound can be converted to a different chemical substance by interaction with a second substance via a chemical reaction. In this process, bonds between atoms may be broken in either or both of the interacting substances, and new bonds formed. Any substance consisting of two or more different types of atoms (chemical elements) in a fixed stoichiometric proportion can be termed a chemical compound; the concept is most readily understood when considering pure chemical substances. It follows from their being composed of fixed proportions of two or more types of atoms that chemical compounds can be converted, via chemical reaction, into compounds or substances each having fewer atoms. The ratio of each element in the compound is expressed in a ratio in its chemical formula. A chemical formula is a way of expressing information about the proportions of atoms that constitute a particular chemical compound, using the standard abbreviations for the chemical elements, and subscripts to indicate the number of atoms involved. For example, water is composed of two hydrogen atoms bonded to one oxygen atom: the chemical formula is  $\text{H}_2\text{O}$  and so is  $\text{CH}_4$ . Many chemical compounds have a unique CAS number identifier assigned by the Chemical Abstracts Service. Globally, more than 350,000 chemical compounds (including mixtures of chemicals) have been registered for production and use.

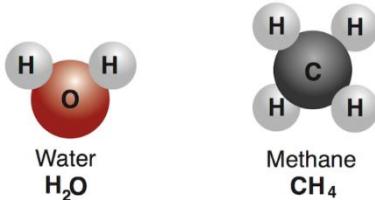

**Figure 1.6 – Compounds**

There are four types of compounds, depending on how the constituent atoms are held together:

- Molecules held together by covalent bonds
- Ionic compounds held together by ionic bonds
- Intermetallic compounds held together by metallic bonds
- Certain complexes held together by coordinate covalent bonds.

### 1.7.1 Molecule

A molecule is an electrically neutral group of two or more atoms held together by covalent bonds. A molecule may be homo-nuclear, that is, it consists of atoms of one chemical element, as with two atoms in the oxygen molecule ( $O_2$ ); or it may be hetero-nuclear, a chemical compound composed of more than one element, as with water (two hydrogen atoms and one oxygen atom;  $H_2O$ ).

### 1.7.2 Ionic Compounds

An ionic compound is a chemical compound composed of ions held together by electrostatic forces termed ionic bonding. The compound is neutral overall, but consists of positively charged ions called cations and negatively charged ions called anions. These can be simple ions such as the sodium ( $Na^+$ ) and chloride ( $Cl^-$ ) in sodium chloride. Individual ions within an ionic compound usually have multiple nearest neighbours, so are not considered to be part of molecules, but instead part of a continuous three-dimensional network, usually in a crystalline structure.

Ionic compounds containing basic ions hydroxide ( $OH^-$ ) or oxide ( $O^{2-}$ ) are classified as bases. Ionic compounds without these ions are also known as salts and can be formed by acid–base reactions. Ionic compounds can also be produced from their constituent ions by evaporation of their solvent, precipitation, freezing, a solid-state reaction, or the electron transfer reaction of reactive metals with reactive non-metals, such as halogen gases. Ionic compounds typically have high melting and boiling points, and are hard and brittle. As solids they are almost always electrically insulating, but when melted or dissolved they become highly conductive, because the ions are mobilized.

### 1.7.3 Intermetallic Compounds

An intermetallic compound is a type of metallic alloy that forms an ordered solid-state compound between two or more metallic elements. Intermetallics are generally hard and brittle, with good high-temperature mechanical properties. They can be classified as stoichiometric or nonstoichiometric intermetallic compounds.

### 1.7.4 Complexes

A coordination complex consists of a central atom or ion, which is usually metallic and is called the coordination centre, and a surrounding array of bound molecules or ions, that are in turn known as ligands or complexing agents.

## Chapter 1


Many metal-containing compounds, especially those of transition metals, are coordination complexes. A coordination complex whose centre is a metal atom is called a metal complex of d block element.

### 1.8 Parts of Atoms

The particles that make up an atom are called subatomic particles (sub- means “smaller size”). These particles are:

- The proton ( $p^+$ ), which is positively (+) charged;
- The electron ( $e^-$ ), which is negatively (-) charged; and
- The neutron ( $n^0$ ), which has no charge, it is neutral (0).

Protons and neutrons occupy the nucleus, or center, of the atom. Electrons exist in regions called shells or orbitals outside of the atom’s nucleus. Electrostatic forces also hold electrons and protons together in the atom. The attraction between negatively charged electrons and positively charged protons in an atom give the atom its structure. The protons and neutrons in the nucleus are attracted to each other by the nuclear force. This force is usually stronger than the electromagnetic force that repels the positively charged protons from one another. The number of electrons and protons in an atom determines its chemical properties. Chemical properties include the specific ways that atoms and molecules react and the energy that they release or use in these reactions.

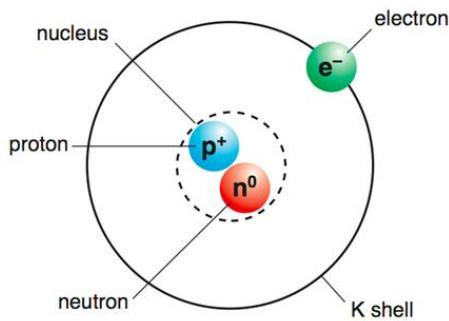

**Figure 1.7 – Parts of an Atom**

### 1.8.1 Size of Subatomic Particles

One hundred million (100,000,000) hydrogen atoms put side-by-side equals about a centimetre. The protons and neutrons are both about one-thousandth (1/1000) the diameter of a hydrogen atom. This means it would take about one hundred billion (100,000,000,000) protons or neutrons put side-by-side to equal a centimetre. Electrons are about one-thousandth (1/1000) the diameter of a proton or neutron. This means that it would take one hundred trillion (100,000,000,000,000) electrons put side-by-side to equal a centimetre!

### 1.8.2 Mass of Subatomic Particles

The electron is by far the least massive of these particles at  $9.11 \times 10^{-31}$  kg. Protons have a mass 1,836 times that of the electron, at  $1.6726 \times 10^{-27}$  kg. Neutrons have a free mass of 1,839 times the mass of the electron, or  $1.6749 \times 10^{-27}$  kg. Neutrons are the heaviest of the three constituent particles.

### 1.8.3 Neutral Atoms

The subatomic particles in an atom determine the properties of the atom. Some atoms exist naturally as neutral, or uncharged, atoms. A single uncharged atom has an equal number of protons (+) and electrons (-). An uncharged atom is electrically neutral because electrons and protons have opposite charges of equal sizes. When the number of protons and electrons in an atom are same, the charges cancel out, or counteract each other.

### 1.8.4 Atomic Number

Atomic number is nothing but the number of protons present in the nucleus of an atom. It is denoted by 'Z'. For neutral atoms, it is the number of protons or electrons in an atom.

### 1.8.5 Atomic Mass Number

An atomic mass number is the sum of numbers of protons and neutrons present in the nucleus of an atom. It is denoted by 'A'.

Example: An element has 11 protons and 12 neutrons in the nucleus of its atom. Find the atomic number (Z) and atomic mass number (A) of that element?

$$\text{Atomic number (Z)} = \text{Number of protons} = 11$$

$$\text{Atomic mass number (A)} = \text{Number of protons} + \text{Number of neutrons} = 11 + 12 = 23.$$

Therefore, the atomic number (Z) and the atomic mass number (A) of that element are 11 and 23.

## Chapter 1

---

### 1.9 Orbits and Energy Levels


Unlike planets orbiting the Sun, electrons cannot be at any arbitrary distance from the nucleus; they can exist only in certain specific locations called allowed orbits. This property, first explained by Danish physicist Niels Bohr in 1913, in the Bohr atom electrons can be found only in allowed orbits, and these allowed orbits are at different energies. The orbits are analogous to a set of stairs in which the gravitational potential energy is different for each step and in which a ball can be found on any step but never in between. An electron shell, or principal energy level, may be thought of as the orbit of one or more electrons around an atom's nucleus. The closest shell to the nucleus is called the “1 shell” (also called “K shell”), followed by the “2 shell” (or “L shell”), then the “3 shell” (or “M shell”), and so on farther and farther from the nucleus. The shells correspond with the principal quantum numbers ( $n = 1, 2, 3, 4 \dots$ ) or are labeled alphabetically with letters used in the X-ray notation (K, L, M, N...). Each shell can contain only a fixed number of electrons: The first shell can hold up to two electrons, the second shell can hold up to eight ( $2 + 6$ ) electrons, the third shell can hold up to 18 ( $2 + 6 + 10$ ) and so on. The general formula is that the  $n$ th shell can in principle hold up to  $2(n^2)$  electrons. Since electrons are electrically attracted to the nucleus, an atom's electrons will generally occupy outer shells only if the more inner shells have already been completely filled by other electrons. However, this is not a strict requirement: atoms may have two or even three incomplete outer shells. Inside each shell there may be subshells corresponding to different rates of rotation and orientation of orbitals and the spin directions of the electrons. In general, the farther away from the nucleus a shell is the more subshells it will have. The subshells are called orbitals.

### 1.10 Orbitals

It is defined as “the three-dimensional region in space around the nucleus where the probability of finding the electron is maximum.” An electron can move anywhere in an atom, even inside the nucleus, or theoretically even at the other side of the universe, but 90% probability is that it is found in a small specific region of space around the nucleus, and this region is nothing but the “orbital.” Each orbital in an atom is characterized by a unique set of values of the three quantum numbers  $n$ ,  $\ell$ , and  $m_l$ , which respectively correspond to the electron's energy (principal quantum number), angular momentum, and an angular momentum vector component (the magnetic quantum number). Each such orbital can be occupied by a maximum of two electrons, each with its own projection of spin  $m_s$ . The simple names s orbital, p orbital, d orbital, and f orbital refer to orbitals with angular momentum quantum number  $\ell = 0, 1, 2$ , and  $3$  respectively.

## Electron Theory

These names, together with the value of  $n$ , are used to describe the electron configurations of atoms. In atoms with a single electron (hydrogen-like atoms), the energy of an orbital (and, consequently, of any electrons in the orbital) is determined mainly by  $n$ . The  $n=1$  orbital has the lowest possible energy in the atom. Each successively higher value of  $n$  has a higher level of energy, but the difference decreases as  $n$  increases.

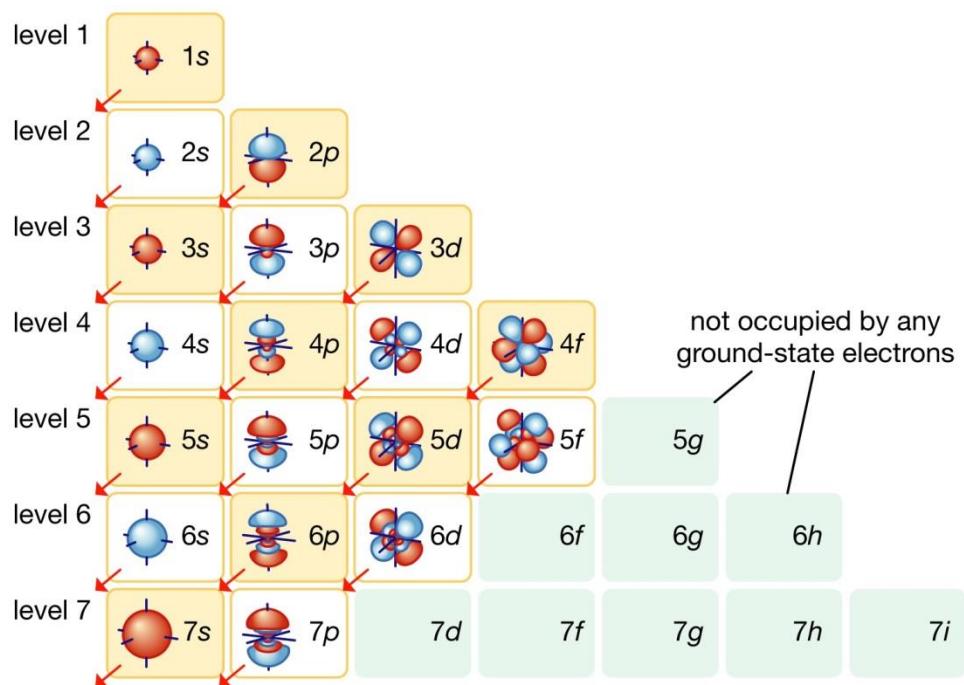

**Figure 1.8 – Energy Levels**

For high  $n$ , the level of energy becomes so high that the electron can easily escape from the atom. In single electron atoms, all levels with different  $\ell$  within a given  $n$  are degenerate in the Schrödinger approximation, and have the same energy. There for with the increase in distance from the nucleus the electron gets more energy.


In atoms with multiple electrons, the energy of an electron depends not only on the intrinsic properties of its orbital, but also on its interactions with the other electrons. These interactions depend on the detail of its spatial probability distribution, and so the energy levels of orbitals depend not only on  $n$  but also on  $\ell$ . Higher values of  $\ell$  are associated with higher values of energy; for instance, the 2p state is higher than the 2s state.

## Chapter 1

When  $\ell = 2$ , the increase in energy of the orbital becomes as large as to push the energy of orbital above the energy of the s-orbital in the next higher shell; when  $\ell = 3$  the energy is pushed into the shell two steps higher. The filling of the 3d orbitals does not occur until the 4s orbitals have been filled.

### 1.11 Applying Energy to an Atom

The laws of quantum mechanics describe the process by which electrons can move from one allowed orbit, or energy level, to another. As with many processes in the quantum world, this process is impossible to visualize. An electron disappears from the orbit in which it is located and reappears in its new location without ever appearing any place in between. This process is called a quantum leap or quantum jump, and it has no analog in the macroscopic world.

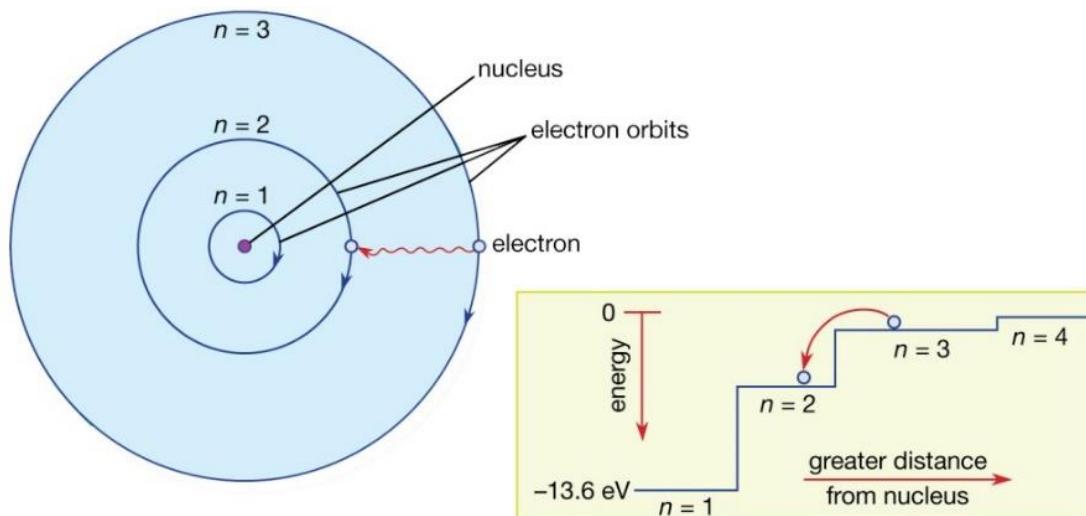

**Figure 1.9 – Application of Energy to an Atom**

As different orbits have different energies, whenever a quantum leap occurs, the energy possessed by the electron will be different after the jump. For example, if an electron jumps from a higher to a lower energy level, the lost energy will have to go somewhere and in fact will be emitted by the atom in a bundle of electromagnetic radiation. This bundle is known as a photon, and this emission of photons with a change of energy levels is the process by which atoms emit light. In the same way, if energy is added to an atom, an electron can use that energy to make a quantum leap from a lower to a higher orbit.

This energy can be supplied in many ways. One common way is for the atom to absorb a photon of just the right frequency. For example, when white light is shone on an atom, it selectively absorbs those frequencies corresponding to the energy differences between allowed orbits.

Each element has a unique set of energy levels, and so the frequencies at which it absorbs and emits light act as a kind of fingerprint, identifying the particular element. This property of atoms has given rise to spectroscopy, a science devoted to identifying atoms and molecules by the kind of radiation they emit or absorb.

### 1.12 Flow of Current in a Conductor

The way that atoms bond together affects the electrical properties of the materials they form. For example, in materials held together by the metallic bond, electrons float loosely between the metal ions. These electrons will be free to move if an electrical force is applied. For example, if a copper wire is attached across the poles of a battery, the electrons will flow inside the wire. Thus, electric current flows, and the copper is said to be a conductor.

The flow of electrons inside a conductor is not quite so simple, though. A free electron will be accelerated for a while but will then collide with an ion. In the collision process, some of the energy acquired by the electron will be transferred to the ion. As a result, the ion will move faster, and an observer will notice the wire's temperature rise. This conversion of electrical energy from the motion of the electrons to heat energy is called electrical resistance. In a material of high resistance, the wire heats up quickly as electric current flows. In a material of low resistance, such as copper wire, most of the energy remains with the moving electrons, so the material is good at moving electrical energy from one point to another. Its excellent conducting property, together with its relatively low cost, is why copper is commonly used in electrical wiring.

The exact opposite situation obtains in materials, such as plastics and ceramics, in which the electrons are all locked into ionic or covalent bonds. When these kinds of materials are placed between the poles of a battery, no current flows - there are simply no electrons free to move. Such materials are called insulators.

While the normal motion of "free" electrons in a conductor is random, with no particular direction or speed, electrons can be influenced to move in a coordinated fashion through a conductive material. This uniform motion of electrons is what we call electricity or electric current.

## Chapter 1

---

To be more precise, it could be called dynamic electricity in contrast to static electricity, which is an unmoving accumulation of electric charge. Just like water flowing through the emptiness of a pipe, electrons are able to move within the empty space within and between the atoms of a conductor. The conductor may appear to be solid to our eyes, but any material composed of atoms is mostly empty space! The liquid-flow analogy is so fitting that the motion of electrons through a conductor is often referred to as a “flow.”

A noteworthy observation may be made here. As each electron moves uniformly through a conductor, it pushes on the one ahead of it, such that all the electrons move together as a group. The starting and stopping of electron flow through the length of a conductive path is virtually instantaneous from one end of a conductor to the other, even though the motion of each electron may be very slow. An approximate analogy is that of a tube filled end-to-end with marbles: The tube is full of marbles, just as a conductor is full of free electrons ready to be moved by an outside influence. If a single marble is suddenly inserted into this full tube on the left-hand side, another marble will immediately try to exit the tube on the right. Even though each marble only travelled a short distance, the transfer of motion through the tube is virtually instantaneous from the left end to the right end, no matter how long the tube is. With electricity, the overall effect from one end of a conductor to the other happens at the speed of light: a swift 186,000 miles per second!!! Each individual electron, though, travels through the conductor at a much slower pace.

### 1.13 Conventional Current and Electron Current

Electron current and conventional current are two types of notations we use to mention current flow in a circuit. These two notations are opposite to each other. We need a notation to do some calculations like in Kirchhoff's law. And we consider conventional current as the standard notation of current flow. But actually, this notation is scientifically not correct. But still, all the laws follow this notation. So, before we get into these notations, we need to understand charges in electricity.

#### 1.13.1 Charges – Positive and Negative Charges

First of all Franklin assumed an electric charge which moved in the opposite direction that it should actually be doing, so he called this electric charge “negative” which means deficiency of charges and so we can consider “positive” means surplus of electric charges. After some time, true direction of flow of electrons was discovered and it was noticed that this labels of positive and negative is incorrect scientifically.

By that time, the notation of positive and negative was extremely widespread and so no efforts were made by engineers to change the old notations. As a result of this, we are still using the same notations that were first assumed by Sir Benjamin Franklin. And this notation we use now is conventional current notation or normal current flow. Let's discuss it in detail.

### 1.13.2 Conventional Current Flow Notation

Before starting with this, we associate the word “positive” with surplus of charges and “negative” with deficiency of charges. This has been a label since Franklin first assumed it. Imagine a battery connected across the conductor. In the electrically stressed conductor, electric charges move from positive terminal to negative terminal of the battery. Positive terminal has surplus of electric charges and so these charges are attracted towards negative terminal of the battery where there is a deficiency of charges. This notation is used widely by the engineers and so it is said as conventional flow notation.

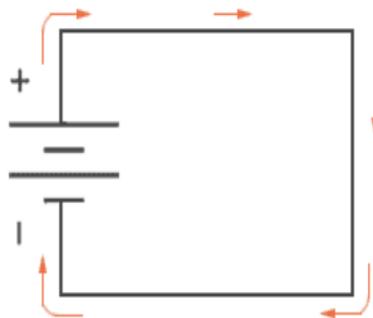


Figure 1.10 – Conventional Flow

### 1.13.3 Electron Flow Notation

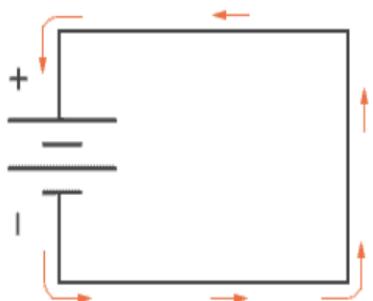


Figure 1.11 – Electron Flow

## Chapter 1

---

As the name itself says, this notation is based on the movement of electrons. This notation shows what actually happens inside an electrically stressed conductor. The negative terminal of battery has high density of electrons. This electron travels from the negative terminal of the battery where the density of electrons is high to the positive terminal where the density of electrons is less and that's why they get attracted towards positive terminal of the battery. Hence this type of current is known as electron current.

### 1.14 Electron Configurations

Elements are placed in order on the periodic table based on their atomic number, how many protons they have. In a neutral atom, the number of electrons will equal the number of protons, so we can easily determine electron number from atomic number. In addition, the position of an element in the periodic table - its column, or group, and row, or period—provides useful information about how those electrons are arranged.

If we consider just the first three rows of the table, which include the major elements important to life, each row corresponds to the filling of a different electron shell: helium and hydrogen place their electrons in the 1n shell, while second-row elements like Li start filling the 2n shell, and third-row elements like Na continue with the 3n shell. Similarly, an element's column number gives information about its number of valence electrons. In general, the number of valence electrons is the same within a column and increases from left to right within a row. Group 1 elements have just one valence electron and group 18 elements have eight, except for helium, which has only two electrons total. The number of electrons in the outermost shell of a particular atom determines its reactivity, or tendency to form chemical bonds with other atoms. This outermost shell is known as the valence shell, and the electrons found in it are called valence electrons. In general, atoms are most stable, least reactive, when their outermost electron shell is full. Most of the elements important in biology need eight electrons in their outermost shell in order to be stable, and this rule of thumb is known as the octet rule. Some atoms can be stable with an octet even though their valence shell is the 3n shell, which can hold up to 18 electrons. Thus, group number is a good predictor of how reactive each element will be:

Helium (He), neon (Ne), and argon (Ar), as group 18 elements, have outer electron shells that are full or satisfy the octet rule. This makes them highly stable as single atoms. Because of their non-reactivity, they are called the inert gases or noble gases.

## Electron Theory

Hydrogen (H), lithium (Li), and sodium (Na), as group 1 elements, have just one electron in their outermost shells. They are unstable as single atoms, but can become stable by losing or sharing their one valence electron. If these elements fully lose an electron - as Li and Na typically do - they become positively charged ions:  $\text{Li}^+$  and  $\text{Na}^+$ .


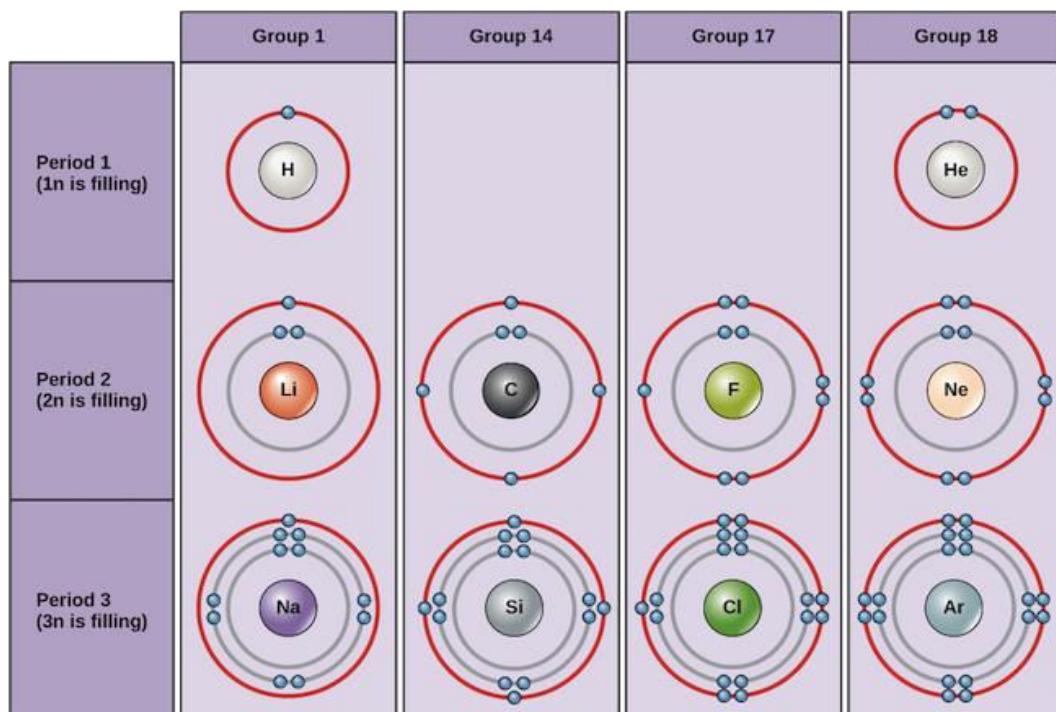


Figure 1.12 – Groups and Periods

Fluorine (F) and chlorine (Cl), as group 17 elements, have seven electrons in their outermost shells. They tend to achieve a stable octet by taking an electron from other atoms, becoming negatively charged ions:  $\text{F}^-$  and  $\text{Cl}^-$ . Carbon (C), as a group 14 element, has four electrons in its outer shell. Carbon typically shares electrons to achieve a complete valence shell, forming bonds with multiple other atoms. Thus, the columns of the periodic table reflect the number of electrons found in each element's valence shell, which in turn determines how the element will react.

## ***Chapter 1***

---

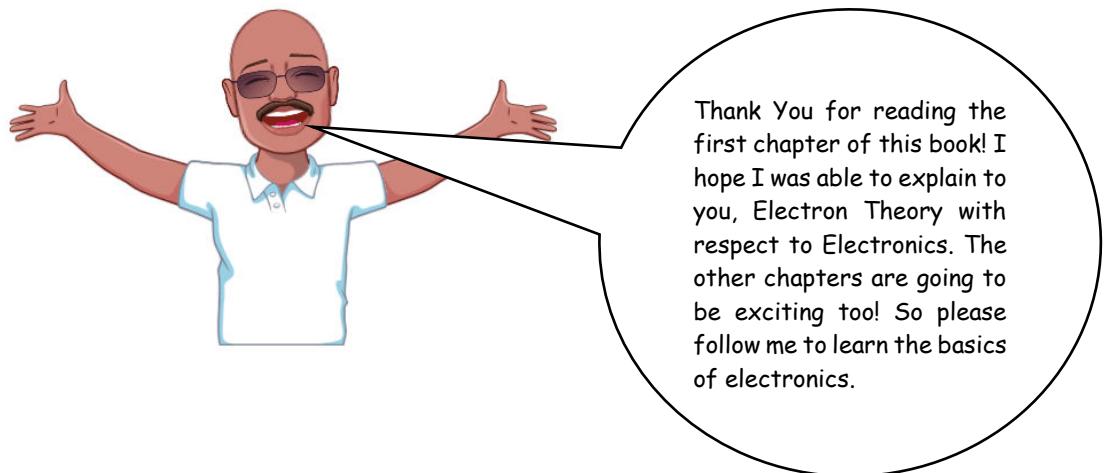

Thank You for reading the first chapter of this book! I hope I was able to explain to you, Electron Theory with respect to Electronics. The other chapters are going to be exciting too! So please follow me to learn the basics of electronics.

### **Sources:**

- <https://brilliant.org/>
- <https://en.wikipedia.org/>
- <https://manoa.hawaii.edu/>
- <https://www.britannica.com/>
- <https://www.codrey.com/>

## 🚢 Chapter 2 🚢

# Semiconductors

---



Sir! What is the importance of learning Semi-conductors in our curriculum?

Semiconductors have a wide application in electronics. It deals with the majority of upcoming technologies. Also, with the introduction of automation in the shipping industry, a good understanding of semiconductors becomes really important for freshers like you!



## **Chapter 2**

---

### **2.1 Introduction**

All of us are familiar with some of the simple applications of electronics like the radio, television and the calculator. If you look inside any electronic equipment, you will find resistors, capacitors, inductors, transformers, semiconductor diodes, transistors and ICs.

We already know something about resistors, capacitors, inductors, and transformers, but small semiconductor devices like diodes and other related components are new to most of us. In modern electronic systems, the whole electronic circuit, containing many diodes, transistors, resistors, etc., are even fabricated on a single chip. This is known as an integrated circuit (IC).

### **2.2 Speciality of Semiconductor Materials**

On the basis of electrical conductivity all the material are classified into three categories, such as conductor, insulator and semiconductor. We are familiar with a conductor and an insulator. To reiterate, conductor have good electrical conductivity, the flow of electron with in conducting material is very smooth if potential difference is applied.


Examples of good conductors are silver, copper etc. The flow of electron is restricted by the property of resistivity in insulating material. Its electrical conductivity is very less in nature. Examples of good insulators are rubber, PVC, glass etc.

Apart from these, there is another group of materials whose electrical conductivity is neither too good as conductor nor too bad as insulator. Its conductivity is in between a conductor and an insulator, and hence termed as a semiconductor. At room temperature these materials have conductivities that are considerably lower than that of conductors, but much higher than insulators. If one increases the temperature, a semiconductor behaves opposite to that of a metal, i.e., the resistivity decreases and obviously conductivity rises. There are certain properties which make semiconductor more popular, namely:

1. The conductivity of semiconductor can be controlled.
2. They have a negative temperature coefficient.
3. They have a unidirectional current flow.
4. Less power is required to operate a semiconductor device.

**2.3 Atomic Structure and Free Electron**

Figure 2.1(a). shows the structure of an aluminum atom. The nucleus of the aluminum atom contains 13 protons (13 P) and 14 neutrons (14N). Note that there are two electrons in the first shell, eight electrons in the second, and only three electrons in the outermost shell. Similarly, the nucleus of copper consists of 29 protons (red) and 34 neutrons (blue). 29 electrons (green) bind to the nucleus, successively occupying available electron shells (rings). Copper is a transition metal in group 11, period 4, and the d-block of the periodic table. It has a melting point of 1083°C.

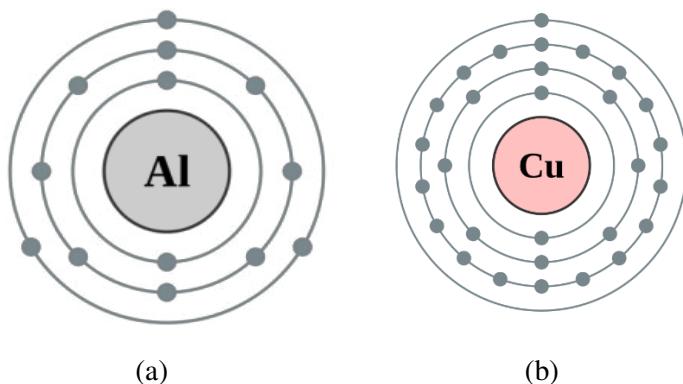**Figure 2.1 – Aluminum Atom**


The electrons in the inner shells are tightly bound by the attractive force of nucleus. But the electrons in the outermost shell experience very little attractive force in *case of metal*. So, these may travel freely from atom to atom. These electrons are termed as *free electron* which take part in electrical conduction.

**2.4 Energy Bands of Metals, Insulators and Semiconductors**

When atoms bond together to form a solid, the energy of electrons in a particular orbit for all atoms differ very slightly in energy. For this reason, closely spaced energy levels form a cluster or band.

## Chapter 2

---

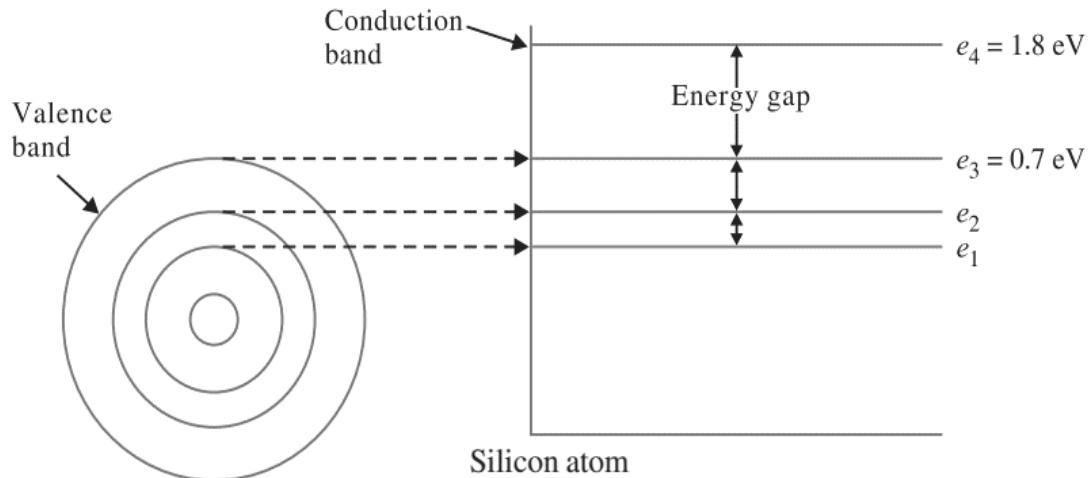

**Figure 2.2 – Silicon Atom**

In the Silicon (Si) atom there are four valence electrons present in the outermost orbit, the combining more Si atoms in this – the third band make it the *valence band*. Valence bands are complete with electrons. Thus, an electron in a completely filled band cannot contribute to electric current. The conduction band is always above the valence band. The conduction band represents the next larger group of permissible energy levels. There is an energy gap, e.g., between the valence band and the conduction band. An electron can jump from the valence band to the conduction band by adding some energy to silicon. The gap between the valence band and the conduction band is called the forbidden energy gap.

The conduction-band energies are in the metal, so the electrons can easily move from a valence band to a conduction band.


An insulating material has an energy-band with a very wide forbidden-energy gap (5 eV or more). Because of this, it is practically impossible for an electron in the valence band to jump the gap, to reach the conduction band. Only at very high temperature can an electron jump the gap.

In case of a semiconductor, the forbidden energy gap is not too long. It is of the order of 1 eV (for germanium,  $E_a = 0.72 \text{ eV}$  and for silicon  $E_a = 1.12 \text{ eV}$ ). The energy provided by heat at room temperature is sufficient to lift electrons from the valence band to the conduction band. Some electrons do jump the gap and go into the conduction band. Therefore, at room temperature, semiconductors are capable of conducting some electric current.

## Semiconductors

An electron in the conduction band experiences almost negligible nuclear attraction. it moves randomly throughout the solid. This is why the electrons in the conduction band are called *free electrons*.

In metal, there is no forbidden energy gap between the valence and conduction bands. The two bands actually overlap as shown in [Figure - 2.3](#)

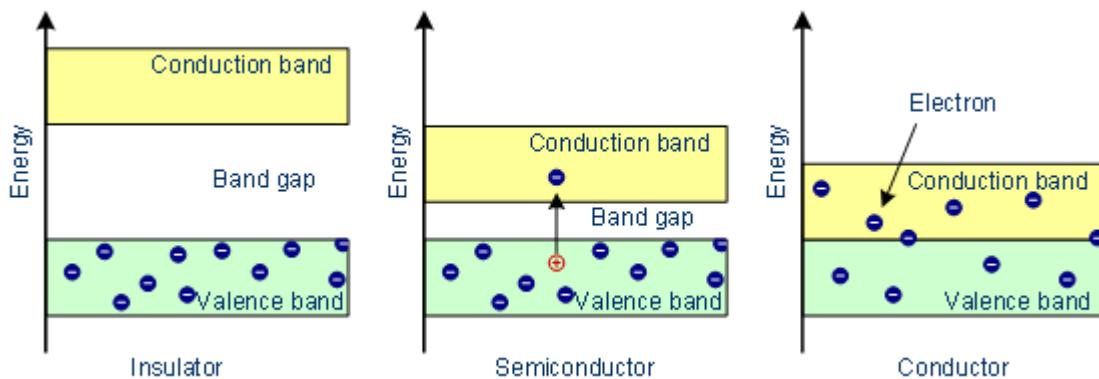

**Figure 2.3 – Differences between an Insulator, Semiconductor and Conductor**

### 2.5 Types of Semiconductors

Semiconductors are mainly two types:


- Intrinsic semiconductor
- Extrinsic semiconductor
  - P-type extrinsic semiconductor
  - N-type extrinsic semiconductor

#### 2.5.1 Intrinsic Semiconductors

They are pure semiconductors without any significant dopant species present. The number of charge carriers is therefore determined by the properties of the material itself instead of the number of impurities. Conductivity of intrinsic semiconductors is poor. Free electrons are only due to natural causes such as thermal effect, light energy, etc.

## Chapter 2

---

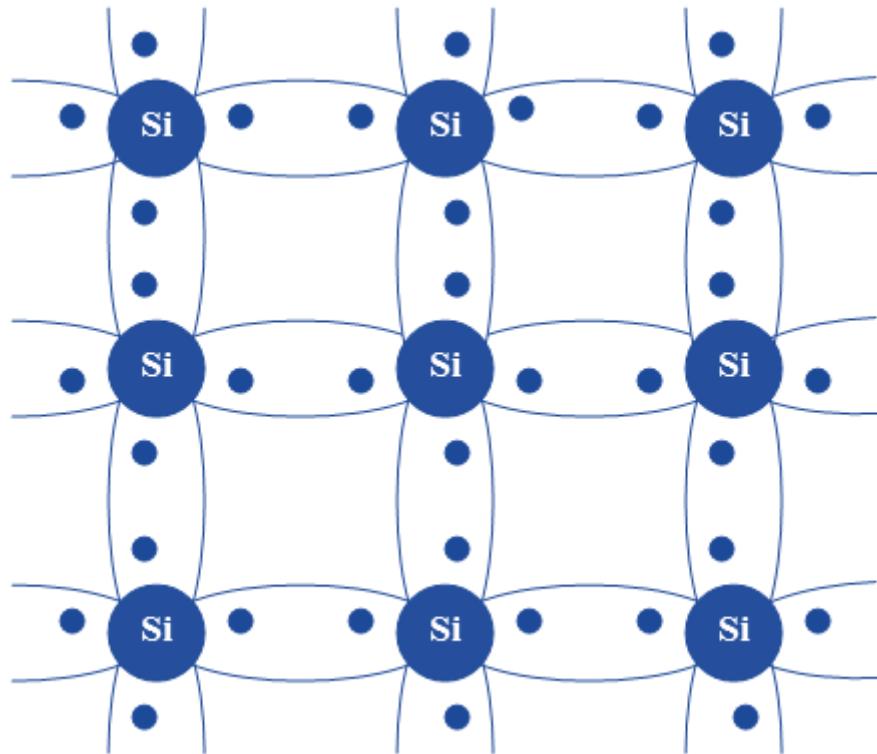


**Figure 2.4 – (Intrinsic Si Semiconductor)**

An impure semiconductor is called an *extrinsic semiconductor*. A small quantity of impure atoms is added in a pure or intrinsic semiconductor to improve its conductivity. The process of adding impurity atoms to pure semiconductor is called Doping. There are two types of impurity are there. One is pentavalent (P, As, Antimony) another one trivalent (Boron, Al) atom.

p-type – adding trivalent impurities.

n-type – adding pentavalent impurities.

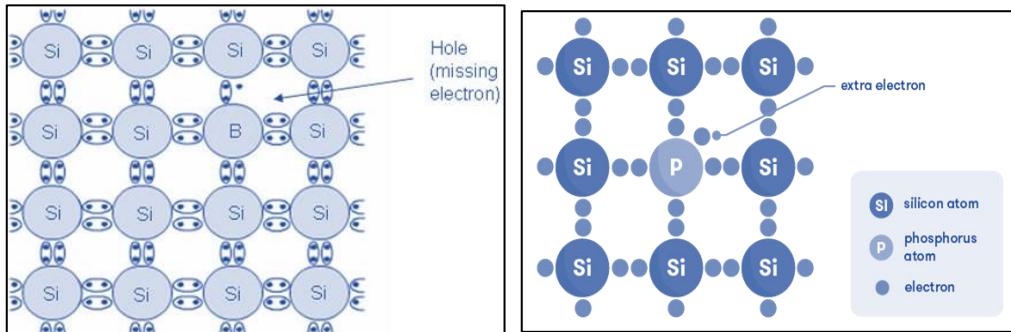

**Figure 2.5 – (p-type doping)**

**Figure 2.6 – (n-type doping)**

*Note: The Deficiency of an electron is called a Hole.*

### 2.5.1.1 N-doping

The 5-valent dopant has an outer electron more than the silicon atoms. Four outer electrons combine with ever one silicon atom, while the fifth electron is free to move and serves as charge carrier. This free electron requires much less energy to be lifted from the valence band into the conduction band, than the electrons which cause the intrinsic conductivity of silicon.


### 2.5.1.2 P-doping

In contrast to the free electron due to doping with phosphorus, the 3-valent dopant effect is exactly the opposite. The 3-valent dopants can catch an additional outer electron, thus leaving a hole in the valence band of silicon atoms. Therefore, the electrons in the valence band become mobile. The holes move in the opposite direction to the movement of the electrons.

## Chapter 2

### 2.6 Photoelectric Effect

When a light wave of sufficient energy is incident on a metal, then electrons are ejected or emitted from its surface. This phenomenon is known as **photoelectric effect**.

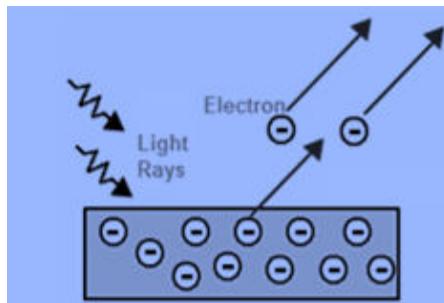

**Figure 2.7 – (p-type doping)**

Figure 2.7 shows a metal plate taken, also source of light present here which is aliened to incident on the metal surface. Electrons gets ejected from the surface of the metal. These electrons are known as photo electrons. Every metal has a different quantum energy of electrons.

1. Photoelectrons are ejected by a metal surface when the frequency of incident radiation becomes equal or greater than the work function of the metal.

$$hf \geq \Theta$$

$\Theta$  = work function of metal


$h$  = Plank constant

$f$  = frequency of light

2. The number of photoelectrons emitted per second is directly proportional to the intensity of incident radiation.
3. The max energy of photoelectrons does not depend on the intensity of incident light but relies on the frequency of light.

**2.7 Thermoelectric Effect**

The phenomenon of production of current in a thermocouple, due to variation of heat is known as thermoelectric effect.

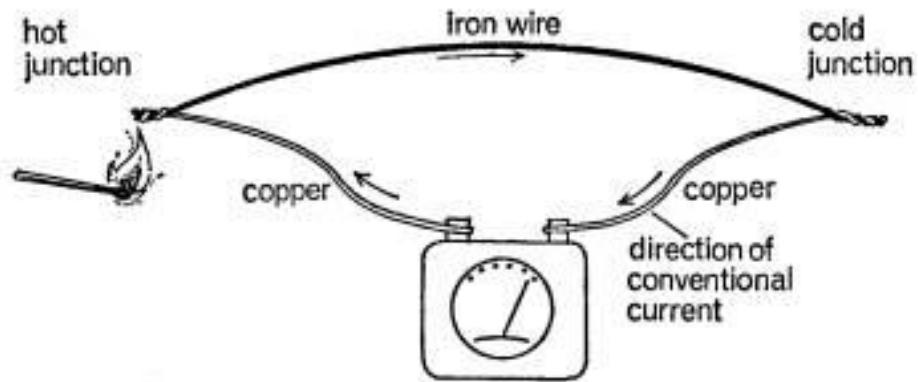

**Figure 2.8 – Thermoelectric Effect**

The Figure above shows two dissimilar metal wires that are coupled at two ends. One junction is kept in a hot area other in cold area. Due to a variation of heat, a very small current (in micro-Amperes) is produced in the loop that can be measured by an ammeter.

**2.8 Hall Effect**

Hall effect is the production of voltage difference across an electrical conductor, transverse to an electric current in the conductor and to an applied magnetic field perpendicular to the current.

By using Hall effect, one can easily identify whether the semiconductor is p-type or n-type. In above figure, a voltage is applied to a conductor or semiconductor, electric current starts flowing through it. In conductor, the electric current conducted by free electrons whereas in semiconductor electric current is conducted by both free electrons and holes. Free electrons in a semiconductor or conductor always try to flow in a straight path. If we apply the force of magnetic field in other direction the free electrons are changed their direction according to the direction of applied magnetic field. If magnetic field direction is fixed according to the type of semiconductor electrons accumulation and deficiency taking place two sides of metal. By using a voltmeter one can measure the hall voltage.

## Chapter 2

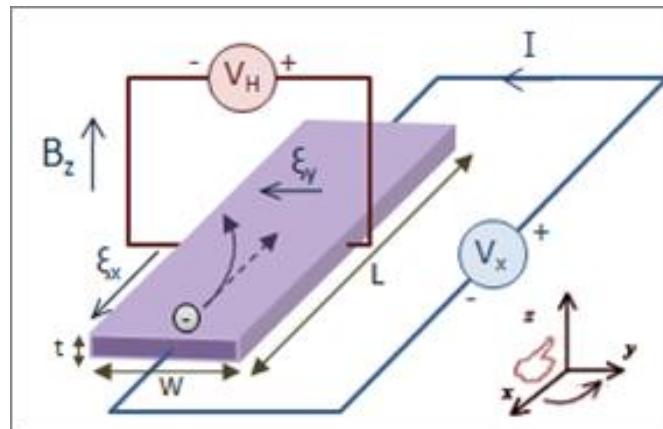


Figure 2.9 – Hall Effect Phenomenon

### 2.9 The P-N Junction Diode

#### 2.9.1 Structure

If we join a piece of P-type material to a piece of N-type material such that the crystal structure remains continuous at the boundary, a PN-junction is formed. Such a PN-junction makes a very useful device. It is called a semiconductor (or crystal) PN junction diode. Like any diode, the PN junction diode has two connections or electrodes. This gives it its name: "di" meaning two and "-ode" as a shortening of electrode.

One electrode of the semiconductor device is termed the *anode* and the other is termed the *cathode*. For a current to flow across the PN diode junction it must be forward biased. Under these conditions' conventional current flows from the anode to the cathode, but not the other way around.


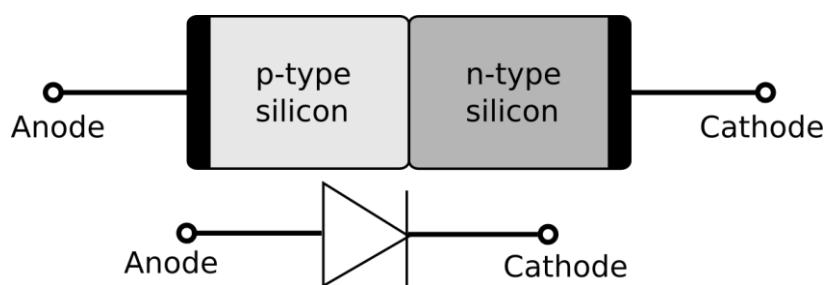
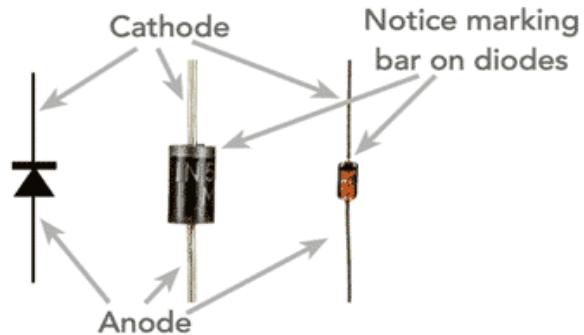


Figure 2.10 – Structure and Symbol of a Diode

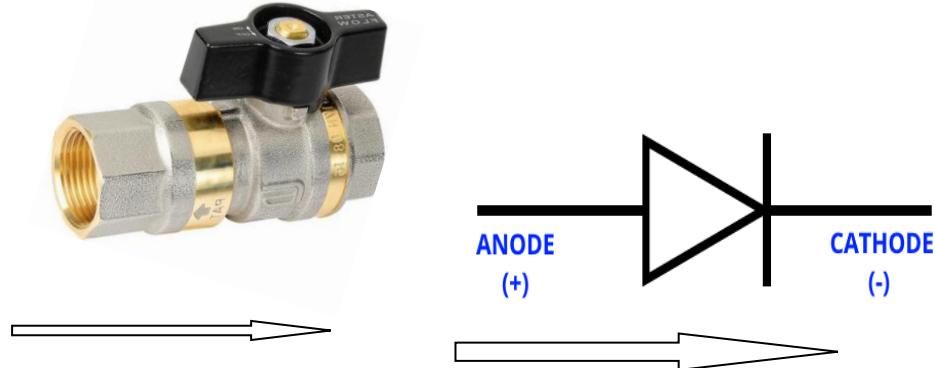

**Figure 2.11 – P-N Junction Diode**

Current flow through the diode is unidirectional (anode to cathode) so it may compare with a non-return valve in mechanical terms.

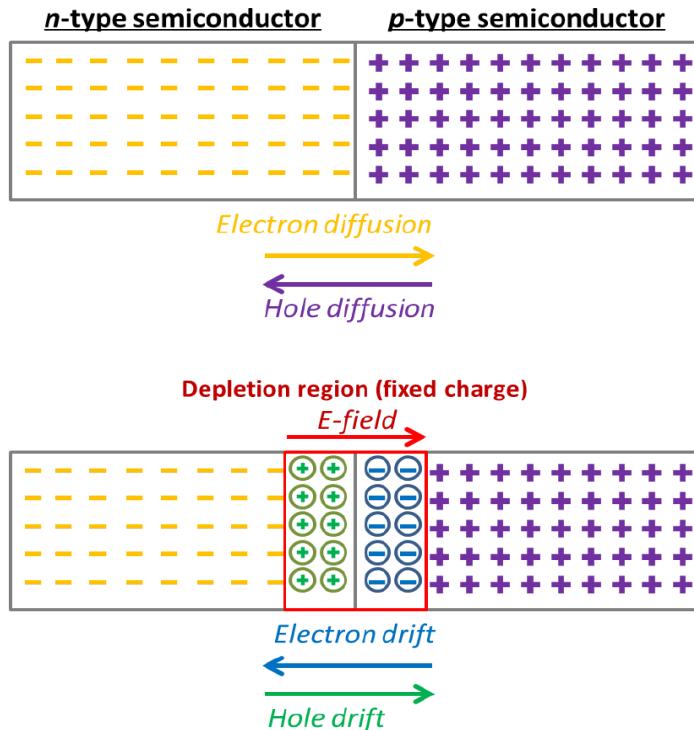


**Figure 2.12 – Water flow through a non-return valve and current flow through a diode**

## Chapter 2

---

### 2.9.2 Operation of a Diode



**Figure 2.13 – Operation of a Diode**

There are two operating regions and three possible “biasing” conditions for the standard Junction Diode and these are-

1. **Zero Bias** – No external potential is applied to the PN junction diode.


Holes from the P region diffuse into the N region. They then combine with the free electrons in the N region. Free electrons from the N region diffuse into the P region. These electrons combine with the hole. At the junction, some of the holes in the P region and some of the free electrons in N region diffuse towards each other and recombine. Each recombination eliminates a hole and a free electron near the junction.

So, the mobile charges are depleted from both sides of junction and that is why this region is termed as the **depletion region** or the **space charge region**.

2. **Reverse Bias** - When a diode is connected in a Reverse-Biased condition, a positive voltage is applied to the N-type material and a negative voltage is applied to the P-type material.

The positive voltage applied to the N-type material attracts electrons towards the positive electrode and away from the junction, while the holes in the P-type end are also attracted away from the junction towards the negative electrode.

The net result is that the depletion layer grows wider due to a lack of electrons and holes and it presents a high-impedance path, almost like an insulator and a high-potential barrier is created across the junction thus preventing current from flowing through the semiconductor material.

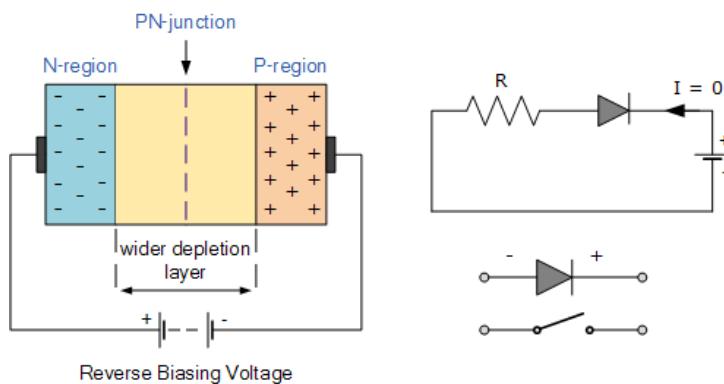

**Figure 2.14 – Reverse-biasing a Diode**

This condition represents a high resistance value to the PN junction and practically zero current flows through the junction diode with an increase in bias voltage. However, a very small reverse leakage current does flow through the junction which can normally be measured in micro-amperes, ( $\mu$ A).

3. **Forward Bias** - When a diode is connected in a **Forward Bias** condition, a negative voltage is applied to the N-type material and a positive voltage is applied to the P-type material.


If the external voltage becomes greater than the value of the potential barrier, approx. 0.7 volts for silicon and 0.3 volts for germanium, the potential barriers opposition will be overcome and current will start to flow.

This is because the negative voltage pushes or repels electrons towards the junction giving them the energy to cross over and combine with the holes being pushed in the opposite direction towards the junction by the positive voltage.

## Chapter 2

---

This results in a characteristics curve of zero current flowing up to this voltage point, called the “knee” on the static curves and then a high current flow through the diode with little increase in the external voltage as shown below.

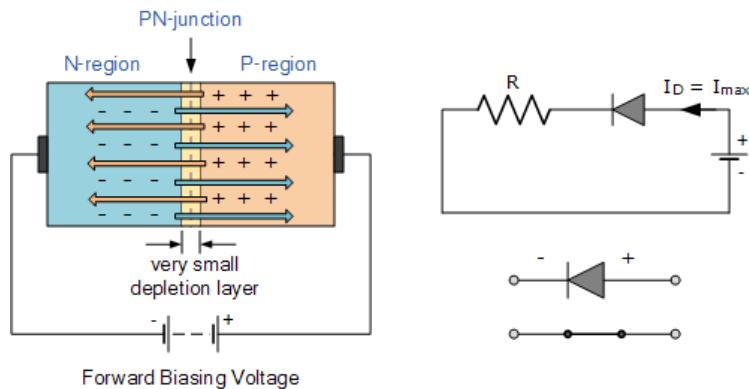

**Figure 2.15 – Reverse-biasing a Diode**

This condition represents the low resistance path through the PN junction allowing very large currents to flow through the diode with only a small increase in bias voltage. Since the diode can conduct “infinite” current above this knee point as it effectively becomes a short circuit, therefore resistors are used in series with the diode to limit its current flow. Exceeding its maximum forward current specification causes the device to dissipate more power in the form of heat than it was designed for resulting in a very quick failure of the device.

### 2.9.3 Rectification by a Diode

The unidirectional conducting property of a diode finds many applications in rectifiers. These are the circuits which convert an ac voltage into a dc voltage.




**Figure 2.16 – Forward-biasing a Diode**

There are three types of diode rectifiers:

- Half-wave rectifier
- Full-wave rectifier
- Bridge rectifier

We shall discuss only a bridge rectifier as other operations are the same as a bridge rectifier.

The bridge rectifier circuit is made of four diodes  $D_1, D_2, D_3, D_4$ , and a load resistor  $R_L$ . The four diodes are connected in a closed-loop configuration to efficiently convert the alternating current (AC) input into a Direct Current (DC) output. The main advantage of this configuration is the absence of the expensive center-tapped transformer. Therefore, the size and cost are reduced.

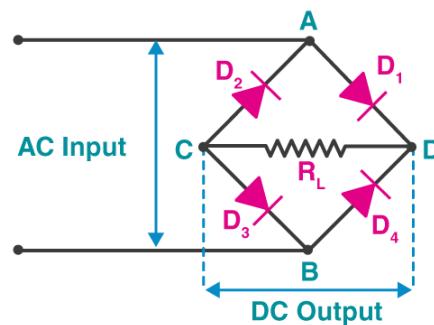

**Figure 2.17 – A Full-wave Bridge Rectifier**


The input signal is applied across terminals A and B and the output DC signal is obtained across the load resistor  $R_L$  connected between terminals C and D. The four diodes are arranged in such a way that only two diodes conduct electricity during each half cycle.  $D_1$  and  $D_3$  conduct electric current during the positive half cycle. Likewise, diodes  $D_2$  and  $D_4$  conduct electric current during a negative half cycle.

#### 2.9.3.1 Working Principle

When an AC signal is applied across the bridge rectifier, during the positive half cycle, terminal A becomes positive while terminal B becomes negative. This results in diodes  $D_1$  and  $D_3$  to become forward-biased while  $D_2$  and  $D_4$  become reverse-biased.


## Chapter 2

---

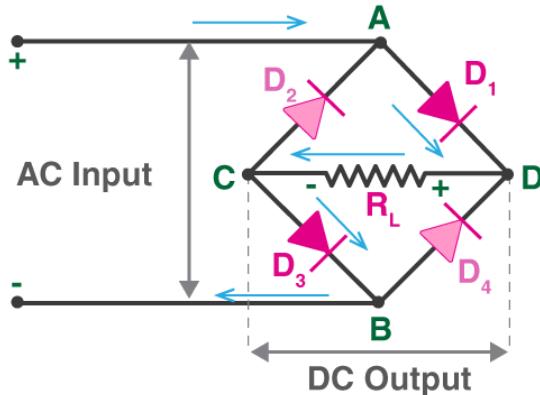

**Figure 2.18 – A Full-wave Bridge Rectifier (+ve Half Cycle)**

During the negative half-cycle, terminal B becomes positive while the terminal A becomes negative. This causes diodes  $D_2$  and  $D_4$  to become forward-biased and diode  $D_1$  and  $D_3$  to be reverse-biased. The current flow during the negative half cycle is shown in the figure below:

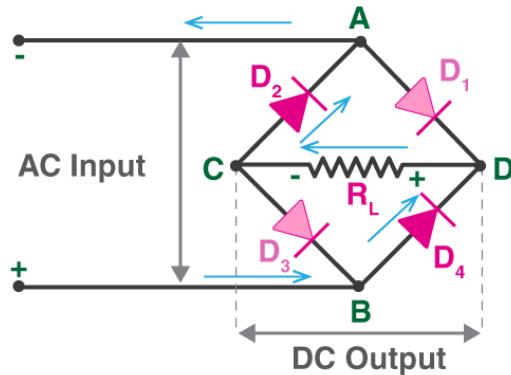

**Figure 2.19 – A Full-wave Bridge Rectifier (-ve Half Cycle)**

From the figures given above, we notice that the current flow across load resistor  $R_L$  is the same during the positive half cycle and the negative half cycles. The output DC signal polarity may be either completely positive or negative. In our case, it is completely positive. If the direction of diodes is reversed then we get a complete negative DC voltage.

Thus, a bridge rectifier allows electric current during both positive and negative half cycles of the input AC signal. The output waveforms of the bridge rectifier are shown in the figure below.

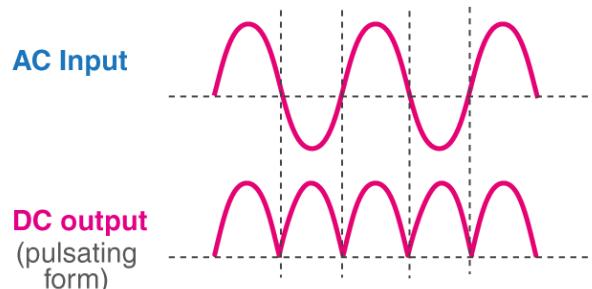


Figure 2.20 – A Full-wave Bridge Rectifier's Input and Output Waveforms

## 2.10 The Transistor

After understanding the working of the diode, which is a single PN junction, let us try to connect two PN junctions which make a new component called a **Transistor**. A Transistor is a three terminal semiconductor device that regulates current or voltage flow and acts as a switch or gate for signals. It is also used to amplify the signal.

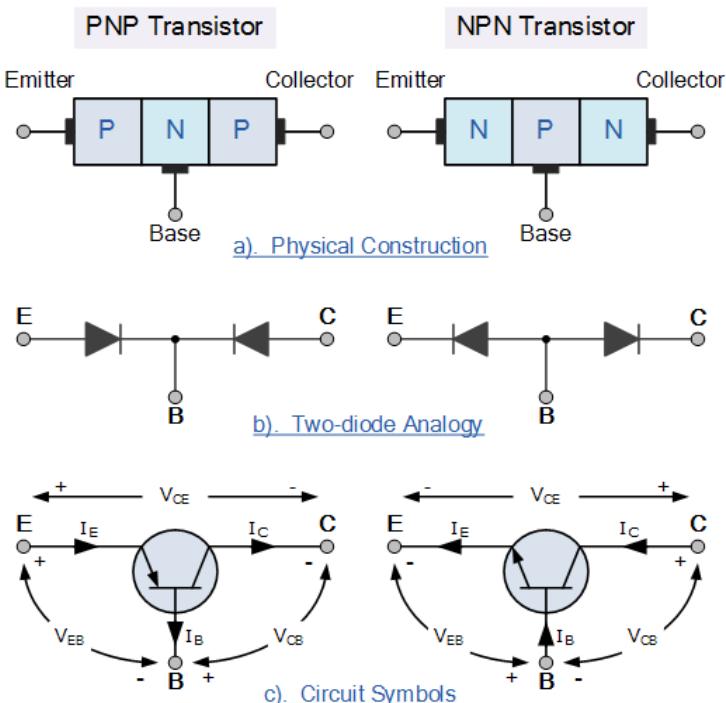


Figure 2.21 – Formation of a Transistor

## Chapter 2

---

The basic construction of a Bipolar Transistor is based on two PN-junctions producing three connecting terminals, with each terminal being given a name to identify it from the other two. These three terminals are known and labeled as the Emitter (E), the Base (B) and the Collector (C) respectively.

### 2.10.1 Configuration

As the Bipolar Transistor is a three-terminal device, there are basically three possible ways to connect it within an electronic circuit with one terminal being common to both the input and output.

- Common Base Configuration – has Voltage Gain but no Current Gain.
- Common Emitter Configuration – has both Current and Voltage Gain.
- Common Collector Configuration – has Current Gain but no Voltage Gain.


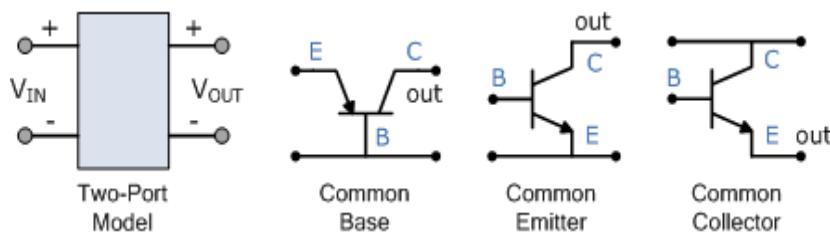


Figure 2.22 – Transistor Configurations

### 2.10.2 The Common Emitter (CE) Configuration

In the Common Emitter or grounded emitter configuration, the input signal is applied between the base and the emitter, while the output is taken from between the collector and the emitter as shown. This type of configuration is the most commonly used circuit for transistor-based amplifiers and which represents the “normal” method of bipolar transistor connection.

The common emitter amplifier configuration produces the highest current and power gain of all the three bipolar transistor configurations. This is mainly because the input impedance is LOW as it is connected to a forward biased PN-junction, while the output impedance is HIGH as it is taken from a reverse biased pn junction.

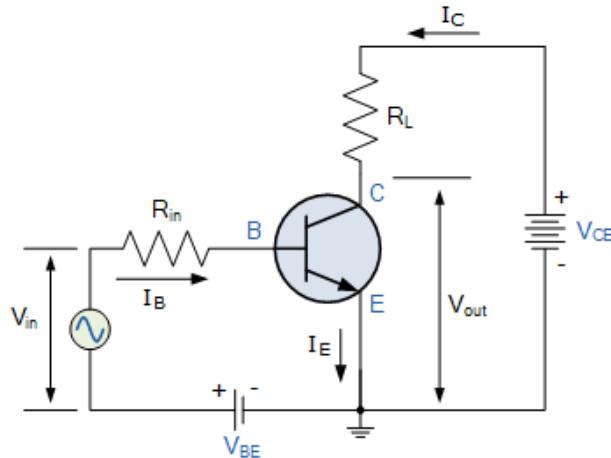

**Figure 2.23 – The CE Configuration**

In this type of configuration, the current flowing out of the transistor must be equal to the currents flowing into the transistor as the emitter current is given as  $I_e = I_c + I_b$ .

As the load resistance ( $R_L$ ) is connected in series with the collector, the current gain of the common emitter transistor configuration is quite large as it is the ratio of  $I_c/I_b$ . A transistors current gain is given the Greek symbol of Beta, ( $\beta$ ).

As the emitter current for a common emitter configuration is defined as  $I_e = I_c + I_b$ , the ratio of  $I_c/I_e$  is called Alpha, given the Greek symbol of  $\alpha$ . Note: that the value of Alpha will always be less than unity.

Since the electrical relationship between these three currents,  $I_b$ ,  $I_c$  and  $I_e$  is determined by the physical construction of the transistor itself, any small change in the base current ( $I_b$ ), will result in a much larger change in the collector current ( $I_c$ ).

Then, small changes in current flowing in the base will thus control the current in the emitter-collector circuit. Typically, Beta has a value between 20 and 200 for most general-purpose transistors. So, if a transistor has a Beta value of say 100, then one electron will flow from the base terminal for every 100 electrons flowing between the emitter-collector terminals.

By combining the expressions for both Alpha,  $\alpha$  and Beta,  $\beta$  the mathematical relationship between these parameters and therefore the current gain of the transistor can be given as:

## Chapter 2

---

$$\text{Alpha, } (\alpha) = \frac{I_C}{I_E} \quad \text{and} \quad \text{Beta, } (\beta) = \frac{I_C}{I_B}$$

$$\therefore I_C = \alpha \cdot I_E = \beta \cdot I_B$$

$$\text{as: } \alpha = \frac{\beta}{\beta + 1} \quad \beta = \frac{\alpha}{1 - \alpha}$$

$$I_E = I_C + I_B$$

Where:

- “Ic” is the current flowing into the collector terminal,
- “Ib” is the current flowing into the base terminal and
- “Ie” is the current flowing out of the emitter terminal.

Then to summaries a little. This type of bipolar transistor configuration has a greater input impedance, current and power gain than that of the common base configuration but its voltage gain is much lower. The common emitter configuration is an inverting amplifier circuit. This means that the resulting output signal has a 180° phase-shift with regards to the input voltage signal.


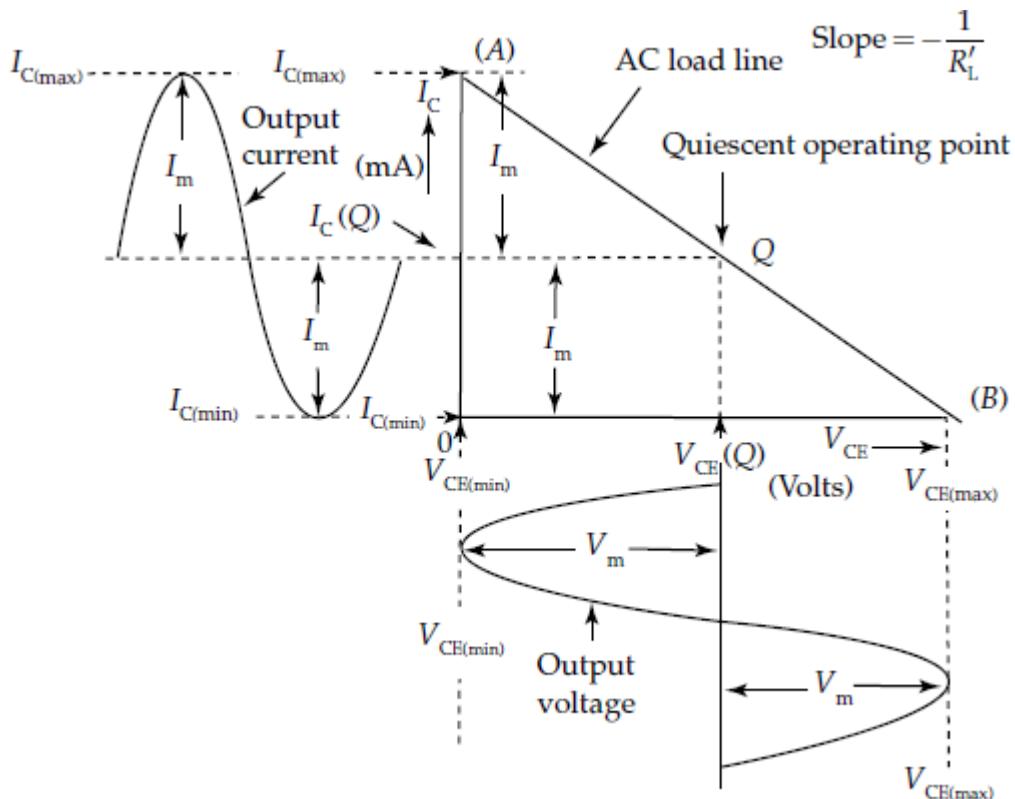


Figure 2.24 –DC load line, active region and amplified signal

Collector Current and Collector Voltage Curves for a Series-fed CE Amplifier

## Chapter 2

---

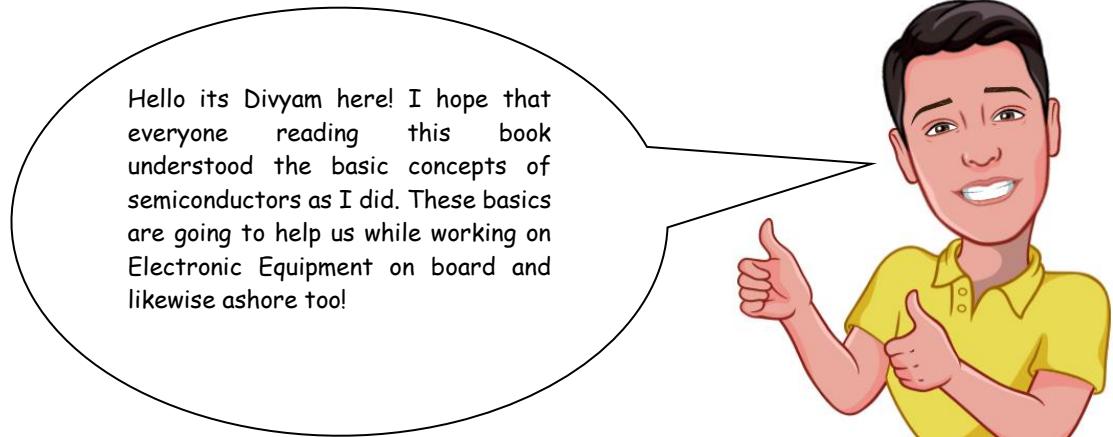

### Sources

- <https://www.electronics-tutorials.ws>
- <https://byjus.com/physics/bridge-rectifier>
- Basic Electronics and Linear Circuits by N N Bhargava
- <https://www.engineeringprojects.com>
- Wikipedia

## Chapter 3

# Silicon Controlled Rectifiers



Sir! Though I've already studied about Thyristors before. But it is a very confusing topic. I find it very difficult to understand its working and applications. Please help me Sir!

Surely Divyam! I hope you are doing fine. Today I am going to clear all your doubts about the Thyristor. It has a wide range of applications e.g., in variable speed motor drives and it is also used in controlling high power electrical applications.



## **Chapter 3**

---

### **3.1 Introduction**

In general, Thyristors are switching devices which are similar to the transistors. Transistors are the tiny electronic components that changed the world, today we can often find them in every electronic device like TVs, mobiles, laptops, calculators, earphones etc. They are adaptable and versatile, but it doesn't mean that they can be used in every application, we can use them as amplifying and switching devices but they cannot handle higher current, also a transistor requires a continuous switching current. So, for all these issues and to overcome these problems we use thyristors.

Generally, the terms SCR and Thyristor (from Thyratron and Transistor) are used interchangeably but the SCR is a kind of Thyristor. The mercury-arc valve was the basis of dc technology back in the day. Engineers in Europe followed the English convention of referring to tubes (vacuum tubes used in early radios) as valves, so the mercury-arc valve name became common.

In 1921, some GE engineers modified the mercury-arc valve with a gas filled tube they called a thyratron. The word thyratron was formed from the Greek words thyra meaning gate and tron meaning tube.

Then in 1957 another group of GE engineers developed the SCR, which many compared to a transistor capable of handling high-power. So, it was natural that someone combined the words thyratron and transistor to form our favored term thyristor. The name became so popular that in 1963 the IEEE (Institute of Electrical and Electronic Engineers) adopted thyristor as the official name.

A Thyristor includes many types of switches, some of them are SCR (Silicon Controlled Rectifier), GTO (Gate Turn OFF), and IGBT (Insulated Gate Controlled Bipolar Transistor) etc. But SCR is the most widely used device, so the word Thyristor became synonymous to SCR. Simply, SCR is a kind of Thyristor.

## Silicon Controlled Rectifiers



Figure 3.1 – A Thyristor

A Thyristor is a four-layered, three-junction semiconductor switching device. It has three terminals namely the anode, cathode, and the gate. The Thyristor is also a unidirectional device like a diode, which means current flows only in one direction.

It consists of three PN junctions in series, as it consists of four layers. The Gate terminal is attached to p-type material near the cathode and is used to trigger the SCR by providing a small voltage to this terminal, which is also called the **Gate-triggering method** to turn on the SCR.

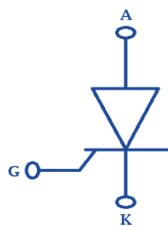


Figure 3.2 – Symbol of a Thyristor

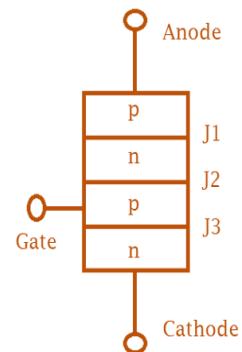


Figure 3.3 – Schematic Diagram of a Thyristor


A variant called an SCS - silicon-controlled switch - brings all four layers out to terminals. The operation of a thyristor can be understood in terms of a pair of tightly coupled bipolar junction transistors, arranged to cause a self-latching action.

## Chapter 3

Thyristors have three states:

1. **Reverse Blocking Mode** - Voltage is applied in the direction that would be blocked by a diode
2. **Forward Blocking Mode** - Voltage is applied in the direction that would cause a diode to conduct, but the thyristor has not yet been triggered into conduction
3. **Forward Conducting Mode** - The thyristor has been triggered into conduction and will remain conducting until the forward current known as the "holding current", drops below a threshold value


### 3.2 The Working Principle of a Thyristor

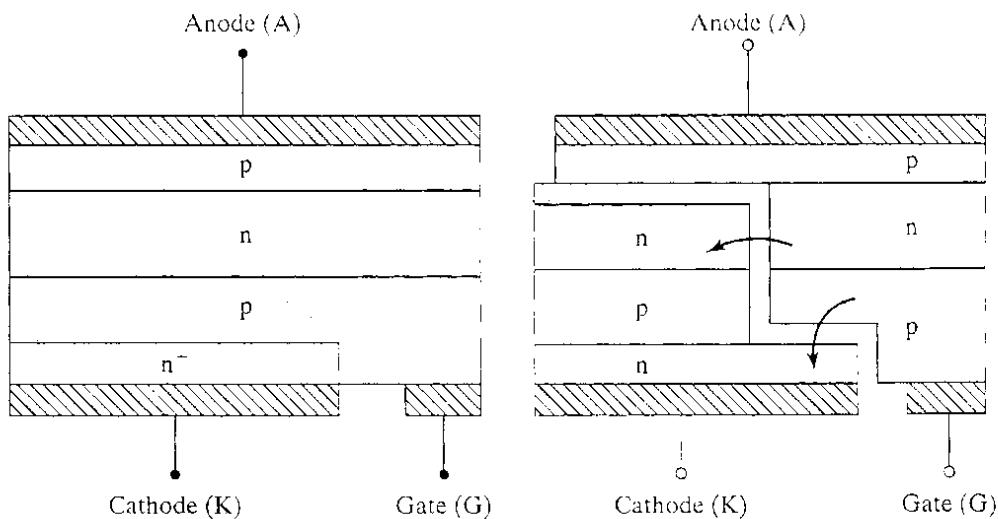

**Figure 3.4 – Formation of a Thyristor**


Junction J2 is reverse biased. Only a very low current flows from A to K. The device is in it's OFF or "Forward Blocking" State.

## Silicon Controlled Rectifiers

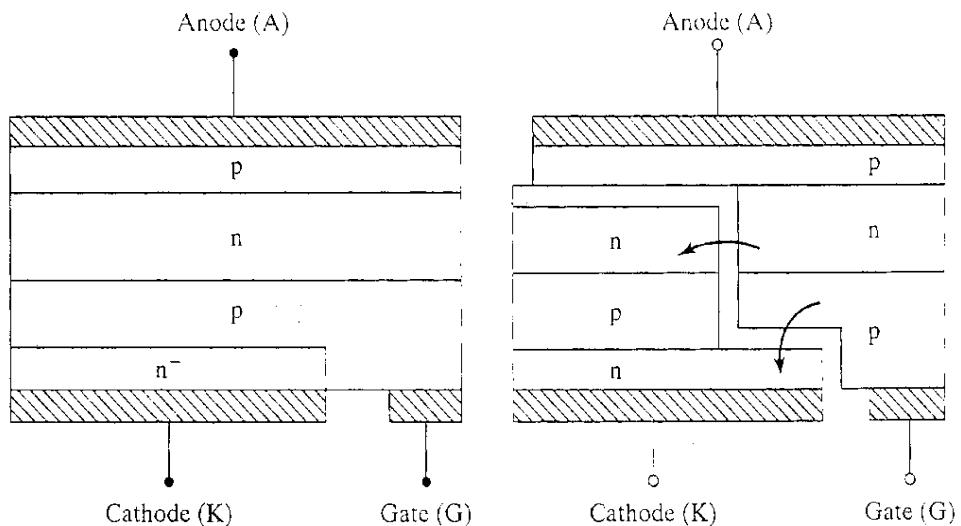

**Figure 3.5 – Forward Blocking State**

Increase the Anode-Cathode voltage until “breakdown” occurs and the Anode current increases; this is the “Conducting state”

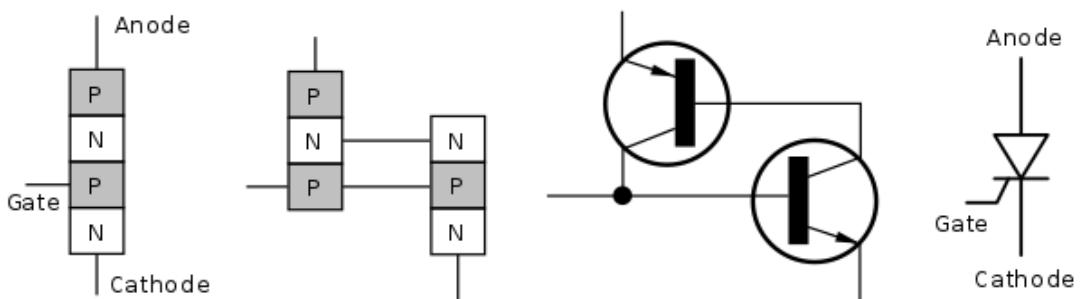

**Figure 3.6 – Structure on The Physical and Electronic Level, and The Symbol**

### 3.3 Function of the Gate Terminal


The thyristor has three p-n junctions (serially namely  $J_1, J_2, J_3$  from the anode).

When the anode is at a positive potential  $V_{AK}$  with respect to the cathode with no voltage applied at the gate, junctions  $J_1$  and  $J_3$  are forward biased, while junction  $J_2$  is reverse biased. As  $J_2$  is reverse biased, no conduction takes place (Off state).

## Chapter 3

---

Now if  $V_{AK}$  is increased beyond the breakdown voltage  $V_{BO}$  of the thyristor, avalanche breakdown of  $J_2$  takes place and the thyristor starts conducting (On state).

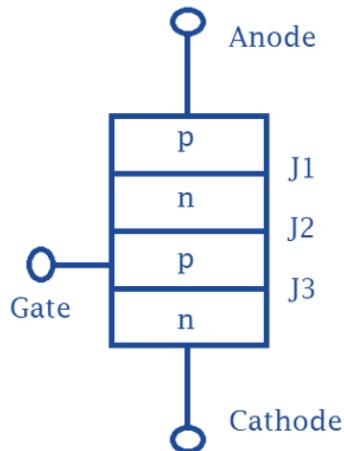

**Figure 3.7 – Schematic Diagram of a Thyristor**


If a positive potential  $V_G$  is applied at the gate terminal with respect to the cathode, the breakdown of the junction  $J_2$  occurs at a lower value of  $V_{AK}$ . By selecting an appropriate value of  $V_G$ , the thyristor can be switched into the on state quickly.

Once an avalanche breakdown has occurred, the thyristor continues to conduct, irrespective of the gate voltage, until: (a) the potential  $V_{AK}$  is removed or (b) the current through the device (anode–cathode) becomes less than the holding current specified by the manufacturer. Hence  $V_G$  can be a voltage pulse, such as the voltage output from a UJT relaxation oscillator.

The gate pulses are characterized in terms of gate trigger voltage ( $V_{GT}$ ) and gate trigger current ( $I_{GT}$ ). Gate trigger current varies inversely with gate pulse width in such a way that it is evident that there is a minimum gate charge required to trigger the thyristor.

### 3.4 Switching Characteristics

In a conventional thyristor, once it has been switched on by the gate terminal, the device remains latched in the on-state (*i.e.*, it does not need a continuous supply of gate current to remain in the On state), provided that the anode current has exceeded the latching current ( $I_L$ ).

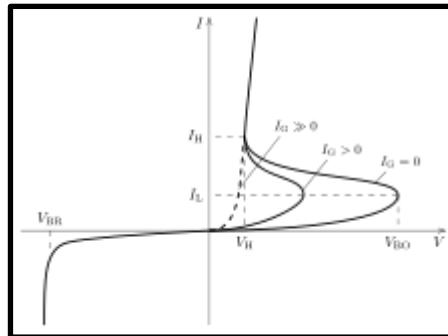

**Figure 3.8 – V-I Characteristics**

As long as the anode remains positively biased, it cannot be switched off unless the current drops below the holding current ( $I_H$ ). In normal working conditions the latching current is always greater than holding current. In the above figure  $I_L$  has to come above the  $I_H$  on y-axis since  $I_L > I_H$ .

A thyristor can be switched off if the external circuit causes the anode to become negatively biased (a method known as natural, or line, commutation). In some applications this is done by switching a second thyristor to discharge a capacitor into the anode of the first thyristor. This method is called *forced commutation*.

After the current in a thyristor has dropped to zero, a finite time delay must elapse before the anode can again be positively biased *and* retain the thyristor in the off-state. This minimum delay is called the circuit commutated turn off time ( $t_Q$ ). Attempting to positively bias the anode within this time causes the thyristor to be self-triggered by the remaining charge carriers (holes and electrons) that have not yet recombined.

For applications with frequencies higher than the domestic AC mains supply (e.g., 50 Hz or 60 Hz), thyristors with lower values of  $t_Q$  are required. Such fast thyristors can be made by diffusing heavy metal ions such as gold or platinum which act as charge combination centers into the silicon.

Today, fast thyristors are more usually made by electron or proton irradiation of the silicon, or by ion implantation. Irradiation is more versatile than heavy metal doping because it permits the dosage to be adjusted in fine steps, even at quite a late stage in the processing of the silicon.

## Chapter 3

### 3.5 Types of Transistors -Their Actions and Characteristics

Thyristors family devices are classified into different types which can be employed for different applications. The triggering signal at the gate terminal causes the thyristor to turn ON and its turn OFF operation depends on the power circuit configuration. So, the external controllability is only to turn ON in case of thyristors

#### 3.5.1 Basic Types of Thyristors

Here we will discuss the various types of thyristors. Thyristors are 2-pin to 4-pin semiconductor devices that act like switches. For example, a 2-pin thyristor only conducts when the voltage across its pins exceeds the breakdown voltage of the device. For a 3-pin thyristor the current path is controlled by the third pin and when a voltage or current is applied to this pin the thyristor conducts. In contrast to transistors, thyristors only work in the ON and OFF states and there is no partial conduction state between these two states. Basic types of thyristors are: SCR, SCS, Triac, Four-layer diode and Diac.


#### 3.5.2 The Four Layer Diode



**Figure 3.9 – Symbol of a Four Layer Diode**

A Four-layer diode has 2 pins and works like a voltage-sensitive switch. When the voltage between the two pins exceeds the breakdown voltage it turns ON, otherwise it's OFF. Current flows from anode to cathode.

#### 3.5.3 The DIAC

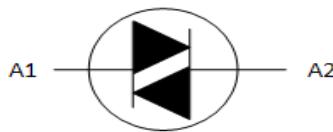

**Figure 3.10 – Symbol of a DIAC**

A DIAC is similar to four-layer diode but it can conduct in both directions meaning it can contact both AC and DC currents.

### 3.5.4 The TRIAC

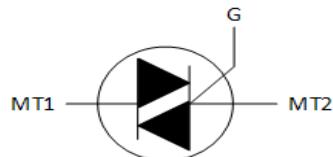


Figure 3.11 – Symbol of a TRIAC

A TRIAC is similar to SCR but it conducts in both directions, meaning that it can switch AC and DC currents. The TRIAC remains in the ON state only when there is current in gate G and it is switched OFF when this current is removed. Current flows in both directions between MT1 and MT2.

### 3.5.5 The Silicon Controlled Rectifier (SCR)


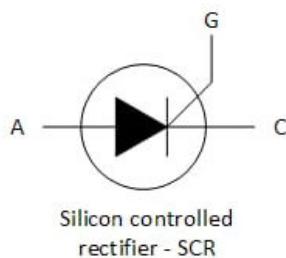


Figure 3.12 – Symbol of an SCR

A Silicon Controlled Rectifier is normally in the OFF state but when a small current enters its gate G it goes to the ON state. If the gate current is removed the SCR remains in ON state and to turn it off the anode to cathode current must be removed or the anode must be set to a negative voltage in relation to cathode. The current only flows in one direction from the anode to the cathode. SCRs are used in switching circuits, phase control circuits, inverting circuits etc.

## Chapter 3

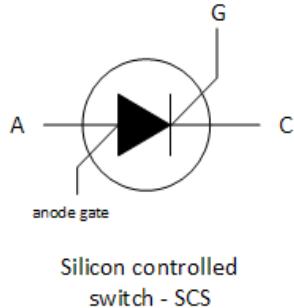

**Figure 3.13 – Symbol of a Silicon Controlled Switch (SCS)**

Working of SCS is similar to SCR but also it can be turned off by applying a positive pulse on the anode gate. The SCS can also be turned ON by applying a negative pulse on anode gate. The current flows only from anode to cathode. SCS are used in counters, lamp drivers, logic circuits etc.

### 3.6 Differences Between a DIAC and a TRIAC

The difference between DIAC and TRIAC include the following.


DIAC	TRIAC
The acronym of the DIAC is “Diode for the alternating current”.	The acronym of the TRIAC is “Triode for the alternating current”.
A DIAC includes two terminals	A TRIAC includes three terminals
It is a bi-directional and uncontrolled device	It is a bi-directional and controlled device.
It can control both positive and negative half cycles of AC signal input.	It can be switched from its off state to ON state for either polarity of the applied voltage.
The DIAC's construction can be done either in NPN otherwise PNP form	The construction of TRIAC can be done with two separate SCRs.
It has less power handling capacity	It has a high-power handling capacity
It doesn't have a firing angle	The firing angle of this device ranges from 0-180° and 180°-360°.
This device plays a key role in activating the TRIAC	This device is used to control the fan, light dimmer, etc.
It has three layers	It has five layers
The advantages of DIAC are, it can be activated by decreasing the level of voltage under its breakdown voltage. Triggering circuit using DIAC is cheap	The advantages of TRIAC are, It can work through the +Ve as well as -Ve polarity of pulses. It uses a single fuse for protection. A secure breakdown can be possible in both directions.

DIAC	TRIAC
The disadvantages of DIAC are, it is a low-power device and doesn't include a control terminal.	The disadvantages of TRIAC are, it is not reliable. As compared with SCR, these have low-ratings. When operating this circuit, we need to be cautious as it can activate in any direction.
The applications of DIAC mainly include different circuits like lamp dimmer, heater control, universal motor speed control, etc.	The applications of TRIAC mainly include control circuits, fans controlling, AC phase control, switching of high-power lamps, and controlling AC power.

### 3.6.1 Characteristics of a DIAC

The V-I characteristics of a DIAC are shown below.

The volt-ampere characteristic of a DIAC is shown in the figure. It looks like a letter Z due to symmetrical switching characteristics for each polarity of the applied voltage.

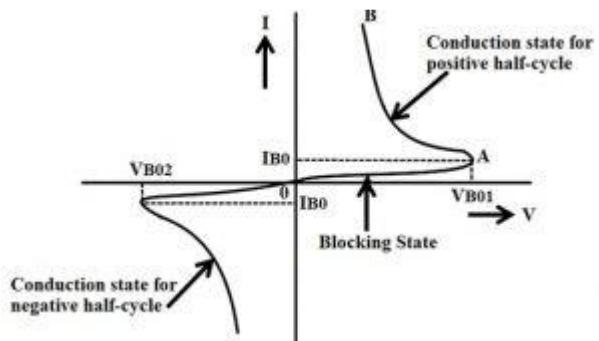

**Figure 3.14 – DIAC Characteristics**

The DIAC performs like an open-circuit until its switching is exceeded. At that position, the DIAC performs until its current decreases toward zero. Because of its abnormal construction, doesn't switch sharply into a low voltage condition at a low current level like the triac or SCR, once it goes into the transmission, the diac preserves an almost continuous –Ve resistance characteristic, which means, voltage reduces with the enlarge in the current.

This means that, unlike the triac and the SCR, the DIAC cannot be estimated to maintain a low voltage drop until its current falls below the level of holding current.

## Chapter 3

---

### 3.6.2 Characteristics of a TRIAC

The V-I characteristics of TRIAC are discussed below.

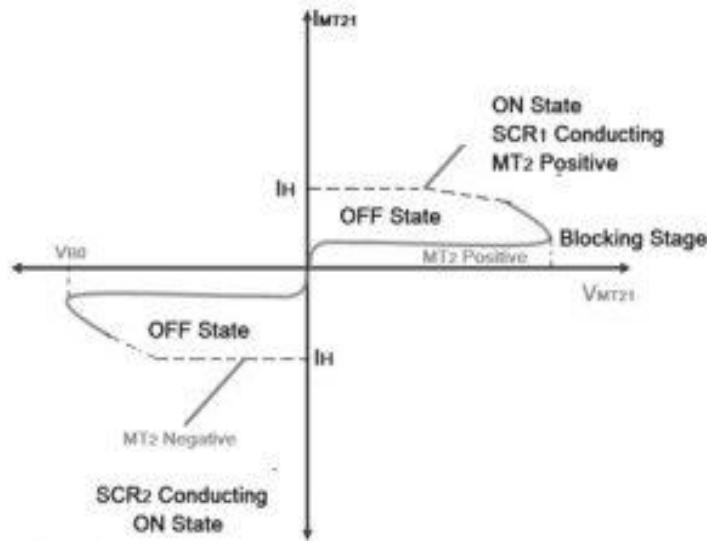


Figure 3.15 – TRIAC Characteristics


The triac is designed with two SCRs which are fabricated in the opposite direction in a crystal. Operating characteristics of triac in the 1st and 3rd quadrants are similar but for the direction of flow of current and applied voltage.

The V-I characteristics of triac in the first and third quadrants are basically equal to those of an SCR in the first quadrant.

It can function with either +Ve or -Ve gate control voltage but in typical operation generally, the gate voltage is +Ve in the first quadrant and -Ve in the third quadrant.

The supply voltage of the triac to switch ON, depends upon the gate current. This allows utilizing a triac to regulate AC power in a load from zero to full power in a smooth and permanent manner with no loss in the device control.

**3.7 Basic Applications of Thyristors:**

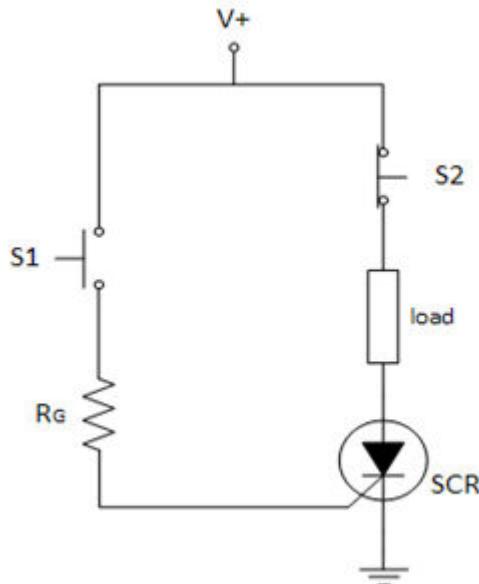

**Figure 3.16 – A Basic Thyristor Circuit**


**3.7.1 Basic Latching Circuit**

In this circuit a SCR is used to form a basic latching circuit. S1 is a normally open switch and S2 is a normally close switch. When S1 is pushed momentary a small current goes into the gate of SCR and turning it ON, thus powering the load. To turn it off we have to push the S2 push-button so the current through SCR stops. Resistor RG is used to set the gate voltage of SCR.

## Chapter 3

---


### 3.7.2 Power Control Circuit

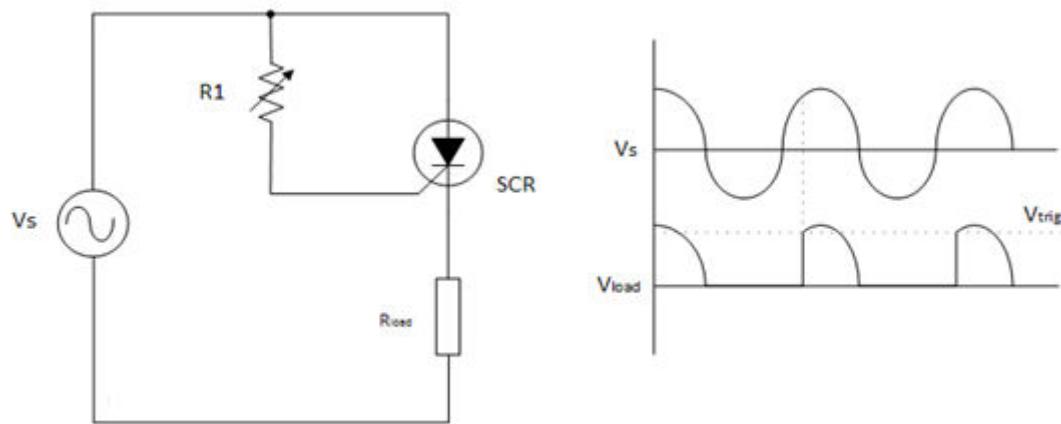

**Figure 3.17 – A Power Control Circuit Using a Thyristor**

In this circuit, an SCR is used to modify a sinusoidal signal so that the load receives less power than what would receive if source voltage was applied directly. The sinusoidal signal is applied to the gate of the SCR via  $R_1$ . When the voltage on the gate exceeds the trigger voltage of the SCR, it goes to ON state and  $V_s$  is applied to the load. During the negative portion of the sine wave the SCR is in OFF state. Increasing  $R_1$  has the effect of decreasing the voltage applied to the gate of the SCR and thus creating a lag in the conduction time. In this way the load is receiving power for less time and thus the average power to load is lower.

### 3.7.3 DC Motor Speed Controller

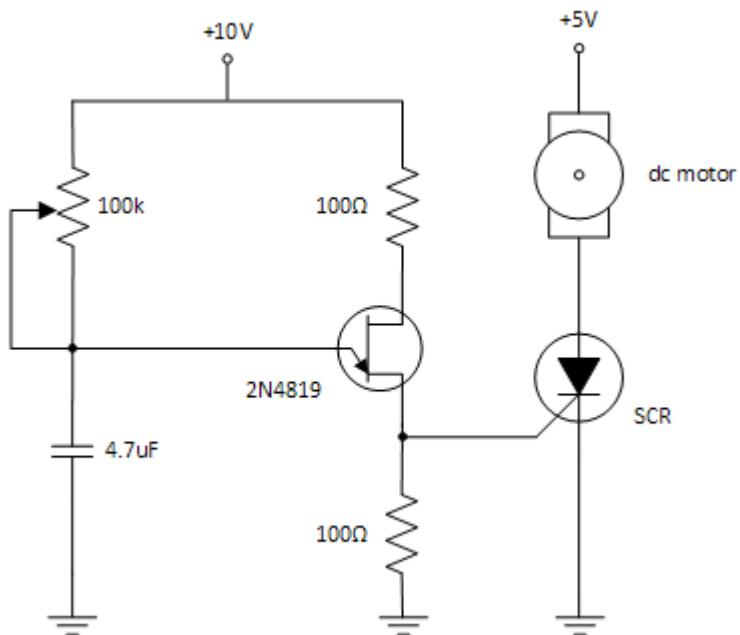

**Figure 3.18 – A DC Motor Controller**

This is a variable speed DC motor controller using a UJT, a SCR and few passive components. A UJT along with resistors and capacitor form an oscillator that supplies AC voltage to the gate of the SCR. When the gate voltage exceeds the triggering voltage of the SCR, the SCR turns ON and the motor is running. By adjusting the potentiometer, the output frequency of the oscillator is changing and thus the times the SCR triggered is changing, which in turn changes the speed of the motor. In this way the motor is receiving a series of pulses that average over time and the speed is adjusted.

### 3.7.4 DIAC and TRIAC Applications

The applications of the DIAC and TRIAC mainly include the following.

- The major application of DIAC is, it can be used in a triggering circuit of the TRIAC by connecting it to the TRIAC's gate terminal. Once the voltage which is applied across the gate terminal decreases under a fixed value, then the voltage at the gate terminal turns to zero and therefore the TRIAC will be deactivated.

## **Chapter 3**

---

- A DIAC is used to build different circuits like lamp dimmer, heat control, the universal motor speed control circuit and starter circuits used in fluorescent lamps.
- A TRIAC is used in the control circuits such as motor control, fan speed controlling, light dimmers, switching of high-power lamps, controlling of AC power in domestic applications.

### **3.7.5 Thyristor Applications**

- Variable speed motor drives.
- Controlling high power electrical applications.
- AC motors, lights, welding machines etc.
- Fault current limiter and circuit breaker.
- Fast switching speed and low conduction is possible in eto thyristor.
- Light dimmers in television, movie theatres.
- Photography for flashes.
- Burglar alarms.
- Electric fan speed control.
- Car ignition switches.

### **3.7.6 Advantages of Thyristors**

- Low cost.
- Can be protected with the help of fuse.
- Can handle large voltage/ current.
- Able to control AC power.
- Very easy to control.
- Easy to turn on.
- The GTO or Gate Turnoff Thyristor has high efficiency.
- Takes less time to operate.
- Thyristor switches can operate with large frequency.
- Requires less space when compared to mechanical switches.

## ***Silicon Controlled Rectifiers***

---


- Can be used for robust operations.
- Maintenance cost of Thyristor is very less.
- Very easy to use for sophisticated controlling.
- Power handling capacity is very good.
- Can be used as an oscillator in digital circuits.
- Can be connected in parallel and in series to provide electronic control at high power levels.
- Thyristors conduct current only in one direction.
- It can be used as a protection device, like a fuse in a power line.

### ***3.7.7 Disadvantages of Thyristors***

- The disadvantages of Thyristor include:
  - Cannot be used for higher frequencies.
  - In AC circuit, Thyristor needs to be turned on each cycle.
  - SCR takes time to turn on and off. This causes delay or damage in the load.
  - It can stop the motor when connected, but cannot hold it stationary.
  - The response rate of Thyristor is very low.
  - Not much use in DC circuits, as the Thyristor cannot be cutoff just by removing the gate drive.
  - Low Efficiency.
  - Latching and Holding current is more in GTO Thyristor.
  - Reverse blocking capability of voltage is less than forward blocking capability.
  - Reliability of TRIAC thyristor is less than SCR.
  - TRIACs have lower dv/dt rating when compared to SCR.

## Chapter 3

---

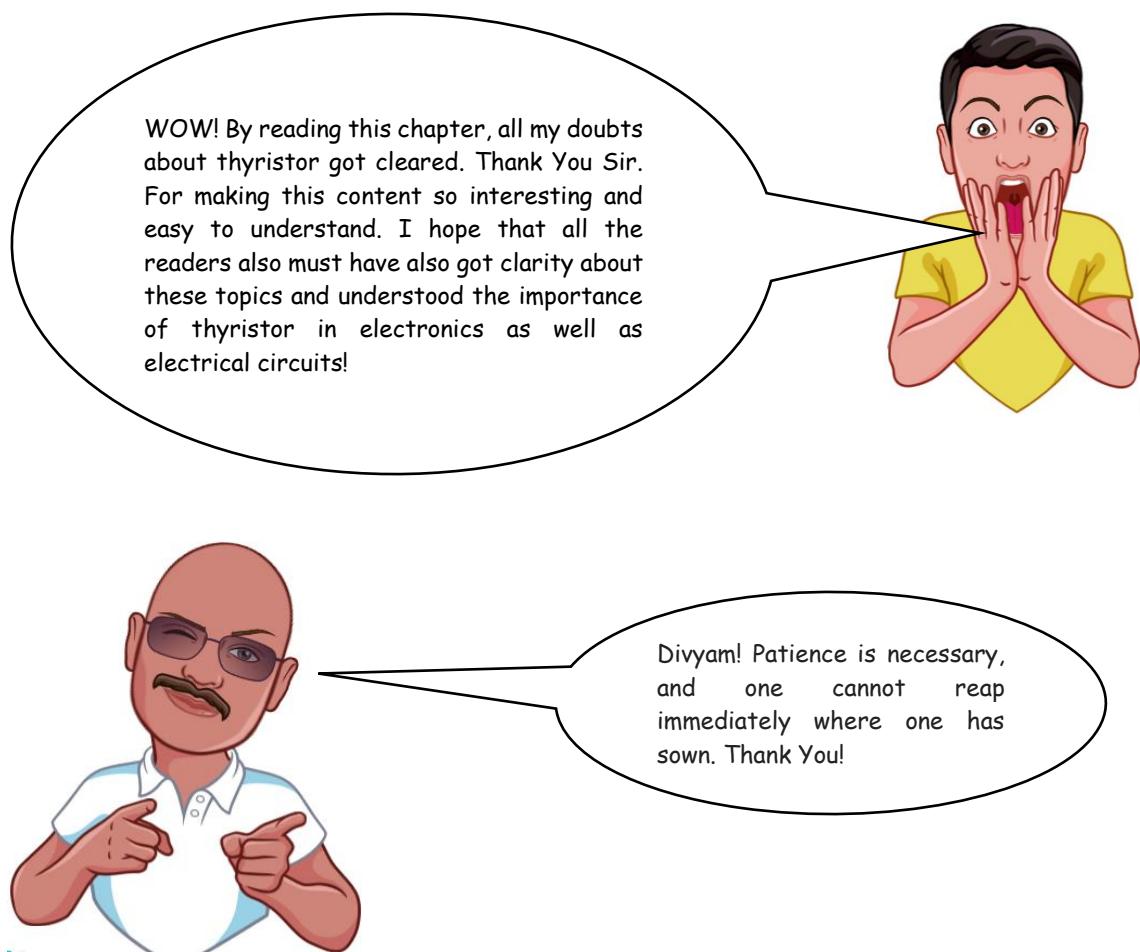

### Sources

- [circuitdigest.com](http://circuitdigest.com)
- [Wikipedia.com](http://Wikipedia.com)
- [electronicshub.com](http://electronicshub.com)
- [electronicslab.com](http://electronicslab.com)
- [elprocus.com](http://elprocus.com)
- [electricalfundablog.com](http://electricalfundablog.com)

## 🚢 Chapter 4 🚢 Power Electronics

---



## Chapter 4

### 4.1 The Unijunction Transistor (UJT)

A unijunction transistor (UJT) is a three-lead electronic semiconductor device with only one junction that acts exclusively as an electrically controlled switch. The UJT is not used as a linear amplifier. It is used in free-running oscillators, synchronized or triggered oscillators, and pulse generation circuits at low to moderate frequencies (hundreds of kilo hertz). It is widely used in the triggering circuits for silicon-controlled rectifiers.

The device has a unique characteristic that when it is triggered, its emitter current increases regeneratively (due to negative resistance characteristic) until it is restricted by emitter power supply. The device is in general, a low-power-absorbing device under normal operating conditions and provides tremendous aid in the continual effort to design relatively efficient systems!

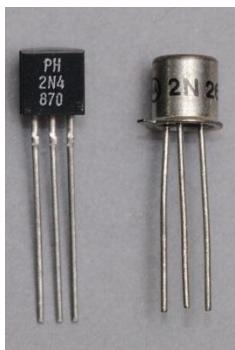


Figure 4.1 – UJT

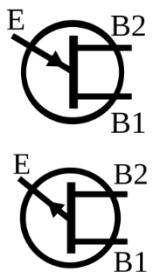


Figure 4.2  
UJT Symbol

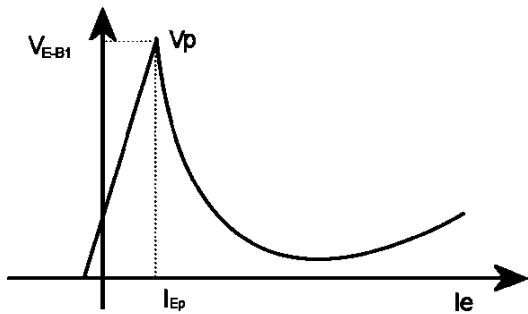


Figure 4.3 – UJT Characteristics

The UJT has three terminals: an emitter (E) and two bases (B1 and B2) and so is sometimes known a “double-base diode”. The base is formed by a lightly doped n-type bar of silicon. Two ohmic contacts B1 and B2 are attached at its ends. The emitter is of p-type is heavily doped; this single PN junction gives the device its name. The resistance between B1 and B2 when the emitter is open-circuit is called interbase resistance. The emitter junction is usually located closer to base-2 (B2) than base-1 (B1) so that the device is not symmetrical, because a symmetrical unit does not provide optimum electrical characteristics for most of the applications.

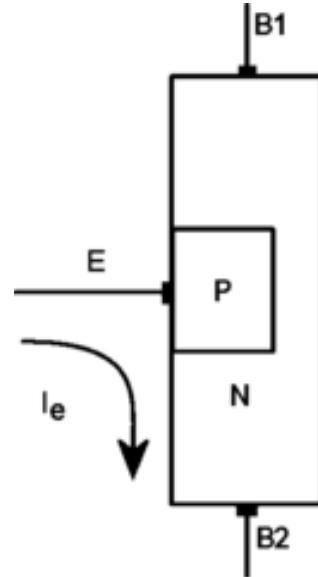


Figure 4.4 – UJT Structure

If no potential difference exists between its emitter and either of its base leads, there is an extremely small current from B1 to B2. On the other hand, if an adequately large voltage relative to its base leads, known as the trigger voltage, is applied to its emitter, then a very large current from its emitter joins the current from B1 to B2, which creates a larger B2 output current.

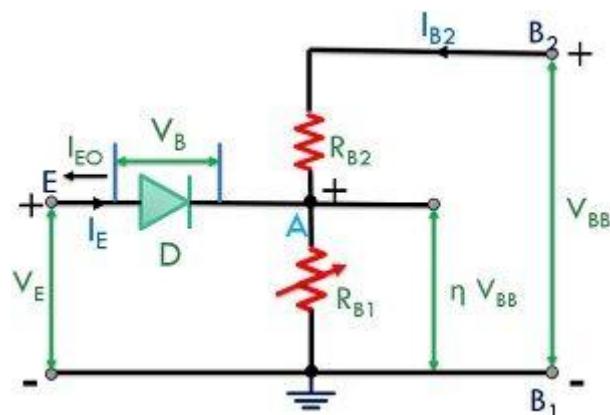


Figure 4.5 – Equivalent Circuit of the UJT

## Chapter 4

---

The symbol for a unijunction transistor represents the emitter lead with an arrow, showing the direction of conventional current when the emitter-base junction is conducting a current. A complementary UJT uses a p-type base and an n-type emitter, and operates the same as the n-type base device but with all voltage polarities reversed.

The device has a unique characteristic that when it is triggered, its emitter current increases regeneratively until it is restricted by emitter power supply. It exhibits a negative resistance characteristic and so it can be employed as an oscillator.

The UJT is biased with a positive voltage between the two bases. This causes a potential drop along the length of the device. When the emitter voltage is driven approximately one diode voltage above the voltage at the point where the P diffusion (emitter) is, current will begin to flow from the emitter into the base region. Because the base region is very lightly doped, the additional current (actually charges in the base region) causes conductivity modulation which reduces the resistance of the portion of the base between the emitter junction and the B2 terminal. This reduction in resistance means that the emitter junction is more forward biased, and so even more current is injected.

Overall, the effect is a negative resistance at the emitter terminal. This is what makes the UJT useful, especially in simple oscillator circuits.


### 4.2 The Field Effect Transistor (FET)

The field-effect transistor (FET) is a type of transistor that uses an electric field to control the flow of current. FETs are devices with three terminals: source, gate, and drain. FETs control the flow of current by the application of a voltage to the gate, which in turn alters the conductivity between the drain and source. FETs are also known as unipolar transistors since they involve single-carrier-type operation. That is, FETs use either electrons or holes as charge carriers in their operation, but not both. Many different types of field effect transistors exist. Field effect transistors generally display very high input impedance at low frequencies. The most widely used field-effect transistor is the MOSFET (metal-oxide-semiconductor field-effect transistor).

#### 4.2.1 Operation

The concept of the field effect transistor is based around the concept that charge on a nearby object can attract charges within a semiconductor channel. It essentially operates using an electric field effect - hence the name. The FET consists of a semiconductor channel with electrodes at either end referred to as the drain and the source.

A control electrode called the gate is placed in very close proximity to the channel so that its electric charge is able to affect the channel. In this way, the gate of the FET controls the flow of carriers (electrons or holes) flowing from the source to drain. It does this by controlling the size and shape of the conductive channel.

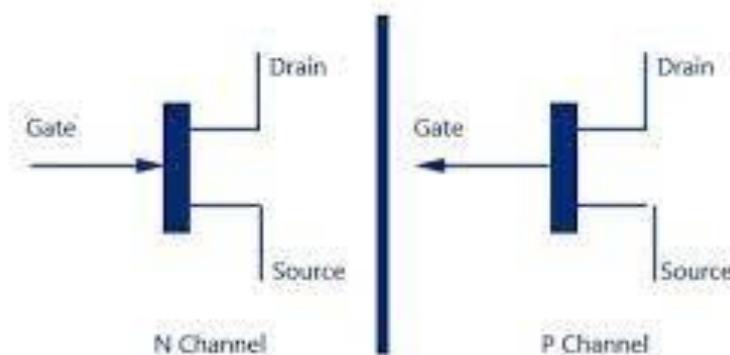

**Figure 4.6 – Field Effect Transistor (FET)**

The semiconductor channel where the current flow occurs may be either P-type or N-type. This gives rise to two types or categories of FET known as P-Channel and N-Channel FETs.

In addition to this, there are two further categories. Increasing the voltage on the gate can either deplete or enhance the number of charge carriers available in the channel.

As a result, there are enhancement mode FET and depletion mode FETs. As it is only the electric field that controls the current flowing in the channel, the device is said to be voltage operated and it has a high input impedance, usually many megohms. This can be a distinct advantage over the bipolar transistor that is current operated and has a much lower input impedance.

Using FETs, circuits like voltage amplifiers, buffers or current followers, oscillators, filters and many more can all be designed, and the circuits are very similar to those for bipolar transistors and even thermionic valves / vacuum tubes. Interestingly valves / tubes are also voltage operated devices, and therefore their circuits are very similar, even in terms of the bias arrangements.

## Chapter 4

### 4.2.2 Field Effect Transistor Types

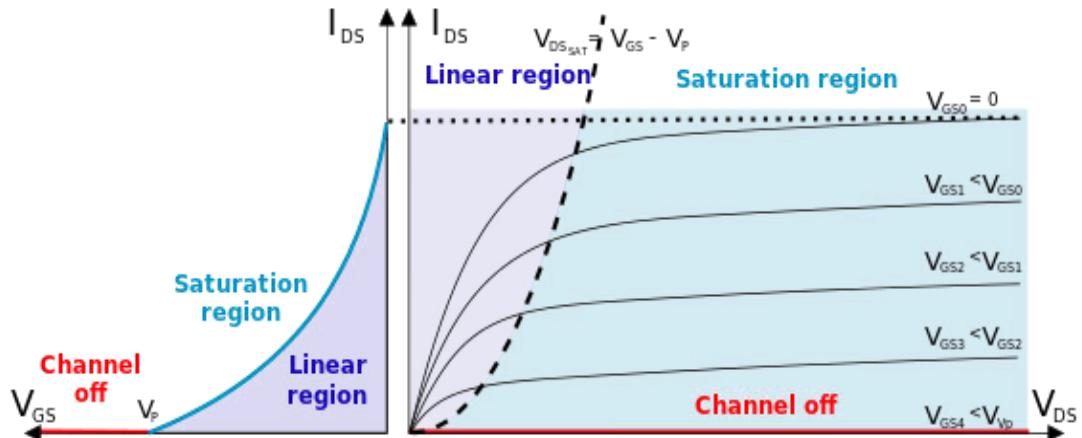


Figure 4.7 – FET Characteristics

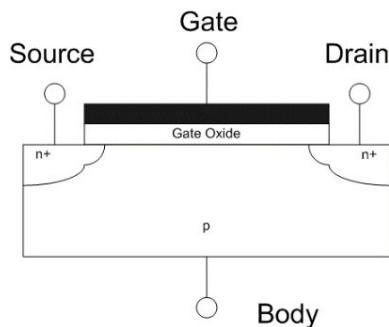


Figure 4.8 – FET Structure

There are many ways to define the different types of FET that are available. The different types mean that during the electronic circuit design, there is a choice of the right electronic component for the circuit. By selecting the right device, it is possible to obtain the best performance for the given circuit. There are many different types of FET on the market for which there are various names. Some of the major categories are detailed below.

- **Junction FET, JFET** The junction FET, or JFET uses a reverse biased diode junction to provide the gate connection. The structure consists of a semiconductor channel which can be either N-type or P-type. A semiconductor diode is then fabricated onto the channel in such a way that the voltage on the diode affects the FET channel. In operation this is reverse biased and this means that it is effectively isolated from the channel - only the diode reverse current can flow between the two. The JFET is the most basic type of FET, and the one that was first developed. However, it still provides excellent service in many areas of electronics.
- **Insulated Gate FET / Metal Oxide Silicon FET MOSFET:** The MOSFET uses an insulated layer between the gate and the channel. Typically, this is formed from a layer of oxide of the semiconductor. The name IGFET refers to any type of FET that has an insulated gate. The most common form of IGFET is the silicon MOSFET - Metal Oxide Silicon FET. Here, the gate is made of a layer of metal set down on the silicon oxide which in turn is on the silicon channel. MOSFETs are widely used in many areas of electronics and particularly within integrated circuits. The key factor of the IGFET / MOSFET is the exceedingly high gate impedance these FETs are able to provide. That said, there will be an associated capacitance and this will reduce the input impedance as the frequency rises.
- **Dual Gate MOSFET** This is a specialised form of MOSFET that has two gates in series along the channel. This enables some considerable performance improvements to be made, especially at RF, when compared to single gate devices. The second gate of the MOSFET provides additional isolation between the input and output, and in addition to this it can be used in applications like mixing / multiplication.
- **MESFET** The MEtal Silicon FET is normally fabricated using Gallium Arsenide and is often referred to as a GaAs FET. Often GaAsFETs are used for RF applications where they can provide high gain low noise performance. One of the drawbacks of GaAsFET technology results from the very small gate structure, and this makes its very sensitive to damage from static, ESD. Great care must be taken when handling these devices.
- **HEMT / PHEMT** The High Electron Mobility Transistor and Pseudomorphic High Electron Mobility Transistor are developments of the basic FET concept, but developed to enable very high frequency operation. Although expensive, they enable very high frequencies and high levels of performance to be achieved.
- **FinFET** FinFET technology is now being used within integrated circuits to enable higher levels of integration to be achieved by allowing smaller feature sizes.

## Chapter 4

- As higher density levels are needed and it becomes increasingly difficult to realise ever smaller feature sizes, FinFET technology is being used more widely.
- **VMOS** VMOS standard for vertical MOS. It is a type of FET that uses a vertical current flow to improve the switching and current carrying performance. VMOS FETs are widely used for power applications.

### 4.3 The Insulated Gate Bipolar Transistor (IGBT)

IGBT is a relatively new device in power electronics and before the advent of IGBT, Power MOSFETs and Power BJT were common in use in power electronic applications. Both of these devices possessed some advantages and simultaneously some disadvantages. On one hand, we had bad switching performance, low input impedance, secondary breakdown and current controlled Power BJT and on the other we had excellent conduction characteristics of it. Similarly, we had excellent switching characteristics, high input impedance, voltage controlled PMOSFETs, which also had bad conduction characteristics and problematic parasitic diode at higher ratings. Though the unipolar nature of PMOSFETs leads to low switching times, it also leads to high ON-state resistance as the voltage rating increases. Thus, the need was for such a device which had the goodness of both PMOSFETs and Power BJT and this was when IGBT was introduced in around the early 1980s and became very popular among power electronic engineers because of its superior characteristics. IGBT has PMOSFET like input characteristics and Power BJT like output characteristics and hence its symbol is also an amalgamation of the symbols of the two parent devices. The three terminals of IGBT are Gate, Collector and Emitter.

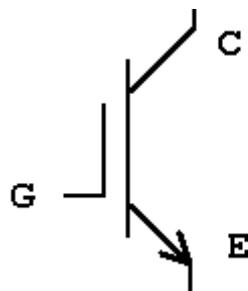
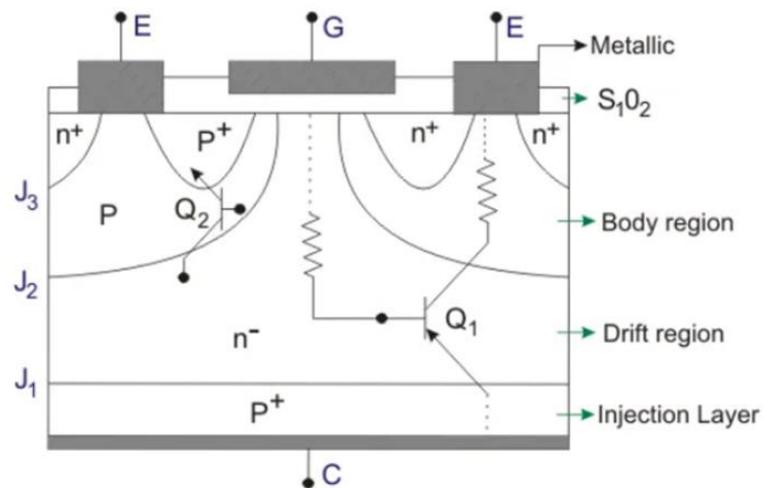


Figure 4.9 – An FET's Symbol

#### 4.3.1 Structure of the IGBT

The structure of IGBT is very much similar to that of PMOSFET, except one layer known as injection layer which is p+ unlike n+ substrate in PMOSFET. This injection layer is the key to the superior characteristics of IGBT. Other layers are called the drift and the body region. The two junctions are labelled J1 and J2. Figure below show the structure of n-channel IGBT.

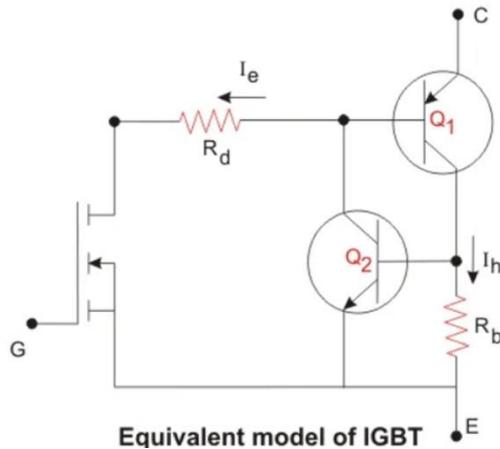


**Figure 4.10 – Structure of an IGBT**

Upon careful observation of the structure, we'll find that there exists an n-channel MOSFET and two BJTs - Q1 and Q2 as shown in the figure. Q1 is p+n-p BJT and Q2 is n-pn + BJT.  $R_d$  is the resistance offered by the drift region and  $R_b$  is the resistance offered by p body region. We can observe that the collector of Q1 is same as base of Q2 and collector of Q2 is same as base of Q1. Hence, we can arrive at an equivalent circuit model of IGBT as shown in the figure below.

## Chapter 4

---



**Figure 4.11**

The two-transistor back-to-back connection forms a parasitic thyristor as shown in the above figure. N-channel IGBT turns ON when the collector is at a positive potential with respect to emitter and gate also at sufficient positive potential ( $>V_{GET}$ ) with respect to emitted.

This condition leads to the formation of an inversion layer just below the gate, leading to a channel formation and a current begins to flow from collector to emitter. The collector current  $I_c$  in IGBT constitutes of two components-  $I_e$  and  $I_h$ .  $I_e$  is the current due to injected electrons flowing from collector to emitter through injection layer, drift layer and finally the channel formed.  $I_h$  is the hole current flowing from collector to emitter through  $Q_1$  and body resistance  $R_b$ . Hence

$$I_c = I_e + I_h$$

Although  $I_h$  is almost negligible and hence

$$I_c \approx I_e.$$

A peculiar phenomenon is observed in IGBT known as Latching up of IGBT. This occurs when collector current exceeds a certain threshold value ( $I_{CE}$ ). In this the parasitic thyristor gets latched up and the gate terminal loses control over collector current and IGBT fails to turn off even when gate potential is reduced below  $V_{GET}$ . For turning OFF of IGBT now, we need typical commutation circuitry as in the case of forced commutation of thyristors. If the device is not turned off as soon as possible, it may get damaged.

### 4.3.2 Characteristics of IGBT

#### 4.3.2.1 Static I-V Characteristics of the IGBT

The figure below shows static i-v characteristics of an n-channel IGBT along with a circuit diagram with the parameters marked.

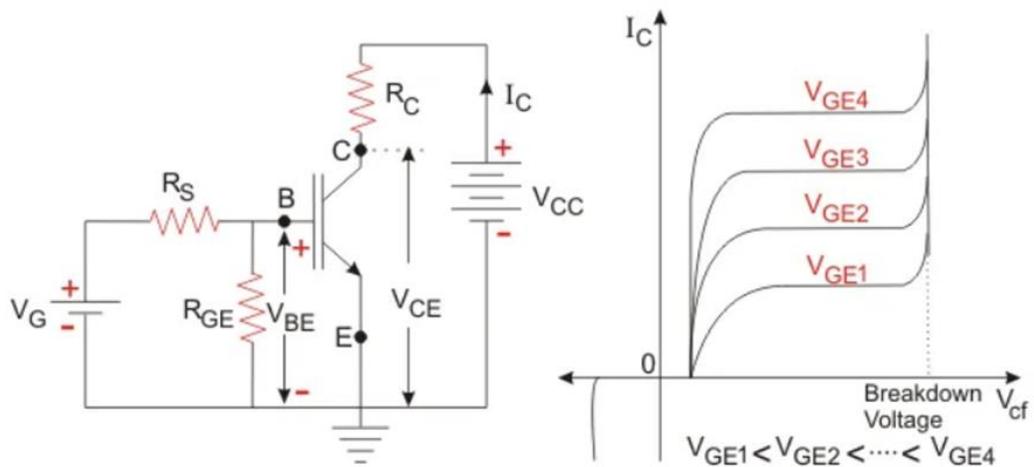


Figure 4.12 – Circuit Diagram and V-I Characteristics

The graph is similar to that of a BJT except that the parameter which is kept constant for a plot is  $V_{GE}$  because IGBT is a voltage-controlled device unlike BJT which is a current controlled device. When the device is in OFF mode ( $V_{CE}$  is positive and  $V_{GE} < V_{GET}$ ) the reverse voltage is blocked by J2 and when it is reverse biased, i.e.,  $V_{CE}$  is negative, J1 blocks the voltage.


#### 4.3.2.2 Switching Characteristics of the IGBT

The figure below shows the typical switching characteristic of IGBT. Turn on time  $t_{on}$  is composed of two components as usual, delay time ( $t_{dn}$ ) and rise time ( $t_r$ ). Delay time is defined as the time in which collector current rises from leakage current  $I_{CE}$  to 0.1  $I_C$  (final collector current) and collector-emitter voltage falls from  $V_{CE}$  to 0.9  $V_{CE}$ . Rise time is defined as the time in which collector current rises from 0.1  $I_C$  to  $I_C$  and collector-emitter voltage falls from 0.9  $V_{CE}$  to 0.1  $V_{CE}$ .

$$t_{on} = t_{dn} + t_r$$

## Chapter 4

---

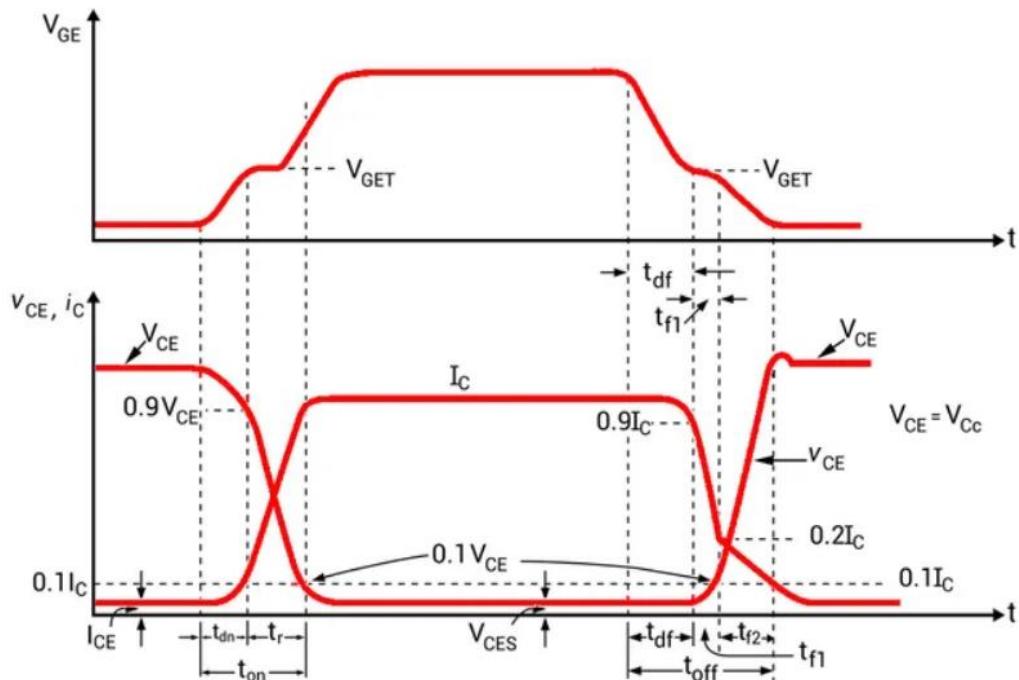

**Figure 4.13 – Typical Switching Characteristics of an IGBT**

The turn off time  $t_{off}$  consists of three components, delay time ( $t_{df}$ ), initial fall time ( $t_{f1}$ ) and final fall time ( $t_{f2}$ ). Delay time is defined as time when collector current falls from  $I_C$  to  $0.9 I_C$  and  $V_{CE}$  begins to rise. Initial fall time is the time during which collector current falls from  $0.9 I_C$  to  $0.2 I_C$  and collector emitter voltage rises to  $0.1 V_{CE}$ . The final fall time is defined as time during which collector current falls from  $0.2 I_C$  to  $0.1 I_C$  and  $0.1 V_{CE}$  rises to final value  $V_{CE}$ .

$$t_{off} = t_{df} + t_{f1} + t_{f2}$$

### 4.3.2.3 Advantages of the IGBT

- Lower gate drive requirements
- Low switching losses
- Small snubber circuitry requirements
- High input impedance
- Voltage controlled device


- Temperature coefficient of ON state resistance is positive and less than PMOSFET, hence less On-state voltage drop and power loss.
- Enhanced conduction due to bipolar nature
- Better Safe Operating Area

#### 4.3.2.4 Disadvantages of the IGBT

- Cost
- Latching-up problem
- High turn off time compared to PMOSFET

#### 4.4 The Gate Turn-off Thyristor (GTO)

A gate turn-off thyristor (GTO) is a special type of thyristor, which is a high-power semiconductor device. It was invented by General Electric.[1] GTOs, as opposed to normal thyristors, are fully controllable switches which can be turned on and off by their third lead, the gate lead. Normal thyristors (silicon-controlled rectifiers) are not fully controllable switches (a “fully controllable switch” can be turned on and off at will). Thyristors can only be turned ON using the gate lead, but cannot be turned OFF using the gate lead. Thyristors are switched ON by a gate signal, but even after the gate signal is de-asserted (removed), the thyristor remains in the ON-state until a turn-off condition occurs (which can be the application of a reverse voltage to the terminals, or a decrease of the forward current below a certain threshold value known as the “holding current”).

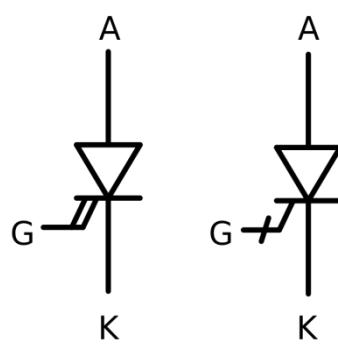

**Figure 4.14 – GTO Symbol**

## Chapter 4

---

Thus, a thyristor behaves like a normal semiconductor diode after it is turned on or “fired”. The GTO can be turned on by a gate signal, and can also be turned off by a gate signal of negative polarity. Turn on is accomplished by a “positive current” pulse between the gate and cathode terminals.

As the gate-cathode behaves like PN junction, there will be some relatively small voltage between the terminals. The turn on phenomenon in GTO is however, not as reliable as an SCR (thyristor) and small positive gate current must be maintained even after turn on to improve reliability. Turn off is accomplished by a “negative voltage” pulse between the gate and cathode terminals.

Some of the forward current (about one-third to one-fifth) is “stolen” and used to induce a cathode-gate voltage which in turn causes the forward current to fall and the GTO will switch off (transitioning to the 'blocking' state.)

GTO thyristors suffer from long switch off times, whereby after the forward current falls, there is a long tail time where residual current continues to flow until all remaining charge from the device is taken away. This restricts the maximum switching frequency to approx 1 kHz.

It may be noted however, that the turn off time of a GTO is approximately ten times faster than that of a comparable SCR. To assist with the turn-off process, GTO thyristors are usually constructed from a large number (hundreds or thousands) of small thyristor cells connected in parallel.

GTO thyristors are available with or without reverse blocking capability. Reverse blocking capability adds to the forward voltage drop because of the need to have a long, low doped P1 region. GTO thyristors capable of blocking reverse voltage are known as Symmetrical GTO thyristors, abbreviated S-GTO. Usually, the reverse blocking voltage rating and forward blocking voltage rating are the same. The typical application for symmetrical GTO thyristors is in current source inverter. GTO thyristors incapable of blocking reverse voltage are known as asymmetrical GTO thyristors, abbreviated A-GTO, and are generally more common than Symmetrical GTO thyristors. They typically have a reverse breakdown rating in the tens of volts. A-GTO thyristors are used where either a reverse conducting diode is applied in parallel (for example, in voltage source inverters) or where reverse voltage would never occur (for example, in switching power supplies or DC traction choppers). GTO thyristors can be fabricated with a reverse conducting diode in the same package. These are known as RCGTO, for Reverse Conducting GTO thyristor.

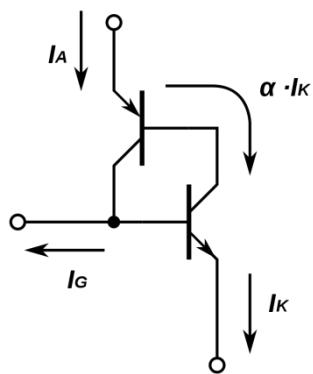


Figure 4.115(a) – GTO Structure

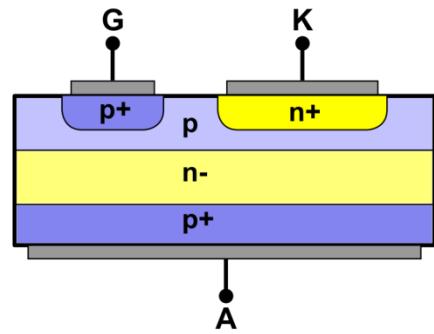


Figure 4.15(b) – GTO Equivalent

Unlike the insulated gate bipolar transistor (IGBT), the GTO thyristor requires external devices (“snubber circuits”) to shape the turn on and turn off currents to prevent device destruction. During turn on, the device has a maximum  $dI/dt$  rating limiting the rise of current. This is to allow the entire bulk of the device to reach turn on before full current is reached. If this rating is exceeded, the area of the device nearest the gate contacts will overheat and melt from over current.

The rate of  $dI/dt$  is usually controlled by adding a saturable reactor (turn-on snubber), although turn-on  $dI/dt$  is a less serious constraint with GTO thyristors than it is with normal thyristors, because of the way the GTO is constructed from many small thyristor cells in parallel. Reset of the saturable reactor usually places a minimum off time requirement on GTO based circuits. During turn off, the forward voltage of the device must be limited until the current tails off.

The limit is usually around 20% of the forward blocking voltage rating. If the voltage rises too fast at turn off, not all of the device will turn off and the GTO will fail, often explosively, due to the high voltage and current focused on a small portion of the device. Substantial snubber circuits are added around the device to limit the rise of voltage at turn off.


Resetting the snubber circuit usually places a minimum on time requirement for GTO based circuits. The minimum on and off time is handled in DC motor chopper circuits by using a variable switching frequency at the lowest and highest duty cycle. This is observable in traction applications where the frequency will ramp up as the motor starts, then the frequency stays constant over most of the speed ranges, then the frequency drops back down to zero at full speed.

## Chapter 4

The main applications are in variable speed motor drives, high power inverter and traction. GTOs are increasingly being replaced by integrated gate-commutated thyristors, which are an evolutionary development of the GTO, and insulated gate bipolar transistors, which are members of the transistor family.

### 4.5 The Integrated Gate-Commuted Thyristor (IGCT)

The integrated gate-commutated thyristor (IGCT) is a power semiconductor electronic device, used for switching electric current in industrial equipment. It is related to the gate turn-off (GTO) thyristor. An IGCT is a special type of thyristor. It is made of the integration of the gate unit with the Gate Commutated Thyristor (GCT) wafer device. The close integration of the gate unit with the wafer device ensures fast commutation of the conduction current from the cathode to the gate. The wafer device is similar to a gate turn-off thyristor (GTO). They can be turned on and off by a gate signal, and withstand higher rates of voltage rise ( $dv/dt$ ), such that no snubber is required for most applications. The structure of an IGCT is very similar to a GTO thyristor

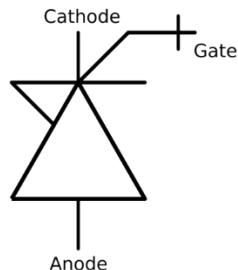


**Figure 4.16 – 7.11 Symbol**

. In an IGCT, the gate turn-off current is greater than the anode current. This results in a complete elimination of minority carrier injection from the lower PN junction and faster turn-off times. The main differences are a reduction in cell size, and a much more substantial gate connection with much lower inductance in the gate drive circuit and drive circuit connection. The very high gate currents and fast  $dI/dt$  rise of the gate current mean that regular wires can not be used to connect the gate drive to the IGCT. The drive circuit PCB is integrated into the package of the device. The drive circuit surrounds the device and a large circular conductor attaching to the edge of the IGCT is used. The large contact area and short distance reduce both the inductance and resistance of the connection.

The IGCT's much faster turn-off times compared to the GTO's allows it to operate at higher frequencies up to several kHz for very short periods of time. However, because of high switching losses, tyIGCT are available with or without reverse blocking capability. Reverse blocking capability adds to the forward voltage drop because of the need to have a long, low-doped P1 region.

IGCTs capable of blocking reverse voltage are known as symmetrical IGCT, abbreviated S-IGCT.

Usually, the reverse blocking voltage rating and forward blocking voltage rating are the same. The typical application for symmetrical IGCTs is in current source inverters. IGCTs incapable of blocking reverse voltage are known as asymmetrical IGCT, abbreviated A-IGCT. They typically have a reverse breakdown rating in the tens of volts. A-IGCTs are used where either a reverse conducting diode is applied in parallel (for example, in voltage source inverters) or where reverse voltage would never occur (for example, in switching power supplies or DC traction choppers). Asymmetrical IGCTs can be fabricated with a reverse conducting diode in the same package. These are known as RC-IGCT, for reverse conducting IGCT. typical operating frequency is up to 500 Hz.

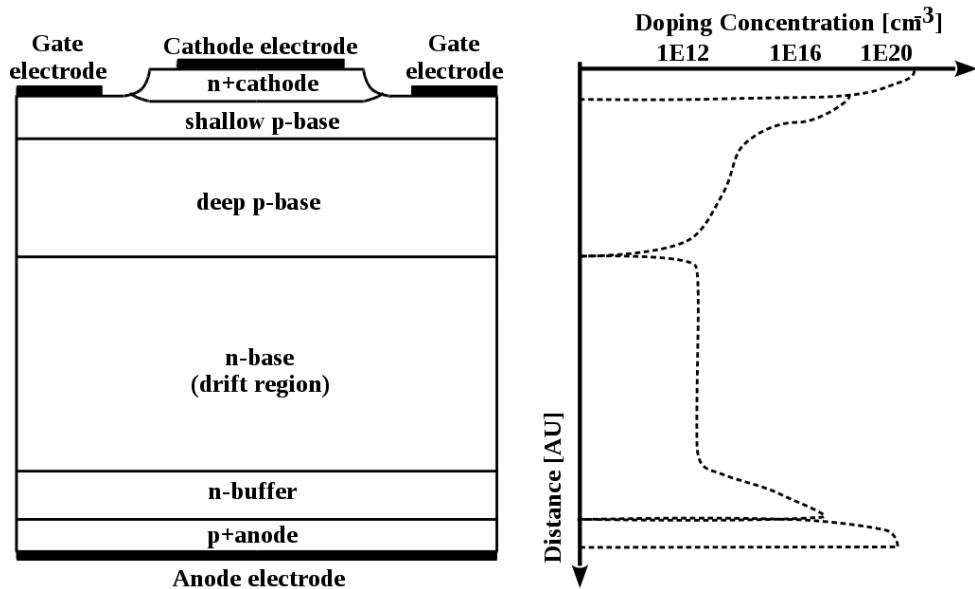


**Figure 4.17 – IGCT Structure**

## Chapter 4

### 4.6 Power Electronic Converters

Power electronic converters are used everywhere in normal daily routines at home, commercial workplaces or in industrial environments like factories and ships. Due to the high-power handling with higher efficiencies, these converters become an integral part of industrial electric drives, high electric power supplies, electric traction systems and automobile control equipments. There are different types of power electronic converters used for performing different functions (such as inversion, rectification, etc.) which are rated from a few milliwatts to a few thousand watts.

Power electronic technology deals with processing and controlling the flow of electrical energy in order to supply voltages and currents in a form that optimally suited for end user's requirements. A power electronic converter uses power electronic components such as SCRs, TRIACs, IGBTs, etc. to control and convert the electric power. The main aim of the converter is to produce conditioning power with respect to a certain application. The block diagram of a power electronic converter is shown in figure below.

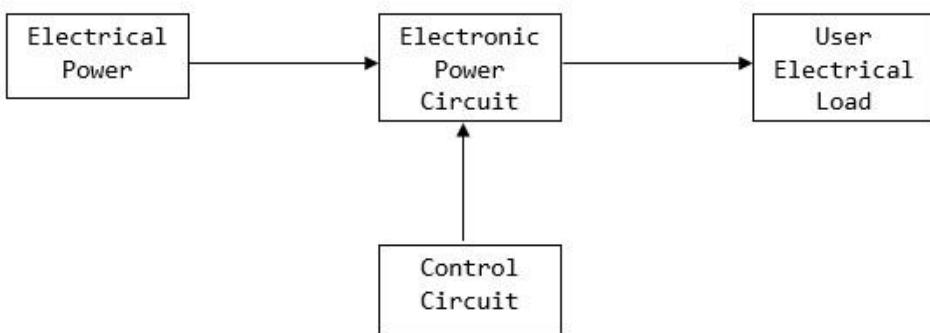

**Figure 4.18 – Power Electronic Converter**

It consists of an electrical energy source, power electronic circuit, a control circuit and an electric load. This converter changes one form of electrical energy to other form of electrical energy. The power electronic circuit consists of both power part and control part.

Power part transfers the energy from source to load and it consists of power electronic switches (SCR or TRIAC), transformers, electric choke, capacitors, fuses and sometimes resistors.


The control circuit or block regulates the elements in the power part of the converter. This block is built with a complex low power electronic circuit that consists of either analog or digital circuit assembly. Power electronic converters perform various basic power conversion functions. This converter is a single power conversion stage that can perform any of the functions in AC and DC power conversion systems. Depending on the type of function performed, power electronic converters are categorized into following types.

- **AC to DC is a Rectifier:** It converts AC to unipolar (DC) current
- **DC to AC is an Inverter:** It converts DC to AC of desired frequency and voltage
- **DC to DC is a Chopper:** It converts constant to variable DC or variable DC to constant DC
- **AC to AC is a Cycloconverter, Matrix Converter:** It converts AC of desired frequency and / or desired voltage magnitude from a line AC supply.

These types of power electronic converters may be found in a wide variety of applications such as switch mode power supplies (SMPS), electrical machine control, energy storage systems, lighting drives, active power filters, power generation and distribution, renewable energy conversion, flexible AC transmission and embedded technology.

#### 4.7 AC to DC Converters or Rectifiers

An AC to DC converter is also called a rectifier, which converts AC supply from main lines to DC supply for the load. The block diagram of an AC to DC converter is shown in figure below. The essential components in this rectifier include transformer, switching unit, filter and a control block.

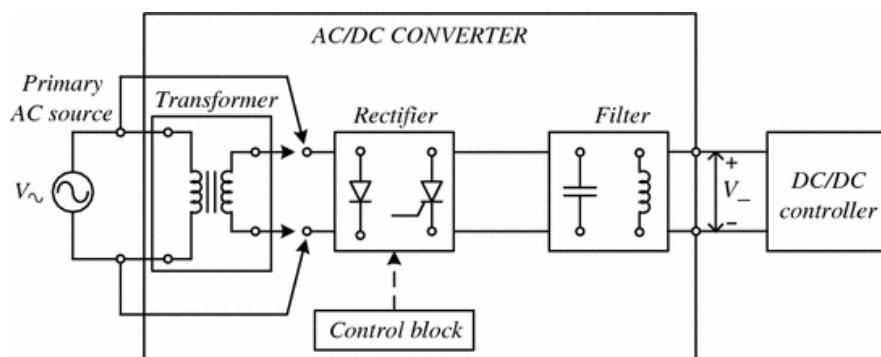

**Figure 4.19 – A Basic Controlled Rectifier Circuit**

## Chapter 4

---

Here, the transformer adjusts the primary AC source supply to the input of rectifier stage. Usually, it is a step-down transformer that reduces the supply voltage to a circuit operating range. The rectifier converts the low voltage AC supply into DC supply. It comprises diode and/or thyristors based on type of rectifier. The output of the rectifier is of pulsed DC and hence it is filtered using filter circuit, which is usually made with a capacitor or a choke. The control block controls the firing angle of thyristors in case of phase-controlled rectifiers. Since the diode is not a controllable device, control block is not needed in case of diode rectifiers.

Rectifiers are majorly classified into two types

- a) Uncontrolled diode rectifiers
- b) Controlled rectifiers

### a) Uncontrolled Diode Rectifiers

This type of rectifier converts AC voltage from mains into a fixed DC voltage. Since the diodes are uncontrollable components (which do not require any triggering), these converters are called as uncontrolled converters as they produce a fixed voltage. The input voltage can be either single phase or three-phase.

The diode rectifiers are classified into following types.


1. Single phase half-wave rectifier
2. Single phase center-tapped full-wave rectifier
3. Single phase full-wave bridge rectifier
4. Three-phase Half-wave diode rectifier
5. Three-phase full-wave diode bridge rectifier

#### 1. Single Phase Half-Wave Rectifier

The half wave rectifier is a type of rectifier that rectifies only half cycle of the waveform. The half rectifier consists of a step-down transformer, a diode connected to the transformer and a load resistance connected to the cathode end of the diode. The circuit diagram of half wave transformer is shown in the image.

The main supply voltage is given to the transformer which will increase or decrease the voltage and give to the diode. In most of the cases we will decrease the supply voltage by using the step-down transformer here also the output of the step-down transformer will be in AC.

This decreased AC voltage is given to the diode which is connected serial to the secondary winding of the transformer, diode is electronic component which will allow only the forward bias current and will not allow the reverse bias current. From the diode we will get the pulsating DC and give to the load resistance  $R_L$ . The input given to the rectifier will have both positive and negative cycles. The half rectifier will allow only the positive half cycles and omit the negative half cycles. So first we will see how half wave rectifier works in the positive half cycles.

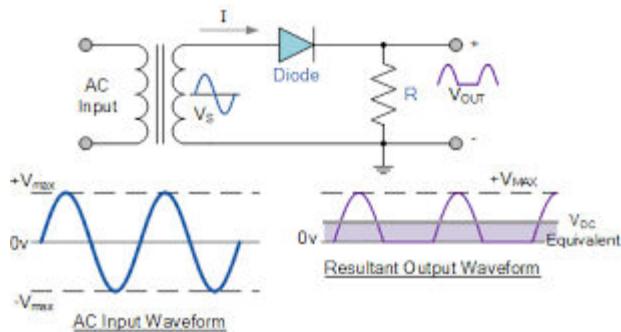

**Figure 4.20 – A Half Wave Rectifier**

## 2. Single Phase Center-Tapped Full-Wave Rectifier

Center tap is the contact made at the middle of the winding of the transformer. In the center tapped full wave rectifier two diodes were used. These are connected to the center tapped secondary winding of the transformer. The circuit diagram shows the center tapped full wave rectifier. It has two diodes. The positive terminal of two diodes is connected to the two ends of the transformer. Center tap divides the total secondary voltage into equal parts. The primary winding of the center tap transformer is applied with the AC voltage.

Thus, the two diodes connected to the secondary of the transformer conducts alternatively. For the positive half cycle of the input diode D1 is connected to the positive terminal and D2 is connected to the negative terminal. Thus, diode D1 is in forward bias and the diode D2 is reverse biased. Only diode D1 starts conducting and thus current flows from diode and it appears across the load  $R_L$ . So positive cycle of the input is appeared at the load. During the negative half cycle the diode D2 is applied with the positive cycle. D2 starts conducting as it is in forward bias. The diode D1 is in reverse bias and this does not conduct.

## Chapter 4

---

Thus, current flows from diode D<sub>2</sub> and hence negative cycle is also rectified, it appears at the load resistor R<sub>L</sub>. By comparing the current flow through load resistance in the positive and negative half cycles, it can be concluded that the direction of the current flow is same.

Thus, the frequency of rectified output voltage is two times the input frequency. The output that is rectified is not pure, it consists of a DC component and a lot of AC components of very low amplitudes.

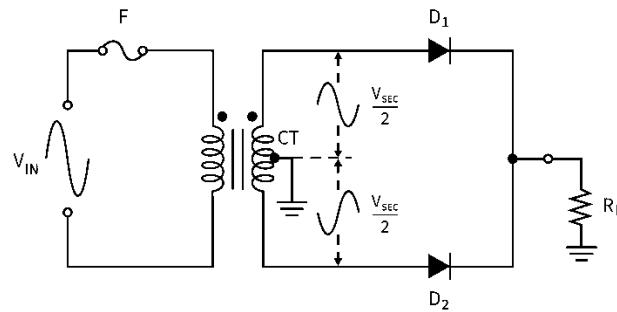


Figure 4.21 – A Centre-Tapped Rectifier

### 3. Single Phase Full-Wave Bridge Rectifier

Bridge is a type of electrical circuit. Bridge rectifier is a type of rectifier in which diodes were arranged in the form of a bridge. This provides full wave rectification and is of low cost. So it is used in many applications. In bridge rectifier four diodes are used. These are connected as shown in the circuit diagram. The four diodes are connected in the form of a bridge to the transformer and the load as shown.

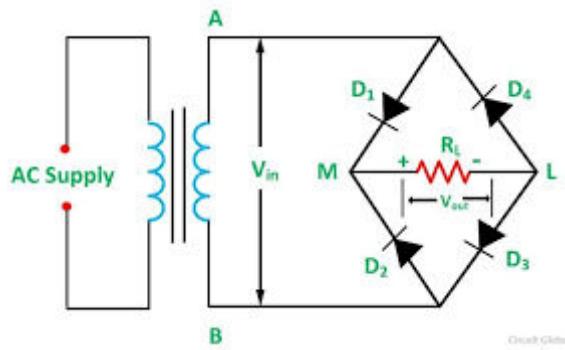



Figure 4.22 – A Full-Wave Bridge Rectifier

The working of a bridge rectifier is simple. The circuit diagram of bridge rectifier is given above. The secondary winding of the transformer is connected to the two diametrically opposite points of the bridge at points 1 and 3. Assume that a load is connected at the output.

The load  $R_L$  is connected to bridge through points 2 and 4. During first half cycle of the AC input, the upper portion of the transformer secondary winding is positive with respect to the lower portion. Thus, during the first half cycle diodes D1 and D4 are forward biased. Current flows through path 1-2, enter into the load  $R_L$ . It returns back flowing through path 4-3. During this half input cycle, the diodes D2 and D3 are reverse biased. Hence there is no current flow through the path 2-3 and 1-4. During the next cycle lower portion of the transformer is positive with respect to the upper portion. Hence during this cycle diodes D2 and D3 are forward biased. Current flows through the path 3-2 and flows back through the path 4-1. The diodes D1 and D4 are reverse biased. So, there is no current flow through the path 1-2 and 3-4. Thus, negative cycle is rectified and it appears across the load.

#### 4. Three-phase Half-Wave Diode Rectifier

It employs three diodes and its anode terminals are connected to three phase source via transformer as shown in figure. The load is connected between the common cathode point and neutral terminal of star connected source. When R-phase is at its peak value, maximum conduction occurs through diode D1 as it is forward biased and no conduction takes place through it during negative alteration of phase R. During Y-phase and B-phase maximum values, other two diodes conduct in a similar manner. The main disadvantage of this rectifier is that the secondary winding consists of DC component of current which can cause the transformer core to go under saturation problem. Therefore, it is not advisable to use three-phase half-wave rectifier for large power applications.

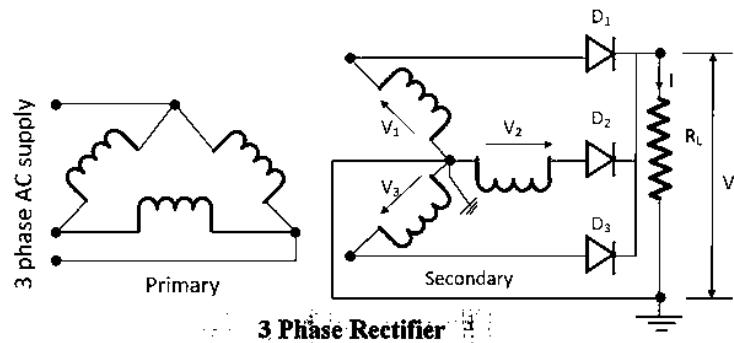

**Figure 4.23 – A Three-phase Half-wave Rectifier**

## Chapter 4

---

### 5. Three-Phase Full-Wave Diode Bridge Rectifier

This type of rectifiers is suitable for high power applications, typically the power output higher than 15KW. The circuit of full-wave diode bridge rectifier is shown in figure. It requires six diodes for the operation of the circuit. This type of circuit doesn't need any neutral connection from three phase source therefore; a star as well as delta-connected sources can be used. Here the output current flows through one diode of the upper group and one diode of lower group of diodes. If anode of a diode is at high potential, this upper group diode will conduct while other two diodes are reversed biased. Similarly, the diode having the cathode at lower potential will conduct while other two diodes are off. The diode pair's conduction for above circuit is given as D6 D1, D1 D2, D2 D3, D3 D4, D4 D5 and D6 D1. Since, one diode from upper group and one diode from lower group are always conducting; negative members of three- phase voltages are rectified, so the output voltage consists of six segments of line voltage during one cycle. For this reason, three phase bridge rectifiers are called as six pulse rectifiers. These are efficient rectifier as compared to half-wave converters. Due to six pulse output, ripple content in the output is very low, typically about 4.5%. This avoids the additional filter circuit in many high-power applications. Even if a filter is required; a small sized filter is enough because of increase in ripple frequency to six times the input frequency.


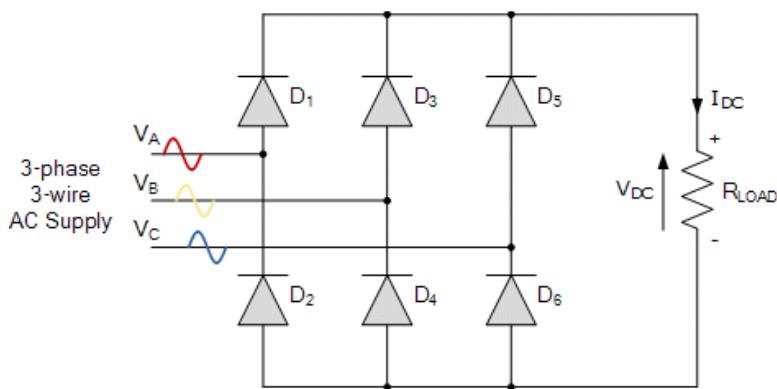


Figure 4.24 – A Three-phase Full-wave Rectifier

#### b) Controlled Rectifiers

These are similar to the uncontrolled rectifiers but the only difference is that the uncontrolled diodes are replaced by controlled thyristor family of devices such as SCRs. These are also called as phase-controlled rectifiers. Unlike diodes, thyristors can be controlled by triggering them at desired instants in order to vary the output voltage.

The block diagram of a controlled rectifier is shown in the figure that transfers the DC power to the load in a control manner by varying triggering angle of thyristors (by the control circuit) using different technologies such as a microprocessor or microcontroller-based techniques. The start of thyristor conduction varies the average value of output voltage of the converter.

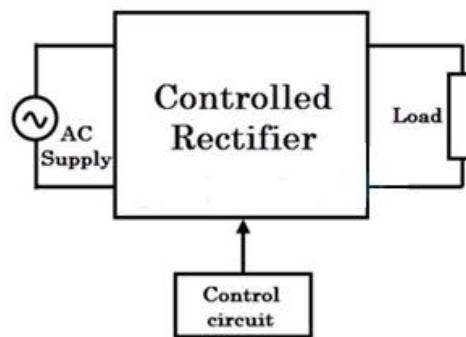

**Figure 4.25 – A Block Diagram of a Controlled Rectifier**


Similar to the uncontrolled rectifier types, these thyristor-based converters are also classified into following types:

1. Single phase half-wave rectifier
2. Single phase full-wave mid-point rectifier
3. Single phase full-wave bridge rectifier
4. Three-phase half-wave converter
5. Three-phase full-wave converter

### 1) Single Phase Half-Wave Rectifier

In this a single thyristor or SCR is connected between the secondary of the transformer and a resistive load as shown in figure. The primary of the transformer is connected to a single-phase supply and consider that load is of resistive.

During the positive half cycle of the input AC supply, thyristor T1 is forward biased, and when it is triggered at some firing angle through gate terminal, it starts conducting current to the load. Since the SCR is a unidirectional device, it turns OFF during negative half-cycle. So, the output voltage is produced only for positive half cycle. The output power delivered by this half-wave rectifier is controlled by phase control, i.e., varying firing angle to the gate terminal.

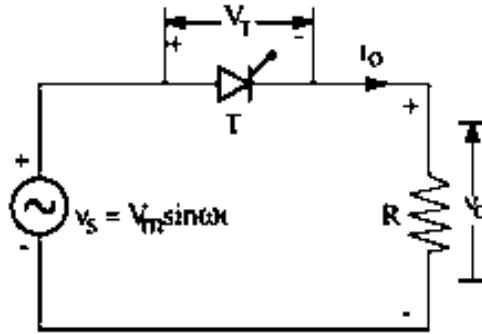

**Figure 4.26 – Half-Wave Rectifier**

## 2) Single-Phase Full-Wave Mid-Point Rectifier

This converter rectifies both positive and negative half-cycles of the input supply. It uses two SCRs with center-tapped secondary transformer as shown in figure. In positive half-cycle of the input supply, thyristor T1 is forward biased while T2 is reverse biased. When T1 is triggered, the supply voltage appears across the load. It conducts till 180 degrees of input supply and turns OFF due to natural commutation. During the negative half cycle, thyristor T2 is forward biased and when it is triggered, it starts conducting. It conducts till next positive half cycle. This type converter produces an output voltage twice that of single-phase half-wave rectifier. These are essential when one of the terminals on DC side has to be grounded. However, a center-tapped transformer with a VA rating twice that of load is required and also high voltage rating thyristors are needed in this converter.

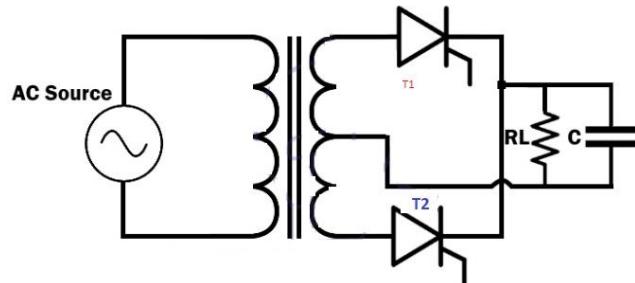


Figure 4.27 – Center-tapped Rectifier

### 3) Single-phase Full-Wave Bridge Rectifier

The circuit diagram of a full wave bridge rectifier using thyristors is shown in figure. It consists of four SCRs which are connected between single phase AC supply and a load. This rectifier produces controllable DC by varying conduction of all SCRs. In positive half-cycle of the input, thyristors T1 and T2 are forward biased while T3 and T4 are reverse biased. Thyristors T1 and T2 are triggered simultaneously at some firing angle in the positive half cycle, and T3 and T4 are triggered in the negative half cycle. The load current starts flowing through them when they are in conduction state. The load for this converter can be RL or RLE depending on the application. By varying the conduction of each thyristor in the bridge, the average output of this converter gets controlled. The average value of the output voltage is twice that of half-wave rectifier.


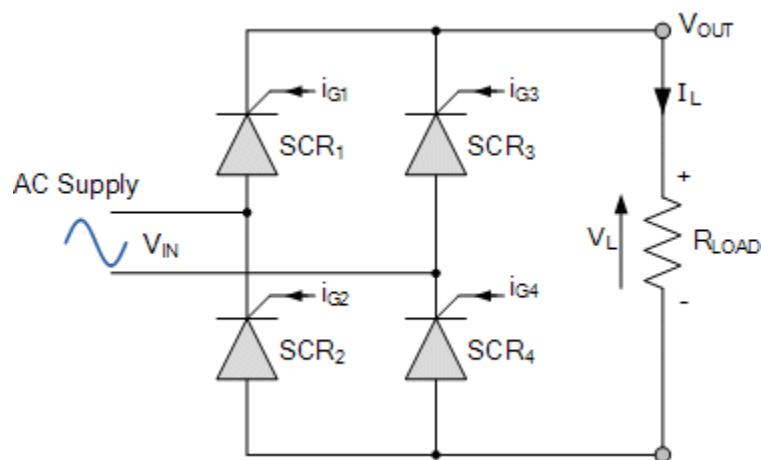


Figure 4.28 – Full-wave Bridge Rectifier

## Chapter 4

---

### 4) Three-Phase Half-Wave Converter

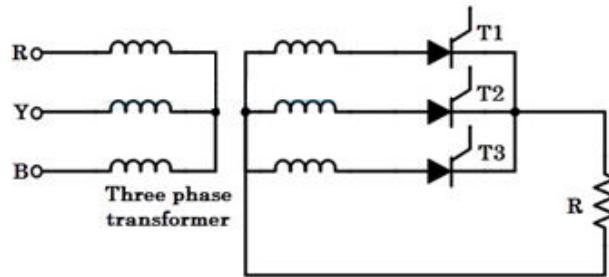


**Figure 4.29 – Three-Phase Half-Wave Rectifier**

The output from single phase converter is small; when high power is required, three phase rectifiers are used. A three-phase half-wave rectifier with thyristors is shown in figure. The three-phase supply is given to this converter through a three-phase transformer with star connected secondary. It works as similar to the three-phase diode bridge rectifier. In this, thyristor T1 is at highest positive anode voltage in the interval  $\pi/6$  to  $5\pi/6$ . During this interval, T1 can be made to conduct by giving a firing pulse to its gate. This thyristor T1 continues to conduct till thyristor T2 is made to conduct in the interval  $5\pi/6 < \omega t < 3\pi/2$ . Now the load current starts flowing through T2. Similarly, thyristor T3 is starts conducting once thyristor T2 is turned OFF. In this, there are three pulses of output voltage during each complete cycle of supply voltage. Thus, the ripple frequency is three times the supply frequency. For this reason, this converter is also called as 3-pulse converter

### 5) Three-Phase Full-Wave Converter

It is obtained by connecting a DC terminal of two three-pulse converters in series. It is also called as 6-pulse bridge converter. This type converter is used in industrial applications where two-quadrant operation is required. Here the load is connected via a three-phase half wave connection to one of three supply lines. Thus, there is no need of transformer; however, for isolation purpose a transformer is connected as shown in figure. Here thyristors T1, T3 and T5 forms a positive group, whereas thyristors T4, T6 and T2 forms a negative group. And thus, positive group SCRs are turned ON for positive supply voltage and negative group thyristors are turned ON for negative supply voltages. In this, one of the thyristors from positive, whose anode voltage is maximum positive will conduct at any instant and simultaneously one of the thyristors from negative group, whose cathode voltage is maximum negative will conduct.

By controlling the firing angle to respective thyristor, average power delivered to the load is changed. The firing angle of particular thyristor in positive group measured from the instant when its anode becomes maximum positive. Similarly, the firing angle for a thyristor in negative group is measured from the instant when its cathode terminal attains a maximum negative value.

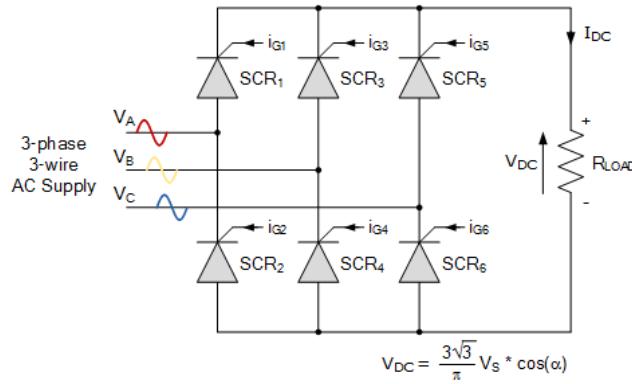


**Figure 4.30 – Three-Phase Full-Wave Rectifier**

#### 4.8 DC to DC Converters

Many DC operated applications need different levels of DC voltage from a fixed DC source. Some of these applications include subway cars, DC traction systems, control of large DC motors, battery operated vehicles, trolley buses, ship propulsion system, etc. They require variable DC to produce variable speed, so a power conversion device is needed.

A DC chopper is a static device that converts a fixed input DC voltage to variable DC output or a fixed DC output of different magnitude (which can be lower or higher) than input value. The block diagram of a DC chopper is shown in the following figure.

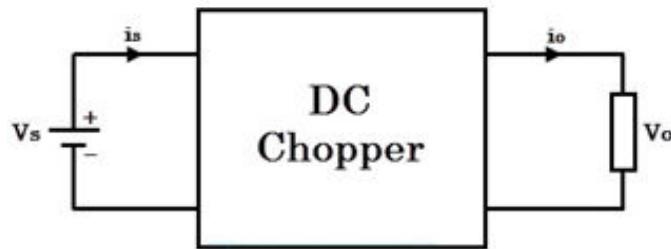

**Figure 4.31 – DC-DC Converter**

## Chapter 4


---

The chopper circuit is connected between DC input source and DC load. This chopper consists of power electronic switching devices such as thyristors which are connected in such a way that they produce required DC voltage to the load.

The output voltage is controlled by adjusting ON time of the thyristor (or switch) which turns changes the width of DC voltage pulse at the output. This method of switching is called as pulse width modulation (PWM) control. The output of the chopper can be less or greater than the input and also it can be fixed or variable. These can be unidirectional or bidirectional devices based on the application it is intended for. DC choppers are mainly used in DC drives, i.e., electric vehicles and hybrid electric vehicles. DC choppers are classified into three basic types based on input and output voltage levels and are discussed below.

### a) Step-down Chopper or Buck converter

A step-down chopper produces an average output voltage lower than the input DC voltage. The circuit for this converter is shown in figure. Here the switching component is a thyristor that switches the input voltage to the load when it is triggered at particular instants.

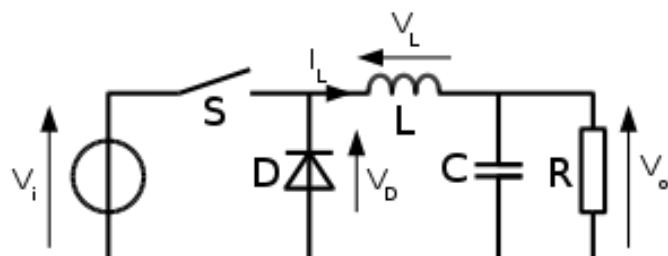


**Figure 4.32 – A Buck Converter**

A diode acts as a free-wheeling diode that allows the load current to flow through it when thyristor is turned OFF. If this diode is absent, a high induced EMF in inductance may cause damage to the switching device. The average output voltage of the converter is varied by controlling turn ON/OFF periods of thyristor. When thyristor is turned ON, the output voltage is same as the input voltage and if it is turned OFF, the output voltage is zero. The output voltage is equal to  $(TON / T) V_{in}$ . So, by controlling the duty ratio  $K = (TON / T)$ , the output voltage will be increased.

**b) The Step-up Chopper or Boost Converter**

In this chopper, the output voltage is always greater than input voltage. The configuration of a boost converter is shown in figure. Here also a switch is used, which is connected in parallel with the load. This switch is a thyristor or an SCR.

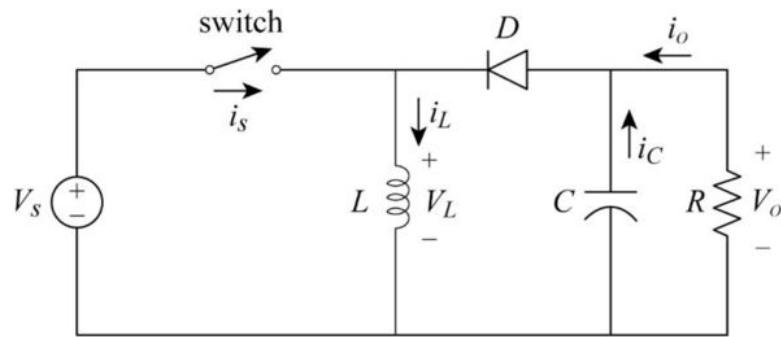


**Figure 4.33 – A Boost Converter**

Similar to the buck converter, a diode is placed in series with the load that allows the load current to flow when the thyristor is turned OFF. When the thyristor is turned ON, the diode is reverse-biased and hence it isolates the load circuit from the source. So the inductor charges to the maximum input voltage source. When the thyristor is turned OFF, the load gets the voltage from input as well as from inductor. So the voltage appearing across the converter output will be more than the input. Here the output voltage is equal to  $(1/1 - d)$  times the input voltage, where  $d$  is the duty ratio ( $TON / T$ ). By varying this duty ratio, the output voltage will be varied till the load gets desired voltage.

**c) Buck / Boost Converter**

This chopper can be used both in step-down and step-up modes by continuously adjusting its duty cycle. The configuration of buck-boost converter is shown in figure that consists of only one switching device, i.e., one thyristor. Along with an inductor and diode, additional capacitor is connected in parallel with this circuit.

## Chapter 4

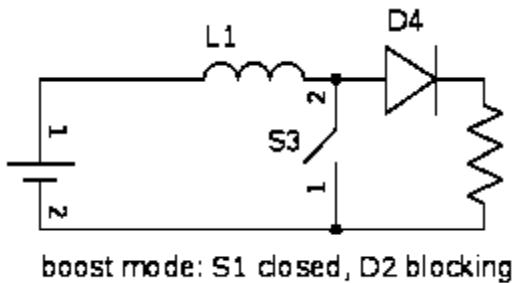

**Figure 4.34 – A Buck / Boost Converter**


When the thyristor is turned ON, the supply current flows to the inductor through the thyristor and induces the voltage in inductor. When the thyristor is OFF, the current in the inductor tends to decrease with the induced emf reversing polarity. The output voltage of this converter remains constant as capacitor is connected across the load. By varying the value of duty ratio to a certain value, the output voltage is lower than the input voltage, typically in the range  $0 \geq k > 0.5$ , thus a buck converter. And the output is higher than the input voltage if the duty ratio is in the range of  $0.5 > K \geq 1$ , thus acts as a boost converter.

### 4.9 AC to AC Converters

AC/AC converters connect an AC source to AC loads by controlling amount of power supplied to the load. This converter converts the AC voltage at one level to the other by varying its magnitude as well as frequency of the supply voltage. These are used in different types of applications including uninterrupted power supplies, high power AC-to-AC transmission, adjustable speed drives, renewable energy conversion systems and aircraft and ship converter systems and marine propulsion system. The types of AC-to-AC converters are discussed below.

#### 4.9.1 AC / AC Voltage Converters


These converters control the rms value of output voltage at a constant frequency. The common application of these converters includes starting of AC motors and controlling power to heaters. A single-phase AC/AC voltage converter consists of a pair of anti-parallel thyristors along with a control circuit as shown in figure. The other names of this controller are single phase full wave converter and AC voltage controller.

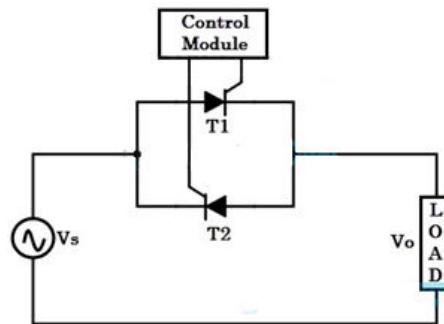

**Figure 4.35 – Triac-Based Voltage Controller**

During positive half cycle of the input signal, thyristor-1 is forward biased and it starts conducting, when the triggering is applied. Thus, the power flows from source to load. In negative half cycle of the input, thyristor-2 is forward biased and starts conducting when it is triggered, while thyristor-1 is turned OFF by natural commutation. By varying the triggering or conduction angle of each thyristor during each half-cycle, the magnitude of voltage appeared across the load is controlled. The other popular form of AC voltage controller is the use of TRIAC in place of two anti-parallel thyristors.

The figure below shows TRIAC-based AC controller along with triggering control circuit. Here diac controls the positive and negative triggering to the TRIAC so that average output voltage to the load is controlled.

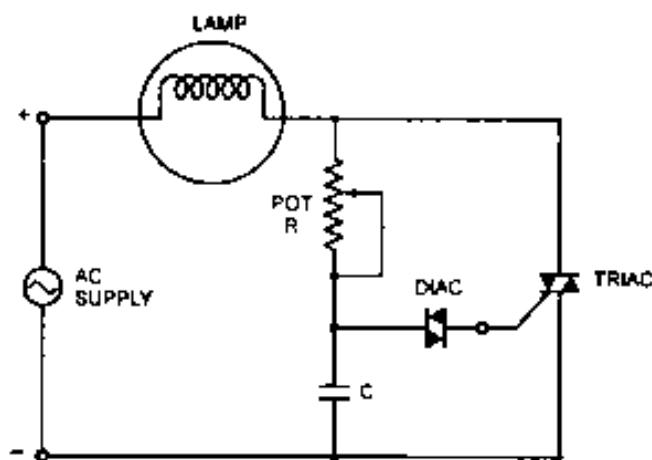

**Figure 4.36 – AC/AC Voltage Converter**

## Chapter 4

---

### 4.9.3 AC/AC Frequency Converters

These converters are mainly used for varying the frequency of the input source to desired level of the load. An AC/AC frequency converter changes the frequency of input voltage/current of the load compared to the frequency of the source. Some of these converters may control magnitude of voltage besides the frequency control. These are mainly used for adjusting the speed of AC drives and also for induction heating. The two major classes of these converters include

- a) Cyclo converters
- b) Matrix converters.

#### a) Cyclo-converter



**Figure 4.37 – A Block Diagram of a Cyclo-converter**

Basically, cyclo-converters are AC to AC converters and are used to vary the frequency of a supply to a desired load frequency. These are naturally commutated, direct frequency converters that use naturally commutated thyristors. These are mainly used in high power applications up to tens of megawatts for frequency reduction. Some of the applications of cyclo-converter include high power AC drives, propulsion systems, high frequency induction heating, synchronous motors in sea and undersea vehicles, electromagnetic launchers, etc. The cyclo-converter is a device that converts AC power of certain frequency to AC power of another frequency (usually lower frequency). It converts the frequency without help of any intermediate DC link.

The output voltage and frequency of a cyclo-converter can be varied continuously and independently using a control circuit. Therefore, unlike other converters, it is a single stage frequency converter. Cyclo-converters are constructed using naturally commutated thyristors with inherent capability of bidirectional power flow. These can be single phase to single phase, single phase to three- phase and three-phase to three phase converters.

So, the control circuit implementation is not simple because large number of SCRs, typically 4 or 8 SCRs for single phase and 36 for three- phase supply. For such controller, a microcontroller or microprocessor or DSP is used to trigger SCRs. Basically, these are divided into two main types, and are given below.

**Step-down Cyclo-converter:** It acts like a step-down transformer that provides the output frequency less than that of input,  $f_o < f_i$ .

**Step-up Cyclo-converter:** It provides the output frequency more than that of input,  $f_o > f_i$ .

In case of step-down cyclo-converter, the output frequency is limited to a fraction of input frequency, typically it is below 20Hz in case 50Hz supply frequency. In this case, no separate commutation circuits are needed as SCRs are line commutated devices.

But in case of step-up cyclo-converter, forced commutation circuits are needed to turn OFF SCRs at desired frequency. Such circuits are relatively very complex. Therefore, majority of cyclo-converters are of step-down type that lowers the frequency than input frequency.

Step-down cyclo-converter circuits can be further classified into following types.

- Single-phase to single-phase cyclo-converters
- Three-phase to single-phase cyclo-converters
- Three-phase to three-phase cyclo-converters

Besides the frequency control, cyclo-converter output voltage can be varied by applying phase control technique. These can be used to provide either fixed frequency output from variable frequency input value or variable frequency output from fixed frequency input. These are mainly used in very high power, low speed AC motors and traction systems, especially low frequency three-phase to single phase systems.

## Chapter 4

### 4.9.3.1 Basic Principle of Operation of Cyclo-converter


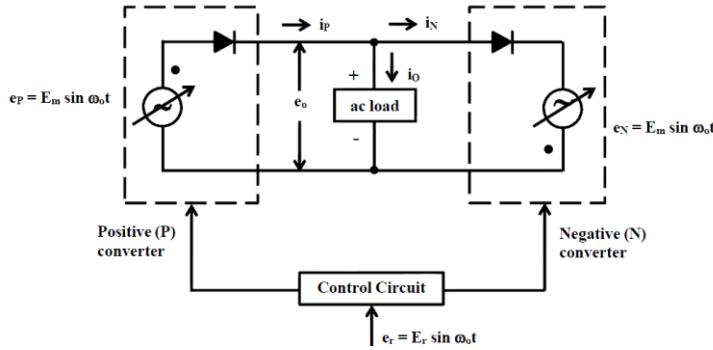


Figure 4.38 – An Equivalent Circuit of a Cyclo-converter

The equivalent circuit of a cyclo-converter is shown in figure. Here each two quadrant phase controlled converter is represented by a voltage source of desired frequency and consider that the output power is generated by the alternating current and voltage at desired frequency. The diodes connected in series with each voltage source represent the unidirectional conduction of each two-quadrant converter.

If the output voltage ripples of each converter are neglected, then it becomes ideal and represents the desired output voltage. If the firing angles of individual converters are modulated continuously, each converter produces same sinusoidal voltages at its output terminals. So the voltages produced by these two converters have same phase, voltage and frequency. The average power produced by the cyclo-converter can flow either to or from the output terminals as the load current can flow freely to and from the load through the positive and negative converters. Therefore, it is possible to operate the loads of any phase angle (or power factor), inductive or capacitive through the cyclo-converter circuit. Due to the unidirectional property of load current for each converter, it is obvious that positive converter carries positive half-cycle of load current with negative converter remaining in idle during this period. Similarly, negative converter carries negative half cycle of the load current with positive converter remaining in idle during this period, regardless of the phase of current with respect to voltage. This means that each converter operates both in rectifying and inverting regions during the period of its associated half cycles. The figure shows ideal output current and voltage waveforms of a cyclo-converter for lagging and leading power factor loads. The conduction periods of positive and negative converters are also illustrated in the figure.

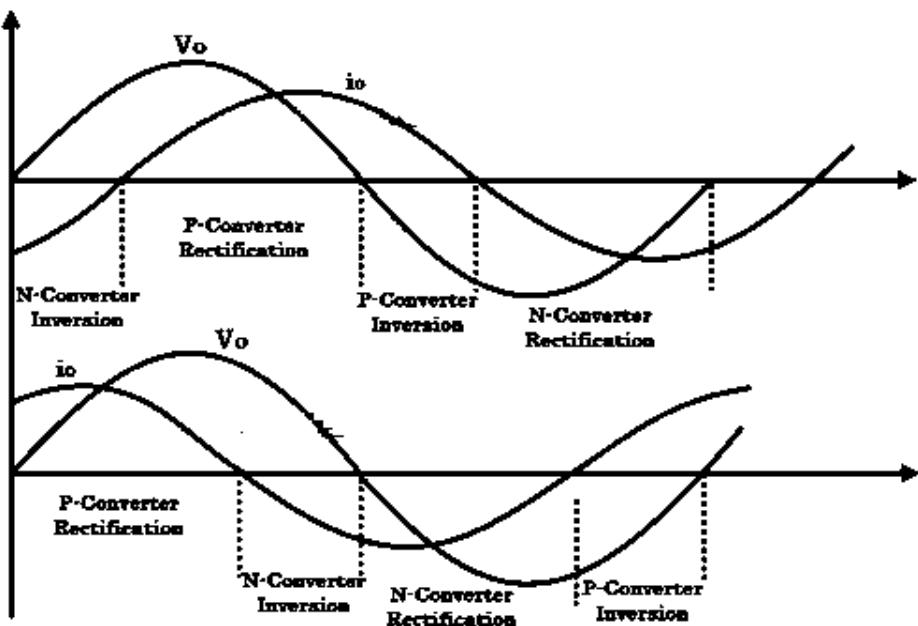

**Figure 4.39 – Ideal Output Current and Voltage Waveforms of a Cyclo-Converter**


The positive converter operates whenever the load current is positive with negative converter remaining in idle. In the same manner negative converter operates for negative half cycle of load current. Both rectification and inversion modes of each converter are shown in figure. This desired output voltage is produced by regulating the firing angle to individual converters.

#### 4.9.3.2 Single-Phase to Single-Phase Cyclo-Converters

It consists of two full-wave, fully controlled bridge thyristors, where each bridge has 4 thyristors, and each bridge is connected in opposite direction (back to back) such that both positive and negative voltages can be obtained as shown in figure below. Both these bridges are excited by single phase, 50 Hz AC supply. During positive half cycle of the input voltage, positive converter (bridge-1) is turned ON and it supplies the load current. During negative half cycle of the input, negative bridge is turned ON and it supplies load current. Both converters should not conduct together that cause short circuit at the input. To avoid this, triggering to thyristors of bridge-2 is inhibited during positive half cycle of load current, while triggering is applied to the thyristors of bridge-1 at their gates. During negative half cycle of load current, triggering to positive bridge is inhibited while applying triggering to negative bridge.

## Chapter 4

By controlling the switching period of thyristors, time periods of both positive and negative half cycles are changed and hence the frequency. This frequency of fundamental output voltage can be easily reduced in steps, i.e., 1/2, 1/3, 1/4 and so on.

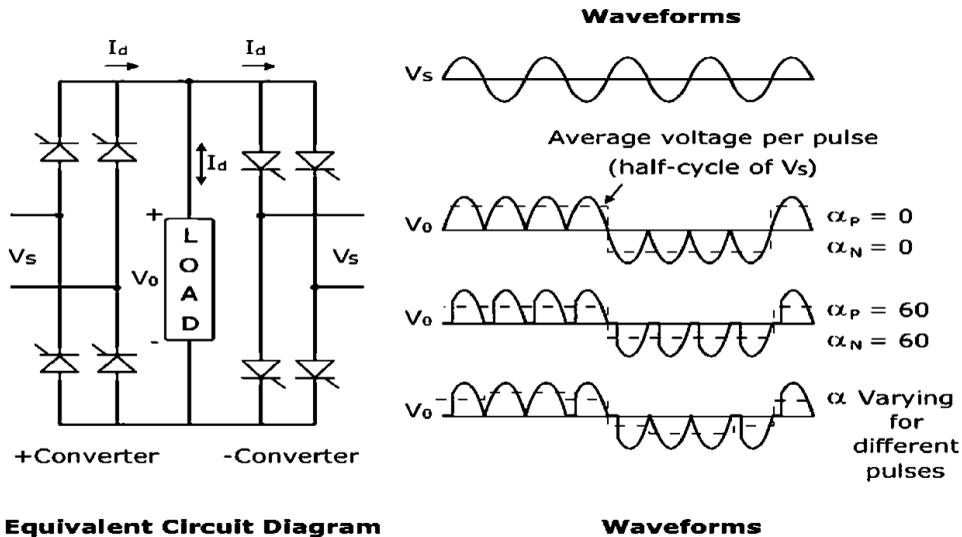


**Fig. 4.40 Cyclo Converter Equivalent Circuit Diagram and Waveforms**

The figure above shows output waveforms of a cyclo-converter that produces one-fourth of the input frequency. Here, for the first two cycles, the positive converter operates and supplies current to the load. It rectifies the input voltage and produce unidirectional output voltage as we can observe four positive half cycles in the figure. And during next two cycles, the negative converter operates and supplies load current. Here current waveforms are not shown because it is a resistive load in where current (with less magnitude) exactly follows the voltage.

Here one converter is disabled if another one operates, so there is no circulating current between two converters. Since the discontinuous mode of control scheme is complicated, most cyclo-converters are operating on circulating current mode where continuous current is allowed to flow between the converters with a reactor. This circulating current type cyclo-converter can be operated on with both purely resistive (R) and inductive (R-L) loads.

### 4.9.3.3 Three-Phase to Single-Phase Cyclo-Converters

Similar to the above cyclo-converter, a three-phase to single phase cyclo converter also consists of positive and negative group thyristors. These cyclo-converters can be half-wave or full bridge converters as shown in figure. Like single phase cyclo-converters, these also produce a rectified voltage at the load terminals by each group of thyristors.

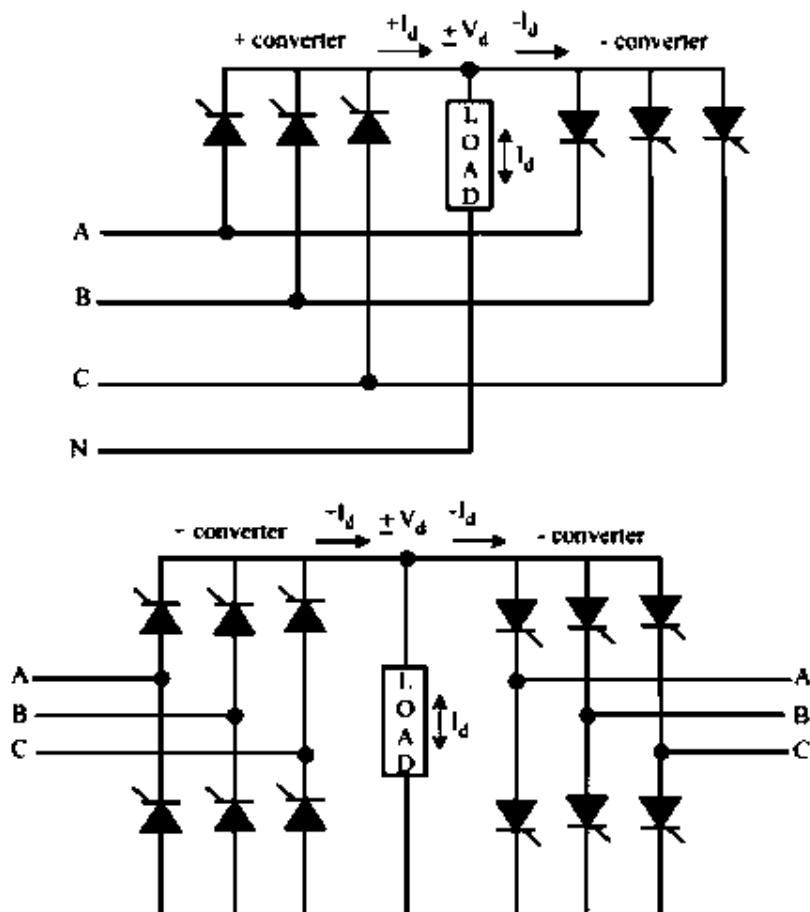

**Figure 4.41 – Three-Phase to Single-Phase Cyclo-Converter**


During the positive half cycle of the input, conduction of the positive group thyristors is controlled and during negative half-cycle, conduction of negative group of thyristors is controlled in order to produce an output voltage at desired frequency.

In a bridge type of cyclo-converter, both positive and negative converters can generate voltages at either polarity, but negative converter only supplies negative current while positive converter supply positive current.

Therefore, the cyclo-converter can operate in four quadrants, i.e., rectification modes of  $(+V, +i)$  and  $(-V, -i)$  and inversion modes of  $(+V, -i)$  and  $(-V, +i)$ .

## Chapter 4


The following figure shows the conversion of three phase supply at one frequency to single phase supply of lower frequency. In this, the firing angle to a positive group of thyristors is varied progressively to produce single phase output voltage. At point M, the firing angle is 90 degrees and it is reduced till point S where it is zero. Again from point T to Y, the delay angle is progressively increased. This varied triggering signals to the thyristors, varies its conduction time periods and hence the frequency of the output voltage.

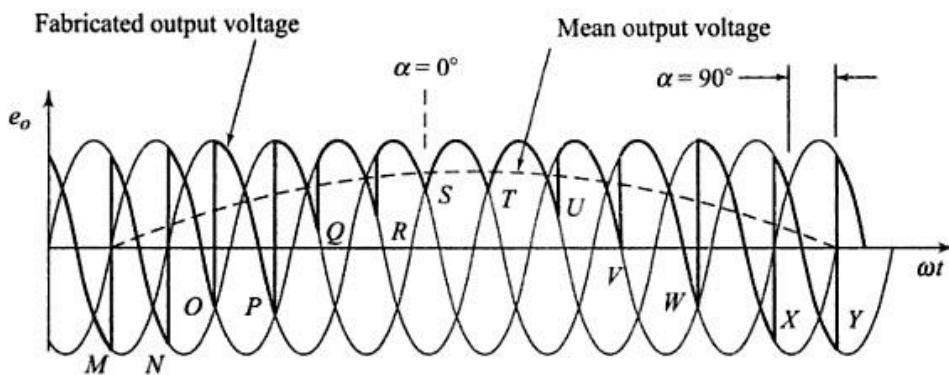

**Figure 4.42 – Conversion of Three Phase Supply at One Frequency To Single Phase Supply of a Lower Frequency**


These are obtained by connecting 3 three-phase to single-phase cyclo-converters to the load. These converters can be connected in star or delta. Three phase cyclo-converter of both half-wave and bridge types are shown in figure below. Three-phase to three-phase cyclo-converter is also called as 18-thyristor cyclo-converter or 3-pulse cyclo-converter and three-phase to three-phase bridge type cyclo-converter is called as 6-pulse cyclo-converter or 36-thyristor cyclo-converter.

This converter consists of six groups of converter circuits where three groups are called as positive group while other three are negative group. During each positive half cycle, positive group carries the current and during negative half cycle, negative group carries the current. The duration for conduction of each group of thyristor determines the desired output frequency. Here, the average value of output voltage is varied by varying the firing or delay angle of SCRs conduction whereas the output frequency can be varied by changing the sequence of firing the SCRs. The neutral connection is no longer necessary with a balanced load and hence this connection can be omitted.

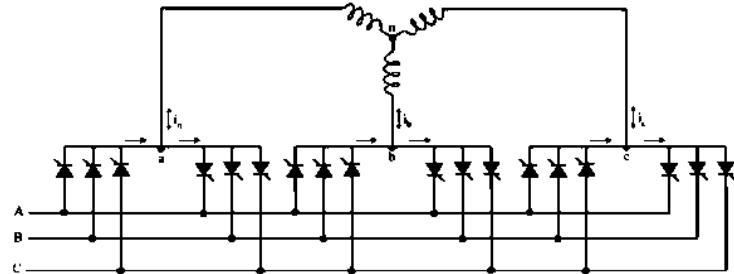

**Figure 4.43 – Three-phase Cyclo-converter with Six Groups of Converter Circuits**

Three-phase cyclo converters are more popular than single-phase type as these can handle very large currents and produce smooth output waveform. It is a highly efficient variable frequency drive, because the pulse number is increased due to the large number of thyristors, which causes small ripple content in the output voltage waveform.

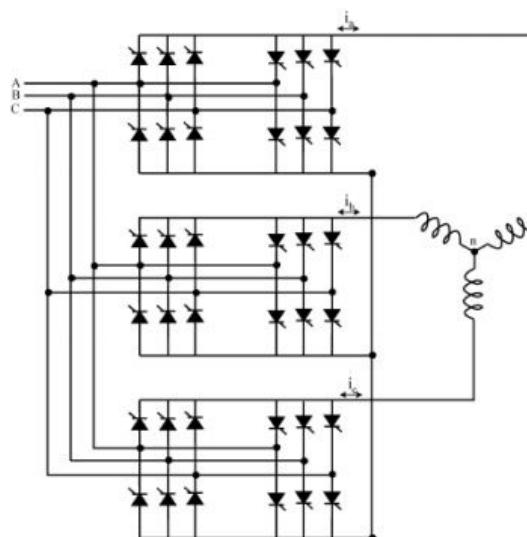

**Figure 4.44 – Three-phase Cyclo-converter with a Star-connected Load**

## **Chapter 4**

---

### **4.9.3.4 Applications of Cyclo-converters**

Cyclo-converters are mainly used for producing low frequency AC voltage. The main application of such requirement is the electric traction system where low frequencies, typically 25 Hz or  $16\frac{2}{3}$  Hz are preferred. In such systems, three-phase squirrel cage induction motor is controlled by a suitable cyclo-converter circuit. Other applications of Cyclo-converter include

- HVDC transmission systems
- Static Var Generation
- Aircraft or shipboard power supplies
- Speed control of high-power AC drives
- Grinding mills
- Cement mill drives
- Electrical Propulsion Syems for ships


### **b) Matrix Converter**

Since the cyclo-converters satisfactorily work only for a certain range of frequencies, matrix converters are invented that has unrestricted frequency conversion capability. These are constructed using full-controlled static devices, mostly uses bidirectional switches. With the use of these switches in three-phase matrix converters, any phase of the load can be connected to any phase of the input supply. By using pulse width modulation techniques, the load frequency and voltages are controlled from zero value to their maximum values.

## **4.10 DC to AC Converters or Inverters**

These converters are connected between DC source of fixed input, and variable AC load. Most commonly, these DC to AC converters are called as inverters.

An inverter is a static device that converts fixed DC supply voltage to variable AC voltage

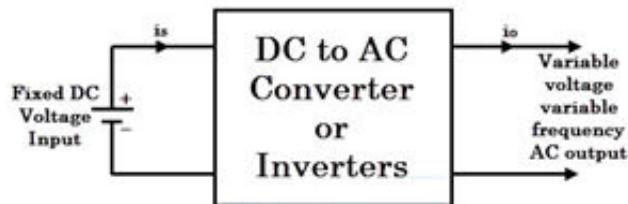

**Figure 4.45 – A Basic Inverter Diagram**

Here the fixed DC voltage is obtained from batteries or by DC link in most power electronic converter. The output of the inverter can be variable/ fixed AC voltage with variable/fixed frequency. This conversion from DC to AC along with variable supply is produced by varying the triggering angle to the thyristors. Most of the thyristors used in inverters are employed with forced commutation technique. These can be single phase or three phase inverter depending on the supply voltage. These converters are mainly divided into two groups. One is PWM based inverters and other multilevel inverters. Further, these are classified voltage source inverter and current source inverter. Each type is subdivided into different types such as PWM, SVPWM, etc. Multilevel inverters are more popular in industrial applications. The inverters overcome the drawbacks of PWM based inverters.

#### 4.11 Multi String Inverters (MSI)

String inverters are a tried-and-true inverter technology, and one of the oldest options available in the market today. It is normally used in solar power system (PV system). A string inverter system aggregates the power output of groups of solar panels in your system into “strings”.

Multiple strings of panels then connect to a single inverter where electricity is converted from DC to AC electricity. Because panels are connected in strings to the inverter, if one or more panels is underproducing energy (due to shading, dirt, or some other factor), the output of the rest of the panels on that string will be reduced.

A string inverter is typically capable of handling multiple strings of panels attached to it. For example, if there are three strings of five panels each, for a total of fifteen panels on a single string. The size of the string inverter in kilowatts (kW) and the wattage of the solar panels there used will determine how many panels can string to one inverter without wasting energy.

## Chapter 4

---

String inverters are an effective, affordable solution for many solar installations. The solar panel systems that are best suited for string inverters have little to no shading, and panels that are on fewer than three separate roof planes.

In these scenarios, normally there is no problem about any reduced output on an individual string due to shading, while the ability to connect multiple strings to the same central inverter affords some flexibility in the direction the different strings of panels are facing.

String inverters may not be right for every solar panel installation; similarly, it's not always worth it to pay a premium for power optimizers or microinverters. String inverters are a proven, durable and affordable technology that are worth considering during your solar shopping journey. Just like solar panels, string inverters have varying efficiencies. An inverter's efficiency is a measure of how much energy is lost in the form of heat during the conversion from DC to AC electricity. Higher efficiency string inverters lead to higher overall system efficiencies and more solar electricity production.


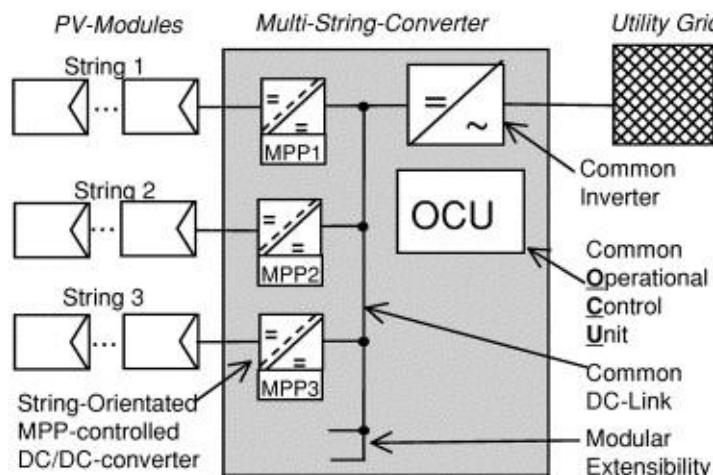


Figure 4.46 – Multi String Inverters

#### 4.12 Linear Regulated Power Supply (Analog Power Supply)

In a linear power supply, the mains AC voltage is converted to a lower voltage directly by a step-down transformer. This transformer has to handle a large power since it works at the AC mains frequency 50/60Hz. Therefore, this transformer is bulky and large, making the power supply heavy and large. Stepped-down voltage is then rectified and filtered to get the DC voltage required for the output. Since the voltage at this level is subjected to vary depending on the distortions of the input voltage, a voltage regulation is done before the output. The voltage regulator in a linear power supply is a linear regulator, which is usually a semiconductor device that acts as a variable resistor. The output resistance value changes with the output power requirement, making the output voltage constant. Thus, the voltage regulator operates as a power dissipating device. Most of the time, it dissipates excess power to make the voltage constant. Therefore, the voltage regulator should have large heat sinks. As a result, the linear power supplies become much heavier. Furthermore, as a result of power dissipation by the voltage regulator as heat, the efficiency of a linear power supply drops as much as about 60%.

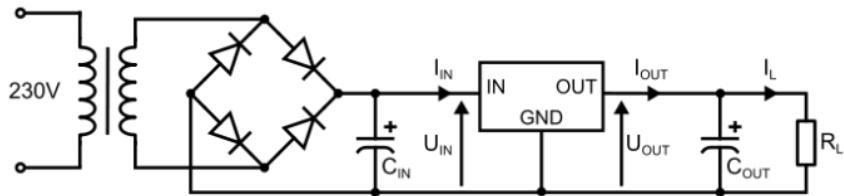

**Figure 4.47 – Linear Regulated Power Supply**

However, linear power supplies do not produce electrical noise on the output voltage. It provides isolation between the output and input because of the transformer. Therefore, linear power supplies are used for high-frequency applications such as radio frequency devices, audio applications, laboratory tests which require noise-free supply, signal processing, and amplifiers.


#### 4.13 Switched Mode Power-supply (SMPS) - Impulse Power Supply

SMPS (switched-mode power supply) operates on a switching transistor device. At first, the AC input is converted to DC voltage by a rectifier, without reducing the voltage, unlike in a linear power supply. Then the DC voltage undergoes a high-frequency switching, typically by a MOSFET transistor. That is, the voltage through the MOSFET is turned on and off by MOSFET Gate signal, usually a pulse-width-modulated signal of about 50 kHz (chopper/inverter block).

## Chapter 4

---

After the chopping operation, the waveform becomes a pulsated-DC signal. After that, a step-down transformer is used to reduce the voltage of the high-frequency pulsated DC signal to the desired level. Finally, an output rectifier and a filter are used to make back the output DC voltage.

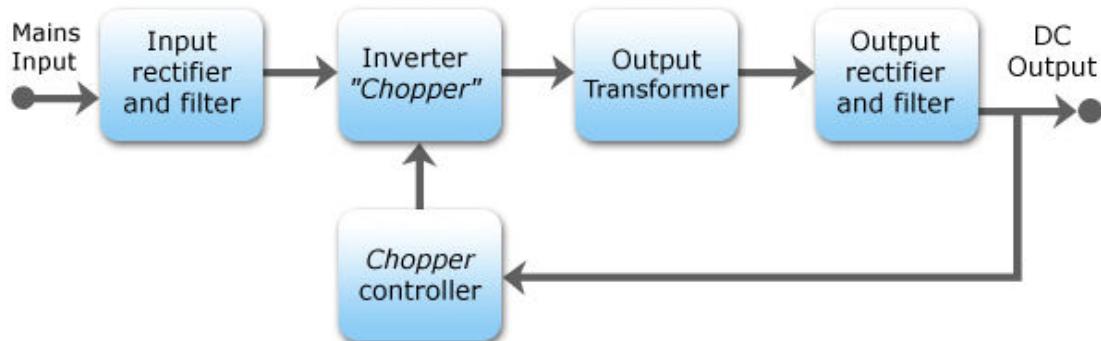


**Figure 4.48 – Switched Mode Power Supply (SMPS)**

The voltage regulation in SMPS is done via a feedback circuit that monitors the output voltage. If the power requirement of the load is high, the output voltage tends to increase. This increment is detected by the regulator feedback circuit and is used to control the on-to-off ratio of the PWM signal. Thus, the average signal voltage changes. As a result, the output voltage is controlled to keep constant. The step-down transformer used in the SMPS operates at a high-frequency; thus, the volume and weight of the transformer are much less than those of a linear power supply. This becomes a major reason for an SMPS to be much smaller and lighter than its linear type counterpart. Moreover, the voltage regulation is done without dissipating excess power as ohmic-loss or heat.

The efficiency of the SMPS gets as high as 85-90%. At the same time, an SMPS generates high-frequency noise due to the switching operation of the MOSFET. This noise can be reflected in the output voltage; however, in some advanced and expensive models, this output noise is mitigated to some extent. Furthermore, the switching creates electromagnetic and radio frequency interference as well. Hence, it is required to use RF shielding and EMI filters in SMPSs. Therefore, SMPS are not suitable audio and radio frequency applications. Less noise-sensitive equipment such as mobile phone chargers, DC motors, high power applications, etc. can be used with SMPSs. Its lighter and smaller design makes it convenient to be used as portable devices as well.

#### 4.14 The Snubber Circuit

The Snubber circuit is one type of  $dv/dt$  protection circuit of the thyristor. With the help of snubber circuit, the false turn-on of a thyristor due to large  $dv/dt$  can be prevented.

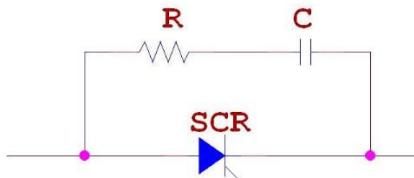

**Figure 4.49 – A Snubber Circuit**

##### 4.14.1 RC Snubber Circuit for SCR $dv/dt$ Protection

This type of snubber circuit consists of a series combination of resistance R and Capacitance C in parallel with a SCR.

- When a reverse voltage is applied, commutation process is initiated and the forward current flow through SCR approaches zero.
- Due to the inductance, current continues to flow due to sweeping of charge carriers at the external junctions.
- When it reaches a peak value, it cannot be further supported by the charge carriers and falls very quickly to zero. This causes a voltage spike with the value of  $L(di/dt)$ .
- Also, when the supply is closed to the circuit (in the above figure say the switch S is closed), sudden voltage appears across SCR.
- Now, as the thyristor current is zero it can be considered as an open switch.
- At this moment, the capacitor C behaves like a short-circuit and therefore voltage across the SCR is zero.
- With the passage of time capacitor C gets charged at a slow rate such that  $dv/dt$  across the capacitor and therefore across SCR is less than the specified maximum  $dv/dt$  rating of the device.
- Thus, the capacitor protects the SCR against high voltages and high  $dv/dt$ .

Based on the above discussion we can say that simply a Capacitor C is sufficient to protect the SCR against  $dv/dt$  false triggering.

## Chapter 4

---

### 4.14.2 Purpose of Resistance R

- In the RC snubber circuit, the resistance R limits the discharge current of capacitor at the instant of firing of SCR.
- Before SCR is fired, capacitor C charges to full voltage V.
- If SCR is fired, when the capacitor voltage is maximum, it discharges through the local path formed by capacitor C, Resistance R and SCR.
- During this time, if the resistance R is not included in the circuit, the discharge current will be high and consequently may damage the SCR due to large  $di/dt$ .
- Thus, the Resistance R in the snubber circuit reduces the discharge current of the capacitor C and thus protect the SCR against large  $di/dt$ .

In actual practice, R, C and the load current parameters should be such that

- $dv/dt$  across C during its charging is less than the specified  $dv/dt$  rating of the SCR

Discharge current at the turn ON of the SCR is within reasonable limits.

Normally R, S and load circuit parameters form an undamped circuit so that  $dv/dt$  is limited to acceptable values.

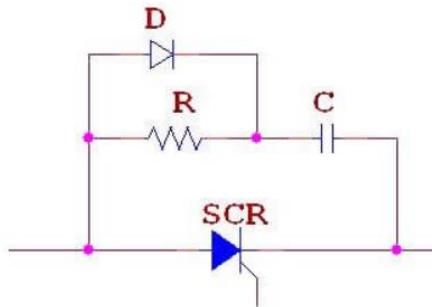


Figure 4.50 – An R-C Snubber Circuit


In some RC snubber circuits, a diode D used to connect in parallel with the resistor R. It is used for the purpose of bypass and thus giving improved  $dv/dt$  protection.

**4.15 The Operational Amplifier (Op-amp)**



**Figure 4.51 – An Op-amp IC**

An operational amplifier (often op amp or op-amp) is a DC-coupled high-gain electronic voltage amplifier with a differential input and, usually, a single-ended output. In this configuration, an op amp produces an output potential (relative to circuit ground) that is typically 100,000 times larger than the potential difference between its input terminals. Operational amplifiers had their origins in analog computers, where they were used to perform mathematical operations in linear, non-linear, and frequency-dependent circuits. An op-amp is fundamentally a voltage amplifying device designed to be used with external feedback components such as resistors and capacitors between its output and input terminals. These feedback components determine the resulting function or “operation” of the amplifier and by virtue of the different feedback configurations whether resistive, capacitive or both, the amplifier can perform a variety of different operations, giving rise to its name of “Operational Amplifier”.

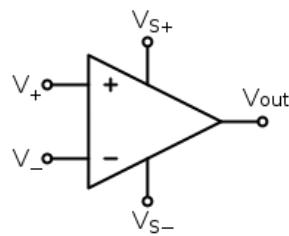

**Figure 4.52 – An Op-amp IC’s Circuit Symbol**

## **Chapter 4**

---

An Operational Amplifier is basically a three-terminal device which consists of two high impedance inputs. One of the inputs is called the Inverting Input, marked with a negative or “-” sign. The other input is called the Non-inverting Input, marked with a positive or “+” sign. A third terminal represents the operational amplifiers output port which can both sink and source either a voltage or a current. In a linear operational amplifier, the output signal is the amplification factor, known as the amplifiers gain (A) multiplied by the value of the input signal and depending on the nature of these input and output signals, there can be four different classifications of operational amplifier gain.

- Voltage – Voltage “in” and Voltage “out”
- Current – Current “in” and Current “out”
- Transconductance – Voltage “in” and Current “out”
- Transresistance – Current “in” and Voltage “out”

The amplifier's differential inputs consist of a non-inverting input (+) with voltage  $V_+$  and an inverting input (-) with voltage  $V_-$ ; ideally the op amp amplifies only the difference in voltage between the two, which is called the differential input voltage. The output voltage of the op amp  $V_{out}$  is given by the equation

$$V_{out} = A_{OL} (V_+ - V_-)$$


Where  $A_{OL}$  is the open-loop gain of the amplifier (the term “open-loop” refers to the absence of an external feedback loop from the output to the input).

#### 4.15.1 Op-amp Characteristics

##### 4.15.1.1 Ideal Op Amps

An ideal op amp is usually considered to have the following characteristics:

- Infinite open-loop gain  $G = v_{\text{out}} / v_{\text{in}}$

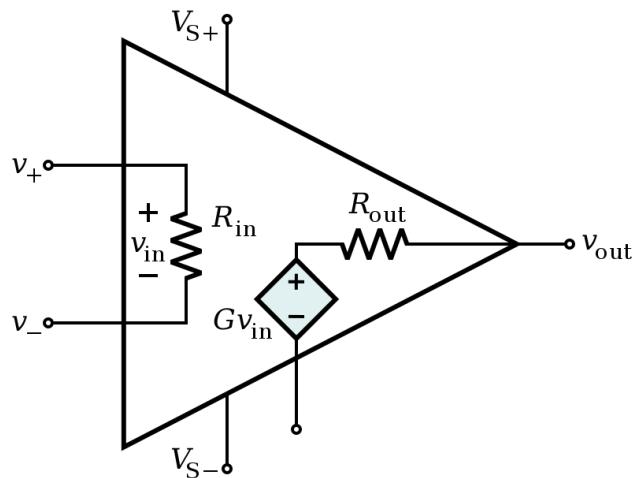

**Figure 4.53 – An Op-amp's Equivalent Circuit**

- Infinite input impedance  $R_{\text{in}}$ , and so zero input current
- Zero input offset voltage
- Infinite output voltage range
- Infinite bandwidth with zero phase shift and infinite slew rate
- Zero output impedance  $R_{\text{out}}$
- Zero noise
- Infinite common-mode rejection ratio (CMRR)
- Infinite power supply rejection ratio.

## **Chapter 4**

---

These ideals can be summarized by the two “golden rules”:

- In a closed loop the output attempts to do whatever is necessary to make the voltage difference between the inputs zero.
- The inputs draw no current.

### **4.15.1.2 Real Op Amps**

Real operational amplifiers suffer from several non-ideal effects:

#### **1. Finite Gain**

Open-loop gain is infinite in the ideal operational amplifier but finite in real operational amplifiers. Typical devices exhibit open-loop DC gain ranging from 100,000 to over 1 million. So long as the loop gain (i.e., the product of open-loop and feedback gains) is very large, the circuit gain will be determined entirely by the amount of negative feedback (i.e., it will be independent of open-loop gain). In cases where closed-loop gain must be very high, the feedback gain will be very low, and the low feedback gain causes low loop gain; in these cases, the operational amplifier will cease to behave ideally.

#### **2. Finite Input Impedances**

The differential input impedance of the operational amplifier is defined as the impedance between its two inputs; the common-mode input impedance is the impedance from each input to ground. MOSFET-input operational amplifiers often have protection circuits that effectively short circuit any input differences greater than a small threshold, so the input impedance can appear to be very low in some tests. However, as long as these operational amplifiers are used in a typical high-gain negative feedback application, these protection circuits will be inactive. The input bias and leakage currents described below are a more important design parameter for typical operational amplifier applications.

#### **3. Non-zero Output Impedance**

Low output impedance is important for low-impedance loads; for these loads, the voltage drop across the output impedance effectively reduces the open loop gain. In configurations with a voltage-sensing negative feedback, the output impedance of the amplifier is effectively lowered; thus, in linear applications, op-amp circuits usually exhibit a very low output impedance. Low-impedance outputs typically require high quiescent (i.e., idle) current in the output stage and will dissipate more power, so low-power designs may purposely sacrifice low output impedance.

#### **4. Input Current**

Due to biasing requirements or leakage, a small amount of current (typically  $\sim 10$  nanoamperes for bipolar op amps, tens of picoamperes for JFET input stages, and only a few pA for MOSFET input stages) flows into the inputs. When large resistors or sources with high output impedances are used in the circuit, these small currents can produce large unmodeled voltage drops. If the input currents are matched, and the impedance looking out of both inputs are matched, then the voltages produced at each input will be equal. Because the operational amplifier operates on the difference between its inputs, these matched voltages will have no effect. It is more common for the input currents to be slightly mismatched. The difference is called input offset current, and even with matched resistances a small offset voltage (different from the input offset voltage below) can be produced. This offset voltage can create offsets or drifting in the operational amplifier.

#### **5. Input Offset Voltage**

This voltage, which is what, is required across the op amp's input terminals to drive the output voltage to zero. In the perfect amplifier, there would be no input offset voltage. However, it exists in actual op amps because of imperfections in the differential amplifier that constitutes the input stage of the vast majority of these devices. Input offset voltage creates two problems: First, due to the amplifier's high voltage gain, it virtually assures that the amplifier output will go into saturation if it is operated without negative feedback, even when the input terminals are wired together. Second, in a closed loop, negative feedback configuration, the input offset voltage is amplified along with the signal and this may pose a problem if high precision DC amplification is required or if the input signal is very small.

#### **6. Common-mode Gain**

A perfect operational amplifier amplifies only the voltage difference between its two inputs, completely rejecting all voltages that are common to both. However, the differential input stage of an operational amplifier is never perfect, leading to the amplification of these common voltages to some degree. The standard measure of this defect is called the common-mode rejection ratio (denoted CMRR). Minimization of common mode gain is usually important in non-inverting amplifiers (described below) that operate at high amplification.

## **Chapter 4**

---

### **7. Power-supply Rejection**

The output of a perfect operational amplifier will be completely independent from its power supply. Every real operational amplifier has a finite power supply rejection ratio (PSRR) that reflects how well the op amp can reject changes in its supply voltage.

### **8. Finite Bandwidth**

All amplifiers have finite bandwidth. To a first approximation, the op amp has the frequency response of an integrator with gain. That is, the gain of a typical op amp is inversely proportional to frequency and is characterized by its gain-bandwidth product (GBWP). For example, an op amp with a GBWP of 1 MHz would have a gain of 5 at 200 kHz, and a gain of 1 at 1 MHz. This dynamic response coupled with the very high DC gain of the op amp gives it the characteristics of a first-order low-pass filter with very high DC gain and low cutoff frequency given by the GBWP divided by the DC gain.

### **9. Non-Linear Input-Output Relationship**

The output voltage may not be accurately proportional to the difference between the input voltages. It is commonly called distortion when the input signal is a waveform. This effect will be very small in a practical circuit where substantial negative feedback is used.

### **10. Limited Output Current**

The output current must be finite. In practice, most op amps are designed to limit the output current so as not to exceed a specified level – around 25 mA for a type 741 IC op amp – thus protecting the op amp and associated circuitry from damage. Modern designs are electronically more rugged than earlier implementations and some can sustain direct short circuits on their outputs without damage.

#### 4.15.2 Op-amp Configurations

##### 4.15.2.1 The Open-Loop Amplifier

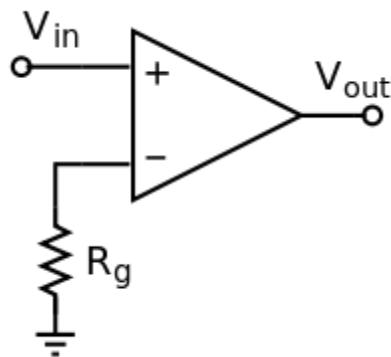


Figure 4.54 – An Op-Amp Without Feedback

The magnitude of  $A_{OL}$  is typically very large (100,000 or more for integrated circuit op amps), and therefore even a quite small difference between  $V_+$  and  $V_-$  drives the amplifier into clipping or saturation. The magnitude of  $A_{OL}$  is not well controlled by the manufacturing process, and so it is impractical to use an open-loop amplifier as a stand-alone differential amplifier. Without negative feedback, and optionally positive feedback for regeneration, an op-amp acts as a comparator. If the inverting input is held at ground (0 V), and the input voltage  $V_{in}$  applied to the non-inverting input is positive, the output will be maximum positive; if  $V_{in}$  is negative, the output will be maximum negative. Since there is no feedback from the output to either input, this is an open-loop circuit acting as a comparator.

##### 4.15.2.2 The Closed Loop Amplifier

In the closed loop configuration, the fraction of the output is fed to input via a feedback loop. Negative Feedback is the process of “feeding back” a fraction of the output signal back to the input, but to make the feedback negative, we must feed it back to the negative or “inverting input” terminal of the op-amp using an external Feedback Resistor called  $R_f$ . This feedback connection between the output and the inverting input terminal forces the differential input voltage towards zero. This effect produces a closed loop circuit to the amplifier resulting in the gain of the amplifier now being called its Closed-loop Gain. Then a closed-loop inverting amplifier uses negative feedback to accurately control the overall gain of the amplifier, but at a cost in the reduction of the amplifiers gain.

## Chapter 4

---

This negative feedback results in the inverting input terminal having a different signal on it than the actual input voltage as it will be the sum of the input voltage plus the negative feedback voltage giving it the label or term of a Summing Point. We must therefore separate the real input signal from the inverting input by using an Input Resistor,  $R_{in}$

### 4.15.2.3 An Inverting Operational Amplifier's Configuration

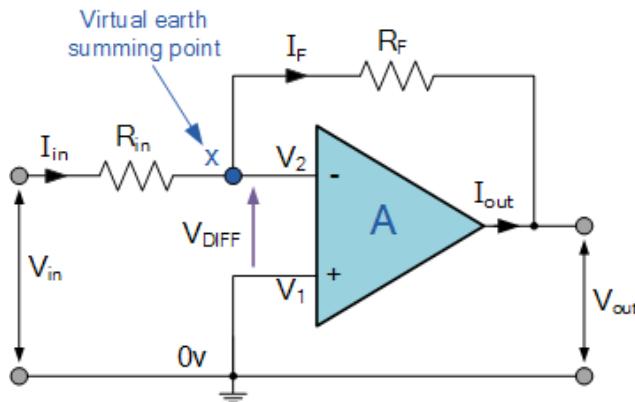


Figure 4.55 – Inverting Amplifier


In this Inverting Amplifier circuit, the operational amplifier is connected with feedback ( $R_f$ ) to produce a closed loop operation. The non-inverting input is connected to ground and the input signal is fed to the inverting input via the input resistance  $R_{in}$ . When dealing with operational amplifiers there are two very important rules to remember about inverting amplifiers, these are: “No current flows into the input terminal” and that “ $V_1$  always equals  $V_2$ ”. However, in real world op-amp circuits both of these rules are slightly broken. This is because the junction of the input and feedback signal (  $X$  ) is at the same potential as the positive ( + ) input which is at zero volts or ground then, the junction is a “Virtual Earth”. Because of this virtual earth node, the input resistance of the amplifier is equal to the value of the input resistor,  $R_{in}$  and the closed loop gain of the inverting amplifier can be set by the ratio of the two external resistors. Then by using the given two rules we can derive the equation for calculating the closed-loop gain of an inverting amplifier,

- No Current Flows into the Input Terminals
- The Differential Input Voltage is Zero as  $V_1 = V_2 = 0$  (Virtual Earth)

$$\text{Gain, } A_v = - R_f / R_{in}$$

The negative sign in the equation indicates an inversion of the output signal with respect to the input as it is  $180^\circ$  out of phase. This is due to the feedback being negative in value. The equation for the output voltage  $V_{out}$  also shows that the circuit is linear in nature for a fixed amplifier gain as  $V_{out} = V_{in} \times \text{Gain}$ . This property can be very useful for converting a smaller sensor signal to a much larger voltage. Another useful application of an inverting amplifier is that of a “transresistance amplifier” circuit. A Transresistance Amplifier also known as a “transimpedance amplifier”, is basically a current-to-voltage converter (Current “in” and Voltage “out”). They can be used in low-power applications to convert a very small current generated by a photo-diode or photo-detecting device etc, into a usable output voltage which is proportional to the input.

#### 4.15.2.4 A Non-Inverting Operational Amplifier’s Configuration

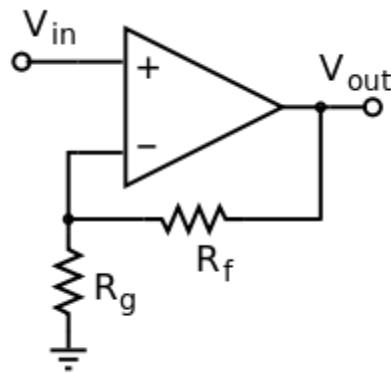

**Figure 4.56 – Non-Inverting Operational Amplifier Configuration**

In this configuration, the input voltage signal, ( $V_{in}$ ) is applied directly to the non-inverting (+) input terminal which means that the output gain of the amplifier becomes “Positive” in value in contrast to the “Inverting Amplifier” circuit we saw in the last tutorial whose output gain is negative in value. The result of this is that the output signal is “in-phase” with the input signal. Feedback control of the non-inverting operational amplifier is achieved by applying a small part of the output voltage signal back to the inverting (-) input terminal via a  $R_f - R_g$  voltage divider network, again producing negative feedback. This closed-loop configuration produces a non-inverting amplifier circuit with very good stability, a very high input impedance,  $R_{in}$  approaching infinity, as no current flows into the positive input terminal, (ideal conditions) and a low output impedance.

## Chapter 4

---

In the Inverting Amplifier, for an ideal op-amp “No current flows into the input terminal” of the amplifier and that “V1 always equals V2”. This was because the junction of the input and feedback signal ( V1 ) are at the same potential. In other words the junction is a “virtual earth” summing point. Because of this virtual earth node the resistors,  $R_f$  and  $R_g$  form a simple potential divider network across the inverting amplifier with the voltage gain of the circuit being determined by the ratios of  $R_g$  and  $R_f$  as shown below.

$$A_v = 1 + (R_f/R_g)$$

We can see from the equation above, that the overall closed-loop gain of a non-inverting amplifier will always be greater but never less than one (unity), it is positive in nature and is determined by the ratio of the values of  $R_f$  and  $R_g$ . If the value of the feedback resistor  $R_f$  is zero, the gain of the amplifier will be exactly equal to one (unity). If resistor  $R_g$  is zero the gain will approach infinity, but in practice it will be limited to the operational amplifiers open-loop differential gain, (  $A_o$  ). We can easily convert an inverting operational amplifier configuration into a non-inverting amplifier configuration by simply interchanging the input connection and the feedback loop.

### 4.15.2.5 Common-mode Rejection Ratio (CMRR)

If a signal is applied equally to both inputs of an op amp, so that the differential input voltage is unaffected, the output should not be affected. In practice, changes in common mode voltage will produce changes in output.

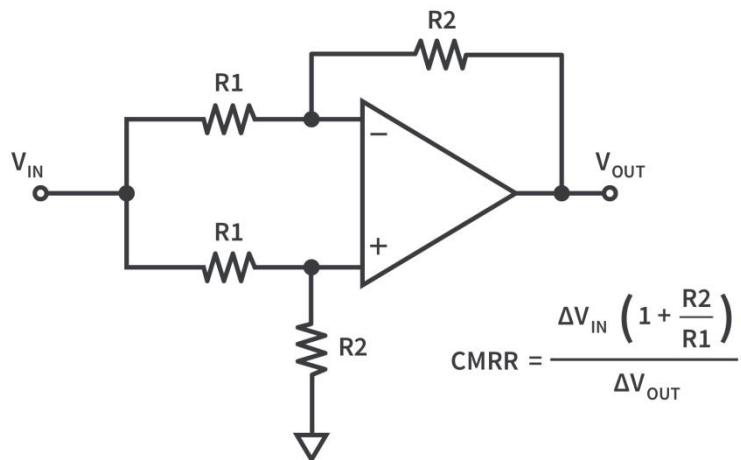


Figure 4.57 – CMRR Test Circuit


The op amp common-mode rejection ratio (CMRR) is the ratio of the common-mode gain to differential-mode gain. For example, if a differential input change of Y volts produces a change of 1 V at the output, and a common-mode change of X volts produces a similar change of 1 V, then the CMRR is X/Y. When the common-mode rejection ratio is expressed in dB, it is generally referred to as common-mode rejection (CMR)

#### 4.16 The Instrumentation Amplifier

An instrumentation amplifier (sometimes shorthanded as In-Amp or InAmp) is a type of differential amplifier that has been outfitted with input buffer amplifiers, which eliminate the need for input impedance matching and thus make the amplifier particularly suitable for use in measurement and test equipment. Additional characteristics include very low DC offset, low drift, low noise, very high open-loop gain, very high common-mode rejection ratio, and very high input impedances. Instrumentation amplifiers are used where great accuracy and stability of the circuit both short and long-term are required. Although the instrumentation amplifier is usually shown schematically identical to a standard operational amplifier (op-amp), the electronic instrumentation amp is almost always internally composed of 3 op-amps. These are arranged so that there is one op-amp to buffer each input (+, -), and one to produce the desired output with adequate impedance matching for the function.

The most commonly used instrumentation amplifier circuit is shown in the figure. The gain of the circuit is

$$Av = \frac{V_{out}}{V_2 - V_1} = (1 + (2R_1/R_{gain})) (R_3/R_2)$$

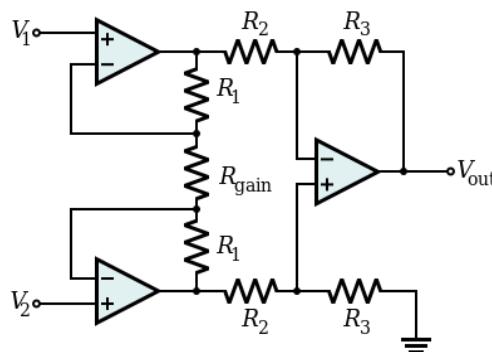

**Figure 4.58 – Typical Instrumentation Amplifier**

## Chapter 4

---

The rightmost amplifier, along with the resistors labelled and is just the standard differential amplifier circuit, with gain =  $R_3/R_2$  and differential input resistance =  $2 \cdot R_2$ . The two amplifiers on the left are the buffers.

With  $R_{\text{gain}}$  removed (open circuited), they are simple unity gain buffers; the circuit will work in that state, with gain simply equal to  $R_3/R_2$  and high input impedance because of the buffers.

The buffer gain could be increased by putting resistors between the buffer inverting inputs and ground to shunt away some of the negative feedback.

However, the single resistor  $R_{\text{gain}}$  between the two inverting inputs is a much more elegant method: it increases the differential-mode gain of the buffer pair while leaving the common-mode gain equal to 1. This increases the common-mode rejection ratio (CMRR) of the circuit and also enables the buffers to handle much larger common-mode signals without clipping than would be the case if they were separate and had the same gain.

Another benefit of the method is that it boosts the gain using a single resistor rather than a pair, thus avoiding a resistor-matching problem, and very conveniently allowing the gain of the circuit to be changed by changing the value of a single resistor. A set of switch-selectable resistors or even a potentiometer can be used for  $R_{\text{gain}}$ , providing easy changes to the gain of the circuit, without the complexity of having to switch matched pairs of resistors.

The ideal common-mode gain of an instrumentation amplifier is zero. In the circuit shown, common-mode gain is caused by mismatch in the resistor ratios  $R_2/R_3$  and by the mis-match in common mode gains of the two-input op-amps. Obtaining very closely matched resistors is a significant difficulty in fabricating these circuits, as is optimizing the common mode performance.

An instrumentation amp can also be built with two op-amps to save on cost, but the gain must be higher than two (+6 dB). Instrumentation amplifiers can be built with individual op-amps and precision resistors, but are also available in integrated circuit form from several manufacturers (including Texas Instruments, Analog Devices, Linear Technology and Maxim Integrated Products). An IC instrumentation amplifier typically contains closely matched laser-trimmed resistors, and therefore offers excellent common-mode rejection.

#### 4.17 The Multivibrator

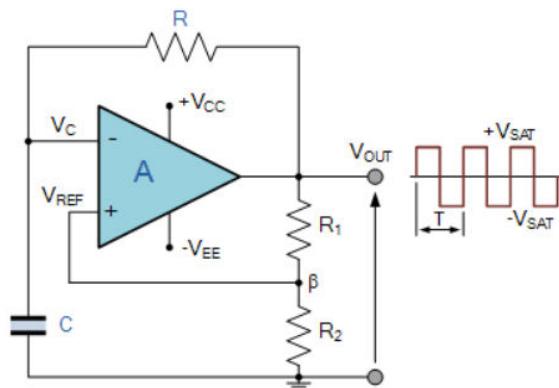


Figure 4.59 – An Op-amp Multivibrator

The Op-amp Multivibrator is an astable oscillator circuit that generates a rectangular output waveform using an RC timing network connected to the inverting input of the operational amplifier and a voltage divider network connected to the other non-inverting input.

Unlike the monostable or bistable, the astable multivibrator has two states, neither of which are stable as it is constantly switching between these two states with the time spent in each state controlled by the charging or discharging of the capacitor through a resistor. In the op-amp multivibrator circuit the op-amp works as an analogue comparator.

An op-amp comparator compares the voltages on its two inputs and gives a positive or negative output depending on whether the input is greater or less than some reference value, V<sub>REF</sub>. However, because the open-loop op-amp comparator is very sensitive to the voltage changes on its inputs, the output can switch uncontrollably between its positive, +V(sat) and negative, -V(sat) supply rails whenever the input voltage being measured is near to the reference voltage, V<sub>REF</sub>.

To eliminate any erratic or uncontrolled switching operations, the op-amp used in the multivibrator circuit is configured as a closed-loop Schmitt Trigger circuit. Schmitt trigger that uses positive feedback provided by resistors R<sub>1</sub> and R<sub>2</sub> to generate hysteresis.

Firstly, let's assume that the capacitor is fully discharged and the output of the op-amp is saturated at the positive supply rail.

## Chapter 4

---

The capacitor, C starts to charge up from the output voltage,  $V_{out}$  through resistor,  $R$  at a rate determined by their RC time constant. We know from our tutorials about RC circuits that the capacitor wants to charge up fully to the value of  $V_{out}$  (which is  $+V(\text{sat})$ ) within five-time constants.

However, as soon as the capacitors charging voltage at the op-amps inverting (-) terminal is equal to or greater than the voltage at the non-inverting terminal (the op-amps output voltage fraction divided between resistors  $R_1$  and  $R_2$ ), the output will change state and be driven to the opposing negative supply rail. But the capacitor, which has been happily charging towards the positive supply rail ( $+V(\text{sat})$ ), now sees a negative voltage,  $-V(\text{sat})$  across its plates. This sudden reversal of the output voltage causes the capacitor to discharge toward the new value of  $V_{out}$  at a rate dictated again by their RC time constant.

Thus, the capacitor is constantly charging and discharging creating an astable op-amp multivibrator output. The period of the output waveform is determined by the RC time constant of the two-timing components and the feedback ratio established by the  $R_1$ ,  $R_2$  voltage divider network which sets the reference voltage level. If the positive and negative values of the amplifier's saturation voltage have the same magnitude, then  $t_1 = t_2$  and the expression to give the period of oscillation becomes:


$$\beta = \frac{R_2}{R_1 + R_2}$$
$$T = 2RC \times \ln\left(\frac{1+\beta}{1-\beta}\right) \quad \therefore f = \frac{1}{T}$$

Where:  $R$  is Resistance,  $C$  is Capacitance,  $\ln()$  is the Natural Logarithm of the feedback fraction,  $T$  is periodic time in seconds, and  $f$  is oscillation Frequency in Hz. Then we can see from the above equation that the frequency of oscillation for an Op-amp Multivibrator circuit not only depends upon the RC time constant but also upon the feedback fraction.

However, if we used resistor values that gave a feedback fraction of 0.462, ( $\beta = 0.462$ ), then the frequency of oscillation of the circuit would be equal to just  $1/2RC$  as shown because the linear log term becomes equal to one. Also, when the two feedback resistors are the same, that is  $R_1 = R_2$ , the feedback fraction is equal to 3 and the frequency of oscillation becomes:  $f = 1/2.2RC$ . We can take this op-amp multivibrator circuit one step further by replacing one of the feedback resistors with a potentiometer to produce a variable frequency op-amp multivibrator.

**4.18 Series Voltage Regulator Using an Op-Amp**

The series regulator circuit using op-amp is shown below.

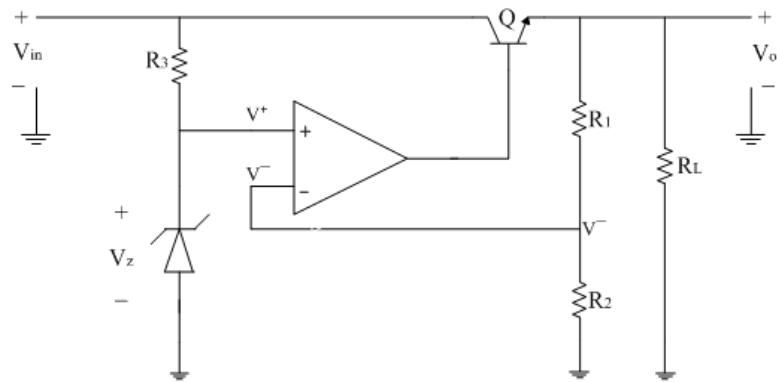

**Figure 4.60 – Series Voltage Regulator**

The op-amp is used as a comparator. It compares the part of the output voltage obtained from potential divider circuit as a feedback with the reference voltage generated by the zener diode  $V_z$ . The output of the op-amp drives the series pass transistor  $Q$ . If there is any change in the output voltage the control signal from the op-amp controls the conduction of the transistor  $Q$ . Thus, the output voltage is maintained at a constant level.

From virtual ground concept

$$V_- = V_+$$

$$V_- = V_+ = [V_o/(R_1+R_2)] R_2$$

The voltage at non-inverting terminal  $V_+$  is nothing but the zener voltage  $V_z$  as shown in figure above.

$$V_+ = V_z$$

The output voltage can be expressed as

$$V_o = [(R_1+R_2)/R_2] V_+$$

$$\therefore V_o = [(R_1+R_2)/R_2] V_z$$

$$\therefore V_o = [1+R_1/R_2] V_z$$

## Chapter 4

### 4.19 The 4-20 mA Current Loop Transmitter Using an Op-Amp

In instrumentation circuitry, DC signals are often used as analog representations of physical measurements such as temperature, pressure, flow, weight, and motion. Most commonly, DC current signals are used in preference to DC voltage signals, because current signals are exactly equal in magnitude throughout the series circuit loop carrying current from the source (measuring device) to the load (indicator, recorder, or controller), whereas voltage signals in a parallel circuit may vary from one end to the other due to resistive wire losses. Furthermore, current-sensing instruments typically have low impedances (while voltage-sensing instruments have high impedances), which gives current-sensing instruments greater electrical noise immunity.

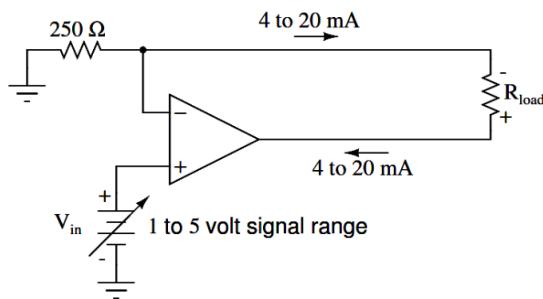


Figure 4.61 – 4-20 mA Transmitter

The input voltage to this circuit is assumed to be coming from some type of physical transducer/amplifier arrangement, calibrated to produce 1 volt at 0 percent of physical measurement, and 5 volts at 100 percent of physical measurement. The standard analog current signal range is 4 mA to 20 mA, signifying 0% to 100% of measurement range, respectively. With a 5 volts input, the 250 Ω (precision) resistor will have 5 volts applied across it, resulting in 20 mA of current in the large loop circuit (with  $R_{load}$ ).

It does not matter what resistance value  $R_{load}$  is, or how much wire resistance is present in that large loop, so long as the op-amp has a high enough power supply voltage to output the voltage necessary to get 20 mA flowing through  $R_{load}$ .

The  $250\ \Omega$  resistor establishes the relationship between input voltage and output current, in this case creating the equivalence of 1-5 V in / 4-20 mA out. If we were converting the 1-5-volt input signal to a 10-50 mA output signal (an older, obsolete instrumentation standard for industry), we'd use a  $100\ \Omega$  precision resistor instead.

## Chapter 4

---

In the end of this book, I would like to take the opportunity to thank all my readers. May all of you achieve more and more in life. All the best for your future. I would like to convey a happy message to all of you by a quote by Swami Vivekanand that is close to my heart, "Strength is Life, Weakness is Death. Expansion is Life, Contraction is Death. Love is Life, Hatred is Death." Thank You.



### Sources

- <https://www.circuitstoday.com/>
- <https://en.wikipedia.org/>
- <https://www.electronics-notes.com/>
- <https://www.electrical4u.com/>
- <https://instrumentationtools.com/>
- <https://www.electronics-tutorials.ws/>
- <https://industrialcircuits.wordpress.com/>
- <https://www.circuitstoday.com/>
- <https://www.electronicshub.org/>
- <https://news.energysage.com/>
- <https://www.differencebetween.com/>

## 🚢 Chapter 5 🚦 ICs and LSI

---



## **Chapter 5**

---

### **5.1 Introduction**

An electronic circuit is created by connecting different discrete components like resistors, capacitors, transistors, mosfets, etc., by soldering them on a PCB (printed circuit board). But it has lot of disadvantages - it consumes lot of space and the chance for a break down is very high due to lots of soldering joints, so it is less reliable. To overcome these problems scientists, developed a method to create the whole circuit into a single silicon chip to form a small package called an Integrated Circuit or IC. That means every IC contain lots of discrete components and they are connected in a manner to achieve a particular function. By this method, the cost and space re easily reduced and also the reliability is greatly increased. ICs are now used in virtually all electronic systems and have revolutionized the world of electronics. Computers, mobile phones, and other digital home appliances are now inextricable parts of the structure of modern societies, made possible by the small size and low cost of ICs.

#### **5.1.1 Advantages of an IC**

- The entire physical size of IC is extremely small than that of discrete circuit.
- The weight of an IC is very less as compared entire discrete circuits.
- It is more reliable.
- Lower power consumption.
- It can easily replace but it can hardly repair, in case of failure.
- High operating speed due to low parasitic capacitance.
- Temperature differences between components of a circuit are small.
- It has suitable for small signal operation.
- Low cost

#### **5.1.2 Disadvantages of an IC**

- It can handle only a limited amount of power.
- It is difficult to be achieved low temperature coefficient.
- The power dissipation is limited to 10 watts.
- Low noise and high voltage operation are not easily obtained.
- Inductors and transformers are needed connecting to exterior to the semiconductor chip as it is not possible to fabricate inductor and transformers on the semiconductor chip surface.
- Not repairable in the case of failure.

Semiconductor ICs are fabricated in a planar process which includes three key process steps – photolithography, deposition (such as chemical vapour deposition), and etching. The main process steps are supplemented by doping and cleaning. More recent or high-performance ICs may instead use the use of multi-gate FinFET or GAAFET transistors instead of planar ones, starting at the 22 nm node (Intel) or 16/14 nm nodes.

Mono-crystal silicon wafers are used in most applications (or for special applications, other semiconductors such as gallium arsenide are used). The wafer need not be entirely silicon. Photolithography is used to mark different areas of the substrate to be doped or to have polysilicon, insulators or metal (typically aluminium or copper) tracks deposited on them. Dopants are impurities intentionally introduced to a semiconductor to modulate its electronic properties. Doping is the process of adding dopants to a semiconductor material.

## **5.2 Fabrication**

Integrated circuits are composed of many overlapping layers, each defined by photolithography, and normally shown in different colors. Some layers mark where various dopants are diffused into the substrate (called diffusion layers), some define where additional ions are implanted (implant layers), some define the conductors (doped polysilicon or metal layers), and some define the connections between the conducting layers (via or contact layers). All components are constructed from a specific combination of these layers.

- In a self-aligned CMOS process, a transistor is formed wherever the gate layer (polysilicon or metal) crosses a diffusion layer.
- Capacitive structures, in form very much like the parallel conducting plates of a traditional electrical capacitor, are formed according to the area of the “plates”, with insulating material between the plates. Capacitors of a wide range of sizes are common on ICs.
- Meandering stripes of varying lengths are sometimes used to form on-chip resistors, though most logic circuits do not need any resistors. The ratio of the length of the resistive structure to its width, combined with its sheet resistivity, determines the resistance.
- More rarely, inductive structures can be built as tiny on-chip coils, or simulated by gyrators.

## Chapter 5

---

There are different technologies to develop the ICs. These are indicating the different generation of this process. Those are SSI, MSI, LSI, VLSI and ULSI. The comparison is given below in the table.

Acronym	Name	Year	Transistor count
SSI	Small scale integration	1964	1-10
MSI	Medium scale integration	1968	10-500
LSI	Large scale integration	1971	500-20000
VLSI	Very large-scale integration	1980	20000-1000000
ULSI	Ultra large-scale integration	1984	>1000000

### 5.3 Large Scale Integration (LSI)

Large-scale integration (LSI) is the process of integrating or embedding thousands of transistors on a single silicon semiconductor microchip. LSI technology was conceived in the mid-1970s when computer processor microchips were under development. LSI is no longer in use. It was succeeded by very large-scale integration (VLSI) and ultra large-scale integration (ULSI) technologies.

### 5.4 Logic Gate Families

Logic Gates like NAND, NOR are used in daily applications for performing logic operations. The Gates are manufactured using semiconductor devices like BJT, Diodes, or FETs. Digital logic circuits are manufactured depending on the specific circuit technology or logic families. The different logic families are RTL (Resistor Transistor Logic), DTL (Diode Transistor Logic), TTL (Transistor-Transistor Logic), ECL (Emitter Coupled Logic) and CMOS (Complementary Metal Oxide Semiconductor Logic). Out of these, RTL and DTL are rarely used. Here we discuss about Transistor-Transistor Logic (TTL) and Emitter Coupled Logic (ECL).

### 5.5 TTL (Transistor Transistor Logic)

The TTL or Transistor-Transistor Logic was invented in the year 1961 by “James L. Buie of TRW”. It is suitable for developing new integrated circuits. The actual name of this TTL is TCTL which means transistor-coupled transistor logic. After their introduction in integrated circuit form in 1963 by Sylvania Electric Products, TTL integrated circuits were manufactured by several semiconductor companies. The 7400 series by Texas Instruments became particularly popular.

TTL manufacturers offered a wide range of logic gates, flip-flops, counters, and other circuits. Variations of the original TTL circuit design offered higher speed or lower power dissipation to allow design optimization.

TTL devices were originally made in ceramic and plastic dual in-line package(s) and in flat-pack form. Some TTL chips are now also made in surface-mount technology packages. The designing of TTL logic gates can be done with resistors and BJTs. There are several variants of TTL which are developed for different purposes such as the radiation-hardened TTL packages for space applications and Low power Schottky diodes that can provide an excellent combination of speed and lesser power consumption.

TTL inputs are the emitters of bipolar transistors. In the case of NAND inputs, the inputs are the emitters of multiple-emitter transistors, functionally equivalent to multiple transistors where the bases and collectors are tied together. The output is buffered by a common emitter amplifier.


When all the inputs are held at high voltage, the base-emitter junctions of the multiple-emitter transistor are reverse-biased. But a small collector current (approximately  $10\mu A$ ) is drawn by each of the inputs. This is because the transistor is in reverse-active mode. An approximately constant current flows from the positive rail, through the resistor and into the base of the multiple emitter transistors. This current passes through the base-emitter junction of the output transistor, allowing it to conduct and pulling the output voltage low (logical zero).

The base-collector junction of the multiple-emitter transistor and the base-emitter junction of the output transistor is in series between the bottom of the resistor and ground. If one input voltage becomes zero, the corresponding base-emitter junction of the multiple-emitter transistor is in parallel with these two junctions.

A phenomenon called current steering means that when two voltage-stable elements with different threshold voltages are connected in parallel, the current flows through the path with the smaller threshold voltage. That is, current flows out of this input and into the zero (low) voltage source. As a result, no current flows through the base of the output transistor, causing it to stop conducting and the output voltage becomes high (logical one).

## Chapter 5

---

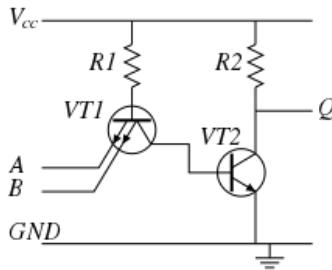

**Figure 5.1 – TTL (Transistor Transistor Logic)**

During the transition the input transistor is briefly in its active region; so it draws a large current away from the base of the output transistor and thus quickly discharges its base. This is a critical advantage of TTL that speeds up the transition.

TTL logic includes several transistors that have several emitters as well as several inputs. The types of TTL or transistor-transistor logic mainly include Standard TTL, Fast TTL, Schottky TTL, High power TTL, Low power TTL and Advanced Schottky TTL.

### 5.5.1 Characteristics of TTL

**Fan Out:** Number of loads the output of a GATE can drive without affecting its usual performance. By load we mean the amount of current required by the input of another Gate connected to the output of the given gate.

**Power Dissipation:** It represents the amount of power needed by the device. It is measured in mW. It is usually the product of supply voltage and the amount of average current drawn when the output is high or low.


**Propagation Delay:** It represents the transition time that elapses when the input level changes. The delay which occurs for the output to make its transition is the propagation delay.

**Noise Margin:** It represents the amount of noise voltage allowed at the input, which doesn't affect the standard output.

### Open Collector Output

The main feature is that its output is 0 when low and floating when high. Usually, an external Vcc may be applied. Transistor Q1 behaves as a cluster of diodes placed back-to-back. With any of the input at logic low, the corresponding emitter-base junction is forward biased and the voltage drop across the base of Q1 is around 0.9V, not enough for the transistors Q2 and Q3 to conduct.

Thus, the output is either floating or  $V_{CC}$ , i.e., High level. Similarly, when all inputs are high, all base-emitter junctions of  $Q1$  are reverse biased and transistor  $Q2$  and  $Q3$  get enough base current and are in saturation mode. The output is at logic low. (For a transistor to go to saturation, collector current should be greater than  $\beta$  times the base current).

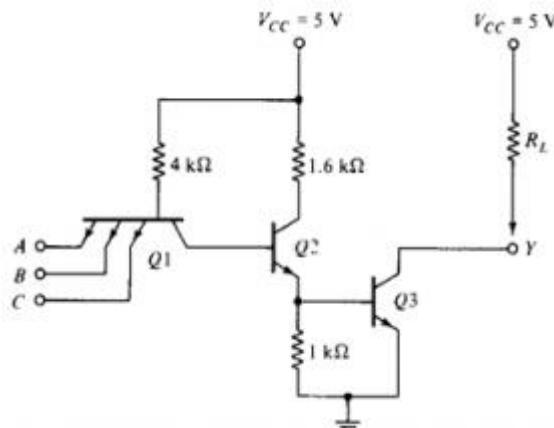

**Figure 5.2 – Open Collector Output**

### 5.5.2 Applications


- In driving lamps or relays
- In performing wired logic
- In the construction of a common bus system

### 5.5.3 Totem Pole Output

Totem Pole means the addition of an active pull up the circuit in the output of the Gate which results in a reduction of propagation delay. Logic operation is the same as the open collector output. The use of transistors  $Q4$  and diode is to provide quick charging and discharging of parasitic capacitance across  $Q3$ . The resistor is used to keep the output current to a safe value.

## Chapter 5

---

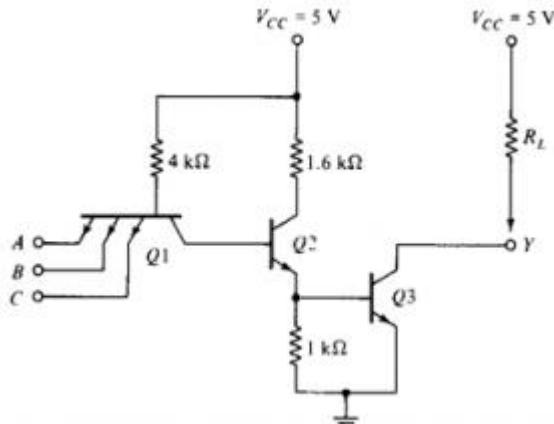

**Figure 5.3 – Totem Pole Output**

### 5.5.4 TTL Family Features

- Logic low level is at 0 or 0.2V.
- Logic high level is at 5V.
- Typical fan out of 10. It means it can support at most 10 gates at its output.
- A basic TTL device draws a power of almost 10mW, which reduces with the use of Schottky devices.
- The average propagation delay is about 9ns.
- The noise margin is about 0.4V.

### 5.5.5 ECL (Emitter Coupled Logic)

The Emitter-coupled logic (ECL) is a BJT-based logic family which is generally considered as the fastest logic available. ECL achieves its high-speed operation by employing a relatively small voltage swing and preventing the transistors from entering the saturation region. In the late 1960s, when the standard TTL family offered 20 ns gate delay the ECL offered an incredible delay of only 1 ns.

ECL is based on an emitter-coupled pair consists of two parallel-connected input transistors and another one parallel-connected transistor in which its base is connected to a reference voltage for implementing NOR logic. The common emitter resistor  $RE$  acts nearly as a current source.

## 5.6 Two-input ECL OR / NOR gate

The circuit comprises of an emitter-coupled logic circuit of the 2-input OR / NOR gate. In this, two transistors are used at the input side. If the input at both the transistors Q1 and Q2 are LOW, it will make VOUT1 to HIGH value. It corresponds to the NOR gate output. At the same time, transistor Q3 is turned ON, which will make the VOUT2 to be HIGH. It corresponds to the OR gate output. Similarly, if both the input of transistors Q1 and Q2 are HIGH, it will turn on both the transistors. It will drive the output at terminal VOUT1 to be LOW. The transistor Q3 is turned OFF during this operation. It will drive the output at terminal VOUT2 to be HIGH.

### 5.6.1 Advantages

- High-speed operation is possible and so the fastest logic family.
- Since transistors are not allowed to enter into saturation, which reduces the storage delay.
- Fan-out capability is high.

Apart from the advantages, it also has its own disadvantage. For the fast switching of transistors, the low and high logic levels are kept close. It reduces the noise margin. Since transistors are not allowed to enter into saturation, the power consumption is more.

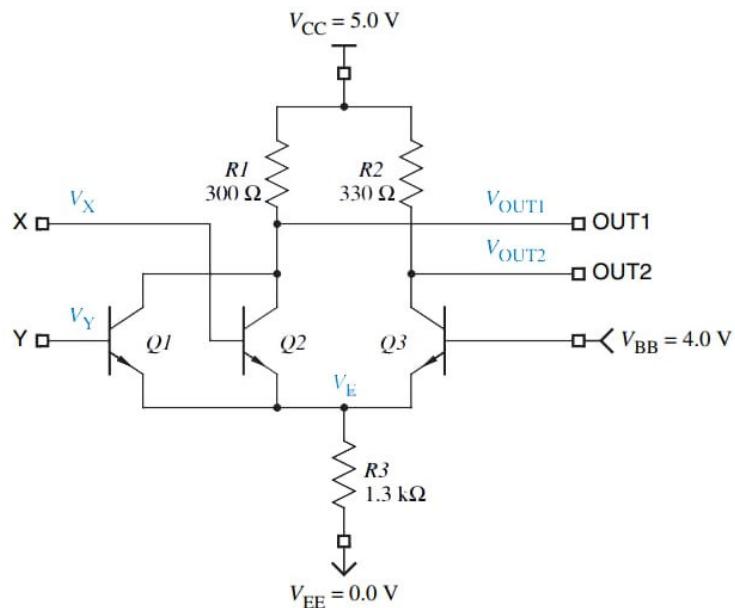


Figure 5.4 – Two-input ECL OR / NOR Gate

## Chapter 5

---

ECL circuits usually operate with negative power supplies (positive end of the supply is connected to ground). Other logic families ground the negative end of the power supply. This is done mainly to minimize the influence of the power supply variations on the logic levels. ECL is more sensitive to noise on the VCC and is relatively immune to noise on VEE. Because ground should be the most stable voltage in a system, ECL is specified with a positive ground.

### 5.7 TTL Comparison with ECL

Specification	TTL	ECL
Basic Gate	NAND	OR/NOR
Fan-out	10	25
Noise Immunity	Strong	Good
Clock Speed in MHz	35	>60
Power in mW	10	40-55
Propagation Delay in ns	10-30	1-2
Noise Margin	Medium	Low

### 5.8 Semiconductor Memories

A Memory is the portion of a system for storing data in large quantities. In semiconductor memories latches or capacitors are used to store the data in binary form either a logical Zero or a logical One. The smallest unit of binary data is a bit. The collection of 8 bits is called a byte of data.

The data is stored as arrays and the one bit of data in it is called a cell. The location of each cell is called an address. There are two major semiconductor memory categories RAM (Random access memory) and ROM (Read only memory).

#### 5.8.1 RAM (Random Access Memory)

In a RAM, all the addresses are accessible in an equal amount of time and can be selected on any order for a read or write operation. All RAMs have both read and write capabilities. RAM loose stored data when the power is turned off, so they are volatile memories. Flip-Flop is an example for RAM.

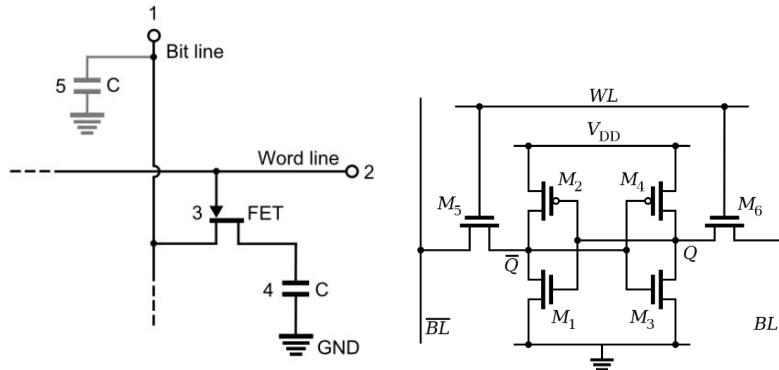


Figure 5.5 – RAM Circuits

The two widely used forms of modern RAM are static RAM (SRAM) and dynamic RAM (DRAM). In SRAM, a bit of data is stored in flip-flop storage cells that are typically implemented with six-transistor memory cell, typically using six MOSFETs (metal-oxide-semiconductor field-effect transistors). This form of RAM is more expensive to produce, but is generally faster and requires less dynamic power than DRAM. In modern computers, SRAM is often used as cache memory for the CPU. DRAM stores a bit of data using a transistor and capacitor pair (typically a MOSFET and MOS capacitor, respectively), which together comprise a DRAM cell. The capacitor holds a high or low charge (1 or 0, respectively), and the transistor acts as a switch that lets the control circuitry on the chip read the capacitor's state of charge or change it. As this form of memory is less expensive to produce than static RAM, it is the predominant form of computer memory used in modern computers.

### 5.8.2 ROM (Read Only Memory)

In a ROM, data is stored permanently or semi permanently. Data can be read from a ROM, but there is no write operation as in the RAM. The ROM, like the RAM is a random-access memory but the term RAM traditionally means a random-access read / write memory. ROMs store data even if power is turned off, so they are non-volatile memories.

### 5.8.3 EPROM

Erasable programmable read-only memory (EPROM) is a type of Programmable ROM which retains its data when the power supply goes off (non-volatile). It can be reprogrammed if an existing program in the memory array is erased first. It contains an NMOSFET array with an isolated gate structure. There are two types - based on the memory-erasing method.

## **Chapter 5**

---

First there is the UVEPROM, here erase can be done by exposure of the mercury array chip to a high intensity UV radiation through quartz window on top of the package. It can be easily recognizable by the transparent fused quartz window on the top of the package, through which the silicon chip is visible. The erasing window must be kept covered with an opaque label to prevent accidental erasure by the UV found in sunlight or camera flashes.

The second one is the EEPROM, it is electrically erasable programmable ROM. It can be both programmed and erased by using electrical pulses. It is available in floating gate type MOS and Metal nitride-oxide silicone (MNOS) types.

### **5.8.4 CMOS Memory**

Complementary metal–oxide–semiconductor (CMOS), is a type of metal–oxide–semiconductor field-effect transistor (MOSFET) fabrication process that uses complementary and symmetrical pairs of p-type and n-type MOSFETs for logic functions. CMOS technology is used for constructing integrated circuit (IC) chips, including microprocessors, microcontrollers, memory chips (including CMOS BIOS), and other digital logic circuits. CMOS technology is also used for analog circuits such as image sensors (CMOS sensors), data converters, RF circuits (RF CMOS), and highly integrated transceivers for many types of communication.

CMOS memory is the area of memory which is sort of semi-permanent. . CMOS holds data very well with minimal power (by the use of a low voltage battery), meaning that it can retain important system configuration data for a device even when it is powered off. Unlike ROM however, CMOS can be updated and changed through the use of plug and play devices. It stores things such as the amount of memory installed, the date and time for the system, the number and size of the hard drives that are installed and the clock.

## **5.9 Central Processing Unit (CPU)**

A central processing unit (CPU) is an electronic circuitry that executes instructions comprising a computer program. The CPU performs basic arithmetic, logic, controlling, and input/output (I/O) operations specified by the instructions in the program. This contrasts with external components such as main memory and I/O circuitry, and specialized processors such as graphics processing units (GPUs).

Principal components of a CPU include the arithmetic logic unit (ALU) that performs arithmetic and logic operations, processor registers that supply operands to the ALU and store the results of ALU operations, and a control unit that controls the fetching (from memory) and execution of instructions by directing the coordinated operations of the ALU, registers and other components.

### ***5.9.1 Operation***


The fundamental operation of most CPUs, regardless of the physical form they take, is to execute a sequence of stored instructions that is called a program. The instructions to be executed are kept in some kind of computer memory. Nearly all CPUs follow the fetch, decode and execute steps in their operation, which are collectively known as the instruction cycle. After the execution of an instruction, the entire process repeats, with the next instruction cycle normally fetching the next-in-sequence instruction because of the incremented value in the program counter.

If a jump instruction was executed, the program counter will be modified to contain the address of the instruction that was jumped to and program execution continues normally. In more complex CPUs, multiple instructions can be fetched, decoded and executed simultaneously. Some instructions manipulate the program counter rather than producing result data directly; such instructions are generally called “jumps” and facilitate program behavior like loops, conditional program execution (through the use of a conditional jump), and existence of functions. In some processors, some other instructions change the state of bits in a “flags” register.

These flags can be used to influence how a program behaves, since they often indicate the outcome of various operations. For example, in such processors a “compare” instruction evaluates two values and sets or clears bits in the flags register to indicate which one is greater or whether they are equal; one of these flags could then be used by a later jump instruction to determine program flow.

## Chapter 5

---

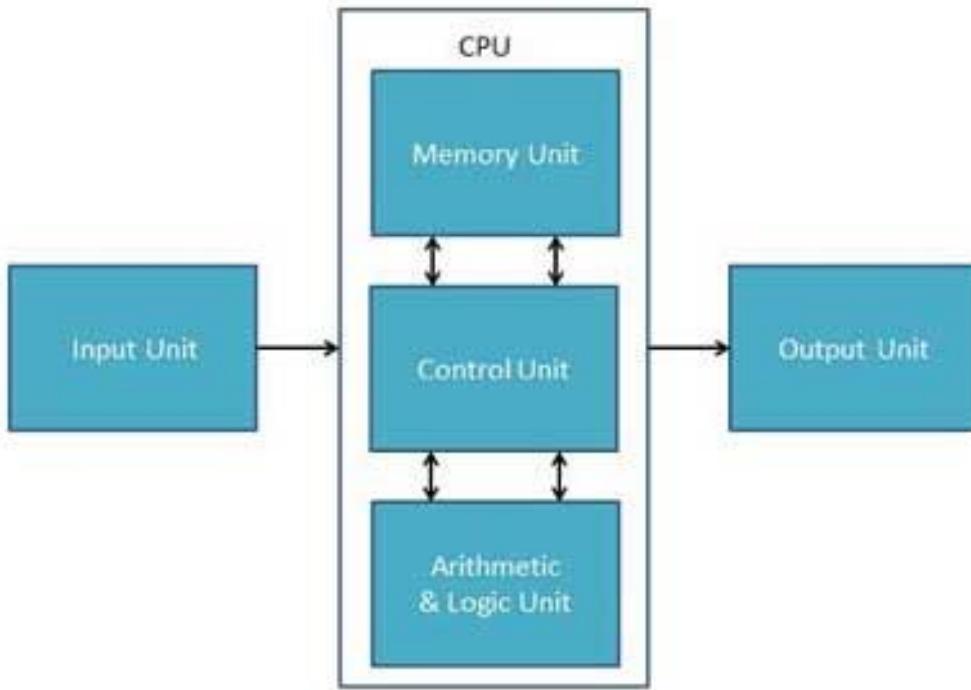

**Figure 5.6 – A Block Diagram of A CPU**

### 5.9.2 *Fetch*

The first step, fetch, involves taking an instruction from program memory. The instruction's location (address) in program memory is determined by the program counter (PC) which stores a number that identifies the address of the next instruction to be fetched.

After an instruction is fetched, the PC is incremented by the length of the instruction so that it will contain the address of the next instruction in the sequence.

### 5.9.3 *Decode*

The instruction that the CPU fetches from memory determines what the CPU will do. In the decode step, performed by the circuitry known as the instruction decoder, the instruction is converted into signals that control other parts of the CPU.

One group of bits (“field”) within the instruction, called the opcode, indicates which operation is to be performed, while the remaining fields usually provide supplemental information required for the operation, such as the operands. Those operands may be specified as a constant value (called an immediate value), or as the location of a value that may be a processor register or a memory address, as determined by some addressing mode.

#### **5.9.4 Execute**

After the fetch and decode steps, the execute step is performed. Depending on the CPU architecture, this may consist of a single action or a sequence of actions. During each action, various parts of the CPU are electrically connected so they can perform all or part of the desired operation and then the action is completed, typically in response to a clock pulse.


Very often the results are written to an internal CPU register for quick access by subsequent instructions. In other cases, results may be written to slower, but less expensive and higher capacity main memory.

For example, if an addition instruction is to be executed, the arithmetic logic unit (ALU) inputs are connected to a pair of operand sources (numbers to be summed), the ALU is configured to perform an addition operation so that the sum of its operand inputs will appear at its output, and the ALU output is connected to storage (e.g., a register or memory) that will receive the sum.

When the clock pulse occurs, the sum will be transferred to storage and, if the resulting sum is too large (i.e., it is larger than the ALU's output word size), an arithmetic overflow flag will be set.

## Chapter 5

---

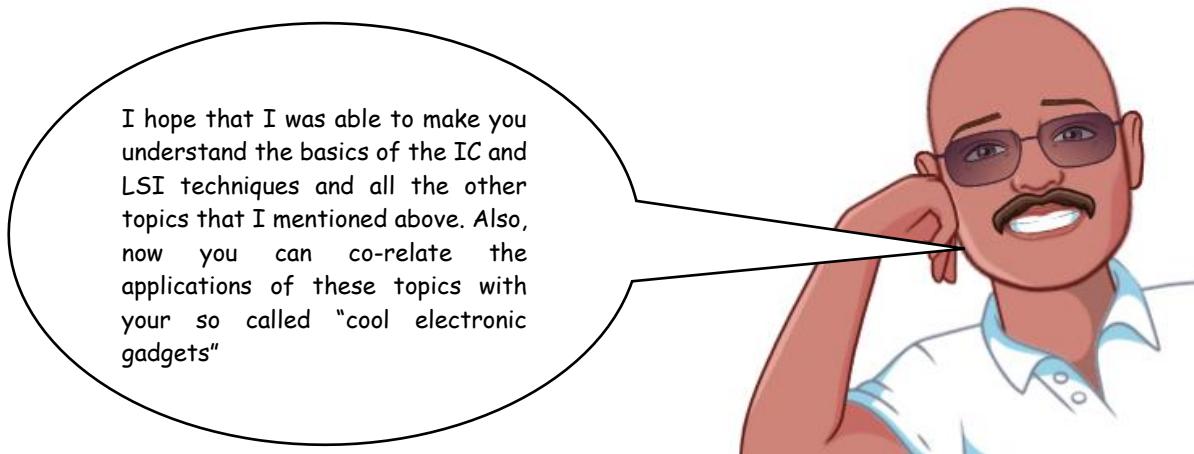


### Sources

- [www.dauenotes.com/](http://www.dauenotes.com/)
- [www.elprocus.com/](http://www.elprocus.com/)
- [www.wikipedia.org/](http://www.wikipedia.org/)
- [http://wakerly.org/DDPP/DDPP4student/Supplementary\\_sections/ECL.pdf](http://wakerly.org/DDPP/DDPP4student/Supplementary_sections/ECL.pdf)

## 🚢 Chapter 6 🚢 Digital Techniques

---

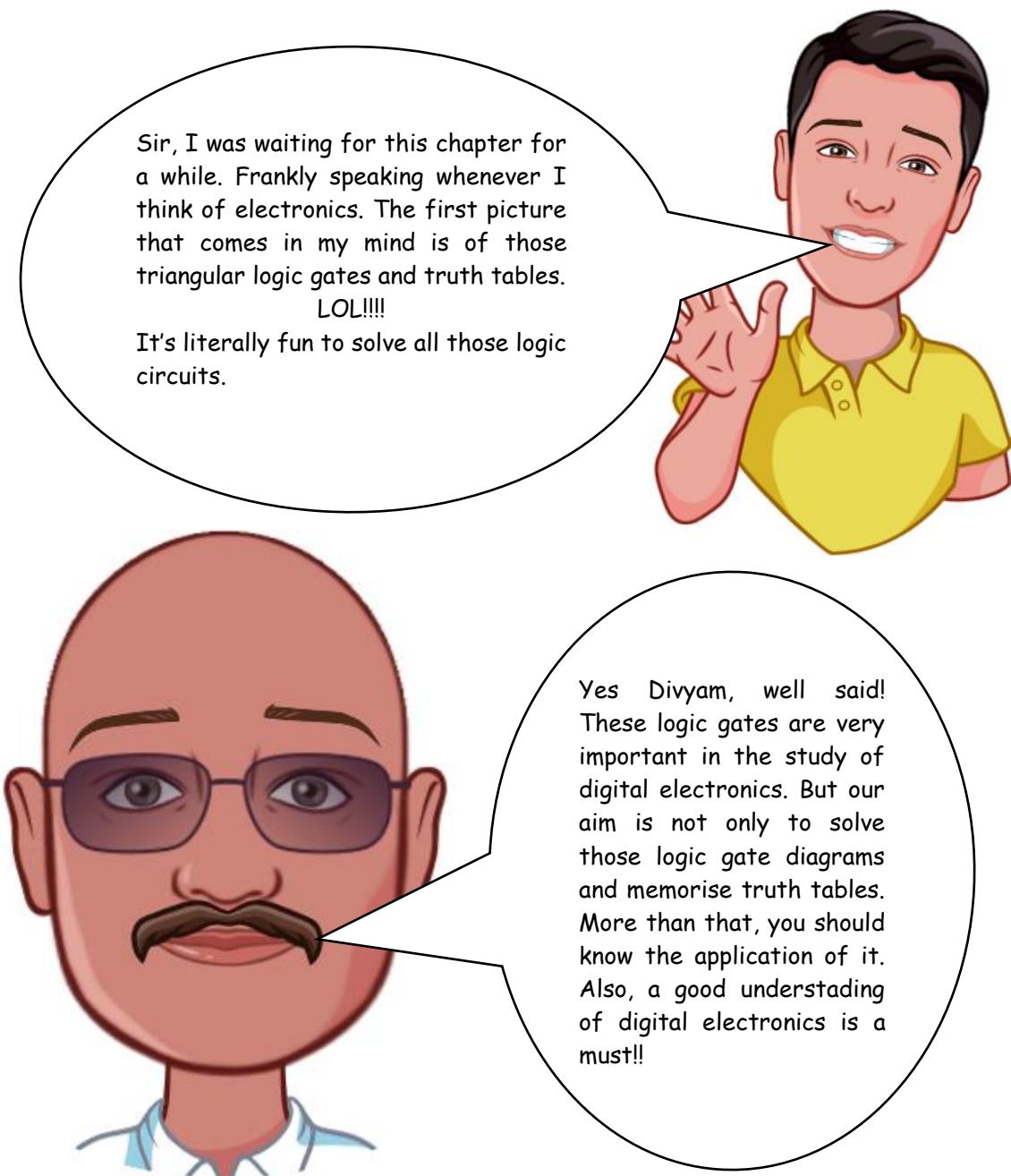

## Chapter 6

### 6.1 Introduction

Nowadays, computers have become an integral part of life as they perform many tasks and operations in quite a short span of time. One of the most important functions of the CPU in a computer is to perform logical operations by utilizing hardware like Integrated Circuits software technologies and electronic circuits, but, how this hardware and software perform such operations is a mysterious puzzle. In order to have a better understanding of such a complex issue, we must have to acquaint ourselves with the term Boolean Logic, developed by George Boole. For a simple operation, computers utilize binary digits rather than digital digits. All the operations are carried out by the Basic Logic gates. This article discusses an overview of what are **basic logic gates** in digital electronics and their working.

### 6.2 What are Basic Logic Gates?

A logic gate is a basic building block of a digital circuit that has two inputs and one output. The relationship between the i/p and the o/p is based on a certain logic. These gates are implemented using electronic switches like transistors, diodes. But, in practice, basic logic gates are built using CMOS technology, FETS, and MOSFET (Metal Oxide Semiconductor FET)s. Logic gates are used in microprocessors, microcontrollers, embedded system applications, and in electronic and electrical project circuits. The basic logic gates are categorized into seven: AND, OR, XOR, NAND, NOR, XNOR, and NOT. These logic gates with their logic gate symbols and truth tables are explained below.



Figure 6.1 – Basic Logic Gates Operation

### 6.3 What are the 7 Basic Logic Gates?

The basic logic gates are classified into seven types: AND gate, OR gate, XOR gate, NAND gate, NOR gate, XNOR gate, and NOT gate. The truth table is used to show the logic gate function. All the logic gates have two inputs except the NOT gate, which has only one input.

When drawing a truth table, the binary values 0 and 1 are used. Every possible combination depends on the number of inputs. If you don't know about the logic gates and their truth tables and need guidance on them, please go through the following infographic that gives an overview of logic gates with their symbols and truth tables.

### 6.4 Why we use Basic Logic Gates?

The basic logic gates are used to perform fundamental logical functions. These are the basic building blocks in the digital ICs (integrated circuits). Most of the logic gates use two binary inputs and generates a single output like 1 or 0. In some electronic circuits, few logic gates are used whereas in some other circuits, microprocessors include millions of logic gates.

The implementation of Logic gates can be done through diodes, transistors, relays, molecules, and optics otherwise different mechanical elements. Because of this reason, basic logic gates are used like electronic circuits.

#### 6.4.1 Binary and Decimal

Before talking about the truth tables of logic gates, it is essential to know the background of binary and decimal numbers. We all know the decimal numbers which we utilize in everyday calculations like 0 to 9. This kind of number system includes the base-

In the same way, binary numbers like 0 and 1 can be utilized to signify decimal numbers wherever the base of the binary numbers is 2.

The significance of using binary numbers here is to signify the switching position otherwise voltage position of a digital component. Here 1 represents the High signal or high voltage whereas "0" specifies low voltage or low signal. Therefore, Boolean algebra was started. After that, each logic gate is discussed separately this contains the logic of the gate, truth table, and its typical symbol.

## Chapter 6

### 6.5 Types of Logic Gates

The different types of logic gates and symbols with truth tables are discussed below:

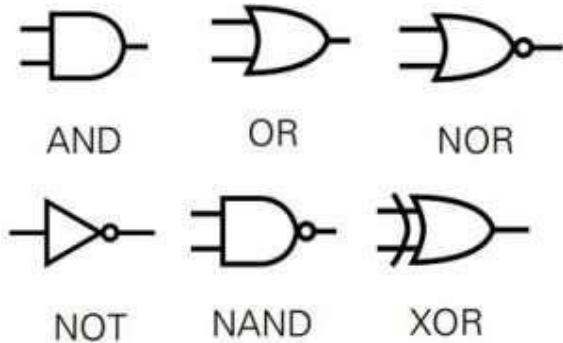


Figure 6.2 – Basic Logic Gates

#### 6.5.1 AND Gate

The AND gate is a digital logic gate with ‘n’ inputs (i/p/s) one output (o/p), which performs logical conjunction based on the combinations of its inputs. The output of this gate is true only when all the inputs are true. When one or more inputs of the AND gate’s i/p/s are false, then only the output of the AND gate is false. The symbol and truth table of an AND gate with two inputs is shown below.

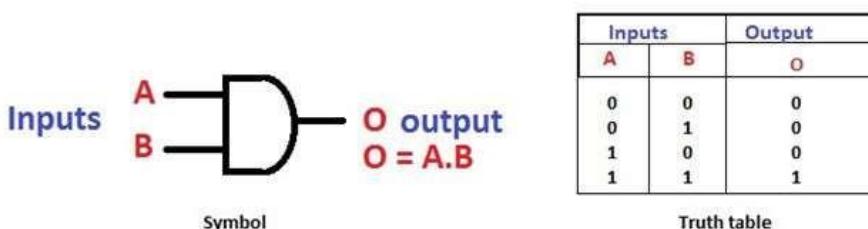


Figure 6.3 – The AND Gate and its Truth Table

#### 6.5.2 OR Gate

The OR gate is a digital logic gate with ‘n’ i/p/s and one o/p, that performs logical conjunction based on the combinations of its inputs. The output of the OR gate is true only when one or more inputs are true. If all the i/p/s of the gate are false, then only the output of the OR gate is false. The symbol and truth table of an OR gate with two inputs is shown below.

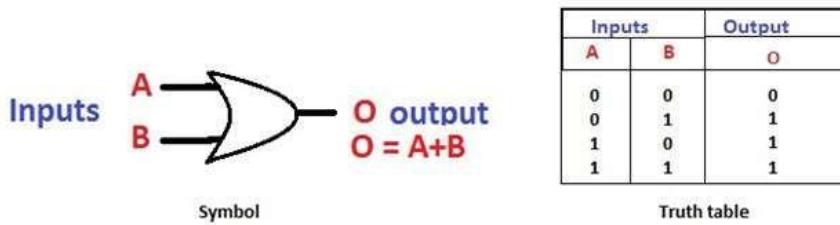


Figure 6.4 – An OR Gate and its Truth Table

### 6.5.3 NOT Gate

The NOT gate is a digital logic gate with one input and one output that operates an inverter operation of the input. The output of the NOT gate is the reverse of the input. When the input of the NOT gate is true then the output will be false and vice versa. The symbol and truth table of a NOT gate with one input is shown below. By using this gate, we can implement NOR and NAND gates.

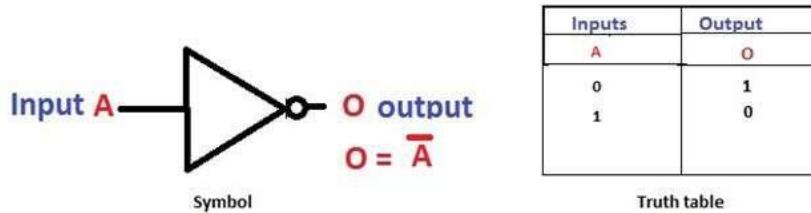


Figure 6.5 – A NOT Gate and Its Truth Table

### 6.5.4 NAND Gate

The NAND gate is a digital logic gate with ‘n’ i/p/s and one o/p, that performs the operation of the AND gate followed by the operation of the NOT gate. A NAND gate is designed by combining the AND with the NOT gates. If the input of the NAND gate high, then the output of the gate will be low. The symbol and truth table of the NAND gate with two inputs is shown below.


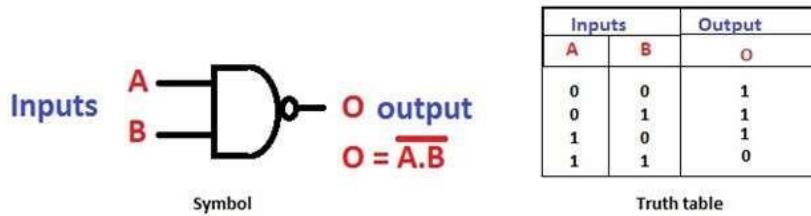


Figure 6.6 – NAND Gate and its Truth Table

## ***Chapter 6***

### 6.5.5 NOR Gate


The NOR gate is a digital logic gate with  $n$  inputs and one output, that performs the operation of the OR gate followed by the NOT gate. NOR gate is designed by combining the OR and NOT gate. When any one of the i/p/s of the NOR gate is true, then the output of the NOR gate will be false. The symbol and truth table of the NOR gate with the truth table is shown below.

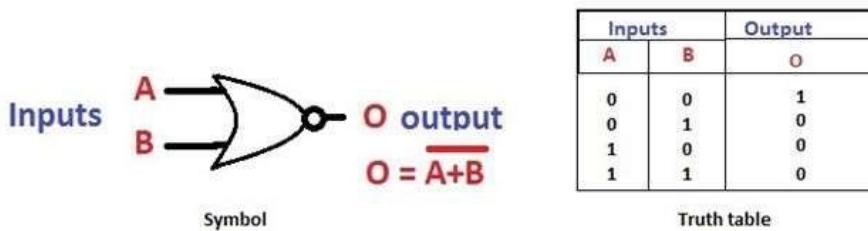

**Figure 6.7 – The NOR Gate and Its Truth Table**

### 6.5.6 Exclusive-OR Gate

The Exclusive-OR gate is a digital logic gate with two inputs and one output. The short form of this gate is Ex-OR. It performs based on the operation of the OR gate. If any one of the inputs of this gate is high, then the output of the EX-OR gate will be high. The symbol and truth table of the EX-OR are shown below.

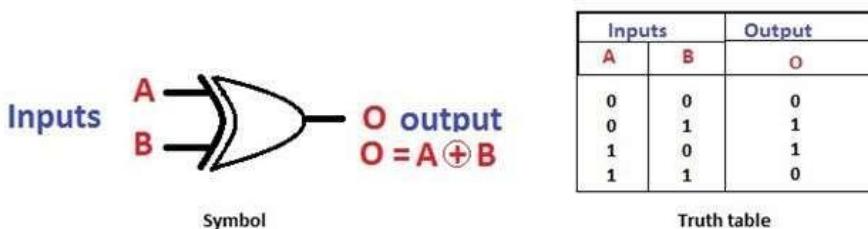


**Figure 6.8 – The EX-OR gate and Its Truth Table**

### 6.5.7 Exclusive-NOR Gate

The Exclusive-NOR gate is a digital logic gate with two inputs and one output. The short form of this gate is Ex-NOR. It performs based on the operation of the NOR gate.

When both the inputs of this gate are high, then the output of the EX-NOR gate will be high. But, if any one of the inputs is high (but not both), then the output will be low.

The symbol and truth table of the EX-NOR are shown below:

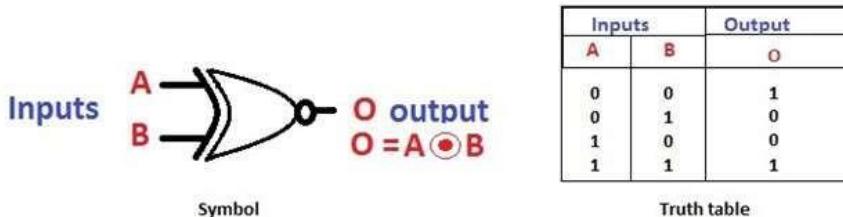

**Figure 6.9 – EX-NOR Gate and Its Truth Table**

The applications of logic gates are mainly determined based upon their truth table, i.e., their mode of operations. The basic logic gates are used in many circuits like a push-button lock, light-activated burglar alarm, safety thermostat, an automatic watering system, etc.

#### 6.5.8 Truth Table to Express Logic Gate Circuit

A gate circuit can be expressed using a common method known as a truth table as shown in the previous Figure 5. This table includes all the input logic state combinations either high (1) or low (0) for every input terminal of the logic gate through the equivalent output logic level like high or low. The NOT logic gate circuit is shown above and its truth table is extremely easy indeed

The truth tables of logic gates are very complex but larger than the NOT gate. The truth table of each gate must include many rows like there are possibilities for exclusive combinations for inputs. For instance, for the NOT gate, there are two possibilities of inputs either 0 or 1, whereas, for the two-input logic gate, there are four possibilities like 00, 01, 10 and 11. Therefore, it includes four rows for the equivalent truth table. For a 3-input logic gate, there are 8 possible inputs like 000, 001, 010, 011, 100, 101, 110 and 111. Therefore, a truth table including 8 rows is required. Mathematically, the required number of rows in the truth table is equivalent to 2 increased to the power of the no. of i/p terminals.

#### 6.5.9 Analysis

The voltage signals in the digital circuits are represented with binary values like 0's and 1's calculated in reference to ground. The deficiency of voltage mainly signifies a "0" whereas the existence of full DC supply voltage signifies a "1". A logic gate is a special type of amplifier circuit that is mainly designed for input as well as output logic level voltages. Logic gate circuits are most frequently symbolized with a schematic diagram through their own exclusive symbols instead of their essential resistors and transistors.

## **Chapter 6**

---

Just like with Op-Amps (operational amplifiers), the connections of power supply to logic gates are frequently misplaced in schematic diagrams for the benefit of simplicity. It includes the probable input logic level combinations through their particular output logic levels.

The easiest way to learn the function of basic logic gates is explained below:

- For AND Gate – If both the inputs are high then the output is also high
- For OR Gate – If a minimum of one input is high then the output is High
- For XOR Gate – If the minimum one input is high then only the output is high
- NAND Gate – If the minimum one input is low then the output is high
- NOR Gate – If both the inputs are low then the output is high.

### **6.6 De Morgan's Theorem**

The first theorem of DeMorgan states that the logic gate like NAND is equal to an OR gate with a bubble. The logic function of the NAND gate is


$$A'B = A' + B'$$

The second theorem of DeMorgan states that the NOR logic gate is equal to an AND gate with a bubble. The logic function of NOR gate is

$$(A+B)' = A' \cdot B'$$

## 6.7 The Conversion of the NAND Gate


The NAND gate can be formed using AND gate and the NOT gate. The Boolean expression and truth table is shown below.

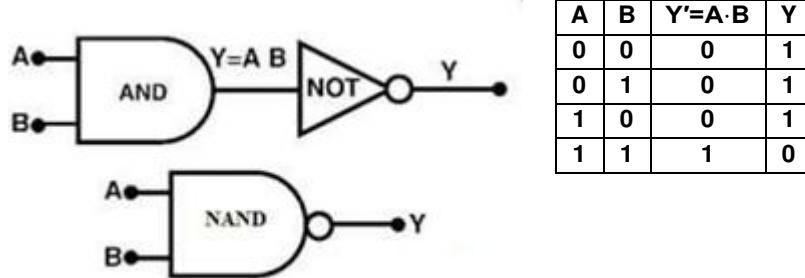

**Figure 6.10 – NAND Logic Gates Formation  $Y = (A \cdot B)'$**

### 6.7.1 NOR Gate Conversion

The NOR gate can be formed using OR gate and NOT gate. The Boolean expression and truth table is shown below.

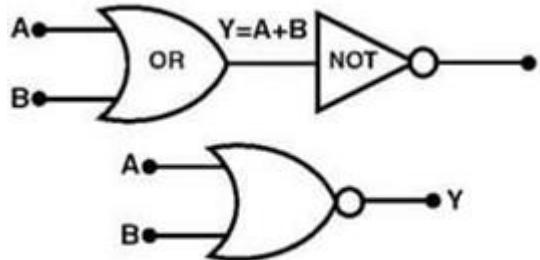

**Figure 6.11 – NOR Logic Gates Formation**

$$Y = (A + B)'$$

A	B	$Y' = A + B$	Y
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

## Chapter 6

### 6.8 Ex-OR Gate Conversion

The Ex-OR gate can be formed using NOT, AND and OR gate. The Boolean expression and truth table is shown below. This logic gate can be defined as the gate that gives high output once any input of this is high. If both the inputs of this gate are high then the output will be low.


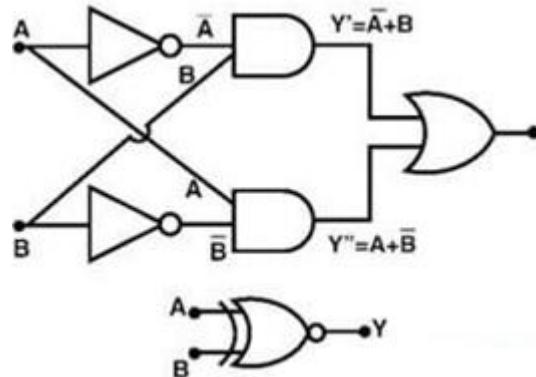


Figure 6.12 – Ex-OR Logic Gates Formation  $Y = A \oplus B$  or  $A'B + AB'$

### 6.9 Ex-NOR Gate Conversion

The Ex-NOR gate can be formed using EX-OR gate and NOT gate. The Boolean expression and truth table is shown below. In this logic gate, when the output is high “1” then both the inputs will be either “0” or “1”.

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

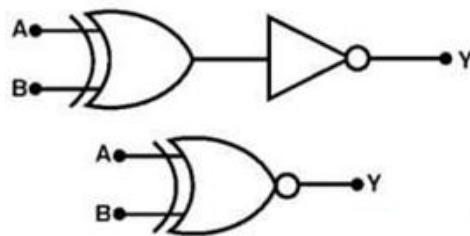

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

**Figure 6.13 – Ex-NOR Gate Formation  $Y = (A'B + AB')'$**

### 6.11 Basic Logic Gates using Universal Gates

Universal gates like NAND gate and NOR gate can be implemented through any boolean expression without using any other type of logic gate. And, they can also be used for designing any basic logic gate. Additionally, these are extensively utilized in integrated circuits as they are simple as well as cost-effective to make. The basic logic gates design using universal gates are discussed below.

The basic logic gates can be designed with the help of universal gates. It uses an error, a bit of test otherwise you can utilize Boolean logic for attaining these through the logic gates equations for a NAND gate as well as a NOR gate.

Here, Boolean logic is used to solve the output you require. It takes some time but it is needed to perform this to obtain a hang of Boolean logic as well as basic logic gates.

## **Chapter 6**

---

### **6.11.1 Basic Logic Gates Using NAND Gate**

The designing of basic logic gates using NAND gate is discussed below.

#### **6.11.1.1 NOT Gate Design using NAND**

The designing of the NOT gate is very simple by simply connecting both the inputs as one.

#### **6.11.1.2 AND Gate Design using NAND**

The designing of AND gate using NAND gate can be done at the NAND gate's output to reverse it and obtain AND logic.

#### **6.11.1.3 OR Gate Design using NAND**

The designing of OR gate using NAND gate can be done by connecting two NOT gates using NAND gates at the NAND's inputs to obtain OR logic.

#### **6.11.1.4 NOR Gate Design using NAND**

The designing of NOR gate using NAND gate can be done by simply connecting another NOT gate through NAND gate to the o/p of an OR gate through NAND. EXOR Gate Design using NAND

This one's a bit tricky. You share the two inputs with three gates. The output of the first NAND is the second input to the other two. Finally, another NAND takes the outputs of these two NAND gates to give the final output.

### **6.11.2 Basic Logic Gates using NOR Gate**

The designing of basic logic gates using NOR gate is discussed below.

#### **6.11.2.1 NOT Gate using NOR**

The designing of NOT gate with NOR gate is simple by connecting both the inputs as one.

#### **6.11.2.2 OR Gate using NOR**

The designing of OR Gate with NOR gate is simple by connecting at the o/p of the NOR gate to reverse it and obtain OR logic.

#### **6.11.2.3 AND Gate using NOR**

The designing of AND gate using NOR gate can be done by connecting two NOT with NOR gates at the NOR inputs to obtain AND logic.

#### **6.11.2.4 NAND Gate using NOR**

The designing of NAND Gate using NOR gate can be done by simply connecting another NOT gate through NOR gate to the AND gate's output with NOR.

#### **6.11.2.5 EX-NOR Gate using NOR**

This type of connection is a bit difficult because the two inputs can be shared with three logic gates. The first NOR gate output is the next input to the remaining two gates. Finally, another NOR gate uses the two NOR gate outputs to provide the last output.

#### **6.11.2.6 Applications**

The applications of basic logic gates are so many however they mostly depend on their truth tables otherwise form of operations. Basic logic gates are frequently used in circuits like a lock with push-button, the watering system automatically, burglar alarm activated through light, safety thermostat and other types of electronic devices.

The main advantage of basic logic gates is, these can be used in a different combination circuit. In addition, there is no boundary to the number of logic gates that can be utilized in a single electronic device. But it can be limited because of the specified physical gap within the device. In digital ICs (integrated circuits) we will discover a collection of the logic gate region unit.

By using mixtures of basic logic gates, advanced operations are often performed. In theory, there's no limit to the number of gates that may be clad along during a single device. However, in the application, there's a limit to the number of gates that may be packed into a given physical area. Arrays of the logic gate area unit are found in digital integrated circuits (ICs). As IC technology advances, the desired physical volume for every individual gate decrease, and digital devices of an equivalent or smaller size become capable of acting with more complicated operations at ever-increasing speeds.

## Chapter 6

### 6.12 Laws of Boolean Algebra

As well as the logic symbols “0” and “1” being used to represent a digital input or output, we can also use them as constants for a permanently “Open” or “Closed” circuit or contact respectively.



A set of rules or Laws of Boolean Algebra expressions have been invented to help reduce the number of logic gates needed to perform a particular logic operation resulting in a list of functions or theorems known commonly as the laws of boolean algebra.






Boolean Algebra is the mathematics we use to analyse digital gates and circuits. We can use these “Laws of Boolean” to both reduce and simplify a complex Boolean expression in an attempt to reduce the number of logic gates required. Boolean Algebra is therefore a system of mathematics based on logic that has its own set of rules or laws which are used to define and reduce Boolean expressions.

The variables used in Boolean Algebra only have one of two possible values, a logic “0” and a logic “1” but an expression can have an infinite number of variables all labelled individually to represent inputs to the expression, for example, variables A, B, C etc, giving us a logical expression of  $A + B = C$ , but each variable can ONLY be a 0 or a 1.

Examples of these individual laws of Boolean, rules and theorems for Boolean Algebra are given in the following table.

#### 6.12.1 Truth Tables for the Laws of Boolean

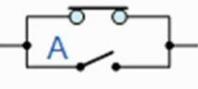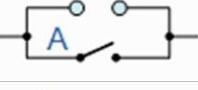Boolean Expression	Description	Equivalent Switching Circuit	Boolean Algebra Law or Rule
$A + 1 = 1$	A in parallel with closed = “CLOSED”		Annulment
$A + 0 = A$	A in parallel with open = “A”		Identity
$A \cdot 1 = A$	A in series with closed = “A”		Identity
$A \cdot 0 = 0$	A in series with open = “OPEN”		Annulment

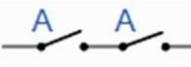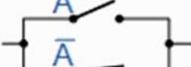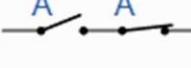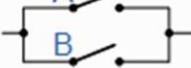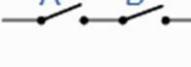Boolean Expression	Description	Equivalent Switching Circuit	Boolean Algebra Law or Rule
$A + A = A$	A in parallel with A = "A"		Idempotent
$A \cdot A = A$	A in series with A = "A"		Idempotent
$\text{NOT } A = A$	NOT NOT A (double negative) = "A"		Double Negation
$A + A = 1$	A in parallel with NOT A = "CLOSED"		Complement
$A \cdot A = 0$	A in series with NOT A = "OPEN"		Complement
$A+B = B+A$	A in parallel with B = B in parallel with A		Commutative
$A \cdot B = B \cdot A$	A in series with B = B in series with A		Commutative
$A+B = A \cdot \bar{B} + B \cdot \bar{A}$	invert and replace OR with AND		de Morgan's Theorem
$A \cdot B = A + B \cdot \bar{A}$	invert and replace AND with OR		de Morgan's Theorem

The basic Laws of Boolean Algebra that relate to the Commutative Law allowing a change in position for addition and multiplication, the Associative Law allowing the removal of brackets for addition and multiplication, as well as the Distributive Law allowing the factoring of an expression, are the same as in ordinary algebra.

Each of the Boolean Laws above are given with just a single or two variables, but the number of variables defined by a single law is not limited to this as there can be an infinite number of variables as inputs to the expression. These Boolean laws detailed above can be used to prove any given Boolean expression as well as for simplifying complicated digital circuits. A brief description of the various Laws of Boolean is given below with A representing a variable input.

## Chapter 6

---

### 6.12.2 Description of the Laws of Boolean Algebra

- Annulment Law – A term AND ‘ed with a “0” equals 0 or OR ‘ed with a “1” = 1
  - $A \cdot 0 = 0$  A variable AND’ed with 0 is always equal to 0
  - $A + 1 = 1$  A variable OR’ed with 1 is always equal to 1
- Identity Law – A term OR ‘ed with a “0” or AND ‘ed with a “1” will always equal that term
  - $A + 0 = A$  A variable OR’ed with 0 is always equal to the variable
  - $A \cdot 1 = A$  A variable AND’ed with 1 is always equal to the variable
- Idempotent Law – An input that is AND’ed or OR’ed with itself is equal to that input
  - $A + A = A$  A variable OR’ed with itself is always equal to the variable
  - $A \cdot A = A$  A variable AND’ed with itself is always equal to the variable
- Complement Law – A term AND’ed with its complement equals “0” and a term OR’ed with its complement equals “1”
  - $A \cdot \bar{A} = 0$  A variable AND’ed with its complement is always equal to 0
  - $A + \bar{A} = 1$  A variable OR’ed with its complement is always equal to 1
- Commutative Law – The order of application of two separate terms is not important
- $A \cdot B = B \cdot A$  The order in which two variables are AND’ed makes no difference
- $A + B = B + A$  the order in which two variables are OR’ed makes no difference
- Double Negation Law – A term that is inverted twice is equal to the original term
  - $\bar{\bar{A}} = \bar{A}$  A double complement of a variable is always equal to the variable
- de\_Morgan’s\_Theorem – There are two “de Morgan’s” rules or theorems:
  - (1) Two separate terms NOR ‘ed together is the same as the two terms inverted (Complement) and AND ‘ed for example:  $A+B = \bar{A} \cdot \bar{B}$
  - (2) Two separate terms NAND ‘ed together is the same as the two terms inverted (Complement) and OR ‘ed for example:  $A \cdot B = \bar{A} + \bar{B}$

Other algebraic Laws of Boolean not detailed above include:

- Boolean\_Postulates – While not Boolean Laws in their own right, these are a set of Mathematical Laws which can be used in the simplification of Boolean Expressions.
  - $0 \cdot 0 = 0$  A 0 AND'ed with itself is always equal to 0
  - $1 \cdot 1 = 1$  A 1 AND'ed with itself is always equal to 1
  - $1 \cdot 0 = 0$  A 1 AND'ed with a 0 is equal to 0
  - $0 + 0 = 0$  A 0 OR'ed with itself is always equal to 0
  - $1 + 1 = 1$  A 1 OR'ed with itself is always equal to 1
  - $1 + 0 = 1$  A 1 OR'ed with a 0 is equal to 1
  - $1 = 0$  The Inverse (Complement) of a 1 is always equal to 0
  - $0 = 1$  The Inverse (Complement) of a 0 is always equal to 1
- Distributive Law – This law permits the multiplying or factoring out of an expression.
- $A(B + C) = A \cdot B + A \cdot C$  (OR Distributive Law)
- $A + (B \cdot C) = (A + B) \cdot (A + C)$  (AND Distributive Law)
- Absorptive Law – This law enables a reduction in a complicated expression to a simpler one by absorbing like terms.
- $A + (A \cdot B) = (A \cdot 1) + (A \cdot B) = A(1 + B) = A$  (OR Absorption Law)
- $A(A + B) = (A + 0) \cdot (A + B) = A + (0 \cdot B) = A$  (AND Absorption Law)
- Associative Law – This law allows the removal of brackets from an expression and regrouping of the variables.
- $A + (B + C) = (A + B) + C = A + B + C$  (OR Associate Law)
- $A(B \cdot C) = (A \cdot B)C = A \cdot B \cdot C$  (AND Associate Law)

## Chapter 6

---

### 6.12.3 Boolean Algebra Functions

Using the information above, simple 2-input AND, OR and NOT Gates can be represented by 16 possible functions as shown in the following table:

Function	Description	Expression
1.	NULL	0
2.	IDENTITY	1
3.	Input A	A
4.	Input B	B
5.	NOT A	A
6.	NOT B	B
7.	A AND B (AND)	A . B
8.	A AND NOT B	A . B
9.	NOT A AND B	A . B
10.	NOT AND (NAND)	A . B
11.	A OR B (OR)	A + B
12.	A OR NOT B	A + B
13.	NOT A OR B	A + B
14.	NOT OR (NOR)	A + B
15.	Exclusive-OR	A . B + A . B
16.	Exclusive-NOR	A . B + A . B

### 6.12.4 Laws of Boolean Algebra Example No1

Using the above laws, simplify the following expression:  $(A + B)(A+C)$   $Q = (A+B).(A+C)$

$A.A + A.C + A.B + B.C$  – Distributive law

$A + A.C + A.B + B.C$  – Idempotent AND law ( $A.A = A$ )

$A(1 + C) + A.B + B.C$  – Distributive law

$A.1 + A.B + B.C$  – Identity OR law

$(1 + C = 1) A(1 + B) + B.C$  – Distributive law

$A.1 + B.C$  – Identity OR law ( $1 + B = 1$ )

$Q = A + (B.C)$  – Identity AND law ( $A.1 = A$ )

Then the expression:

$(A + B)(A + C)$  can be simplified to  $A + (B.C)$  as in the Distributive law.

### **6.13 Transistor-Transistor Logic (TTL)**

The Transistor-Transistor Logic (TTL) is a logic family made up of BJTs (bipolar junction transistors). As the name suggests, the transistor performs two functions like logic as well as amplifying. The best examples of TTL are logic gates namely the 7402 NOR Gate and the 7400 NAND gate.

TTL logic includes several transistors that have several emitters as well as several inputs. The types of TTL or transistor-transistor logic mainly include Standard TTL, Fast TTL, Schottky TTL, High power TTL, Low power TTL and Advanced Schottky TTL.

The designing of TTL logic gates can be done with resistors and BJTs. There are several variants of TTL which are developed for different purposes such as the radiation-hardened TTL packages for space applications and Low power Schottky diodes that can provide an excellent combination of speed and lesser power consumption.

#### **6.13.1 TTL Family Features**

The features of the TTL family include the following.

- Logic low level is at 0 or 0.2V.
- Logic high level is at 5V.
- Typical fan out of 10. It means it can support at most 10 gates at its output.
- A basic TTL device draws a power of almost 10mW, which reduces with the use of Schottky devices.
- The average propagation delay is about 9ns.
- The noise margin is about 0.4V

## Chapter 6

### 6.13.2 NOT GATE Implementation by TTL

When the input is low, the corresponding base-emitter junction is forward biased, and the base-collector junction is reverse biased. As a result, transistor Q2 is cut off and also transistor Q4 is cut off. Transistor Q3 goes to saturation and diode D2 starts conducting and output is connected to Vcc and goes to logic high. Similarly, when input is at logic high, the output is at logic low.

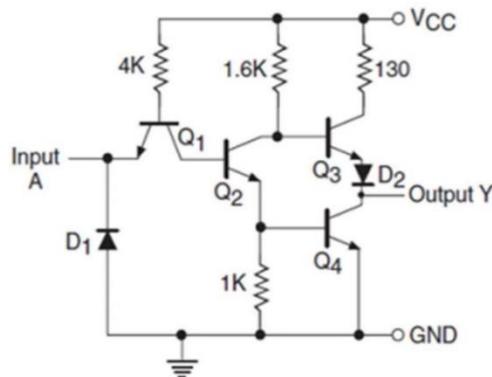


Figure 6.14 –A TTL Not Gate Circuit

### 6.14 CMOS (Complementary Metal Oxide Semiconductor)

The main advantage of CMOS over NMOS and BIPOLAR technology is the much smaller power dissipation. Unlike NMOS or BIPOLAR circuits, a Complementary MOS circuit has almost no static power dissipation. Power is only dissipated in case the circuit actually switches. This allows integrating more CMOS gates on an IC than in NMOS or bipolar technology, resulting in much better performance. Complementary Metal Oxide Semiconductor transistor consists of P-channel MOS (PMOS) and N-channel MOS (NMOS)


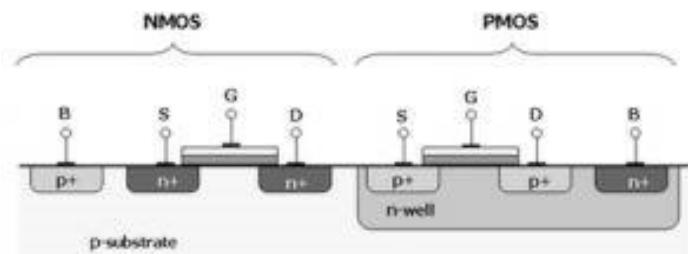


Figure 6.15 – CMOS Structure

#### **6.14.1 CMOS Working Principle**

In CMOS technology, both N-type and P-type transistors are used to design logic functions. The same signal which turns ON a transistor of one type is used to turn OFF a transistor of the other type. This characteristic allows the design of logic devices using only simple switches, without the need for a pull-up resistor. In CMOS logic gates a collection of n-type MOSFETs is arranged in a pull-down network between the output and the low voltage power supply rail (Vss or quite often ground). Instead of the load resistor of NMOS logic gates, CMOS logic gates have a collection of p-type MOSFETs in a pull-up network between the output and the higher-voltage rail (often named Vdd).

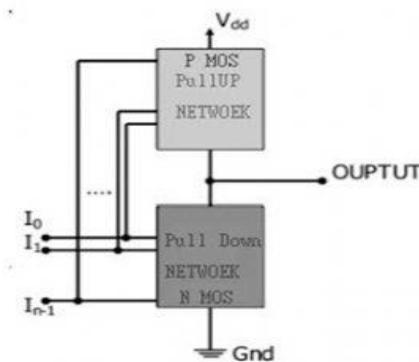

**Figure 6.16 – CMOS using Pull-Up and Pull-Down**

Thus, if both a p-type and n-type transistor have their gates connected to the same input, the p-type MOSFET will be ON when the n-type MOSFET is OFF, and vice-versa. The networks are arranged such that one is ON and the other OFF for any input pattern as shown in the Figure below.


#### **6.14.2 CMOS Inverter**

The inverter circuit as shown in the Figure below. It consists of PMOS and NMOS FET. The input A serves as the gate voltage for both transistors.

The NMOS transistor has input from  $V_{ss}$  (ground) and the PMOS transistor has input from  $V_{dd}$ . The terminal Y is output. When a high voltage ( $\sim V_{dd}$ ) is given at input terminal (A) of the inverter, the PMOS becomes an open circuit, and NMOS switched OFF so the output will be pulled down to  $V_{ss}$ .

## Chapter 6

---

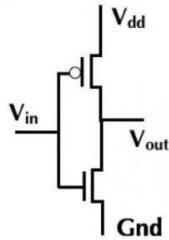

**Figure 6.17 – A CMOS Inverter**

When a low-level voltage ( $<V_{dd}$ ,  $\sim 0v$ ) applied to the inverter, the NMOS switched OFF and PMOS switched ON. So the output becomes  $V_{dd}$  or the circuit is pulled up to  $V_{dd}$ .


INPUT	LOGIC INPUT	OUTPUT	LOGIC OUTPUT
0 v	0	$V_{dd}$	1
$V_{dd}$	1	0 v	0

### 6.15 Binary Adder- Subtractor

Binary Adder-Subtractor is a special type of circuit that is used to perform both operations, i.e., Addition and Subtraction. The operation which is going to be used depends on the values contained by the control signal. In Arithmetic Logical Unit, it is one of the most important components. To work with Binary Adder-Subtractor, it is required that we have knowledge of the XOR gate, Full-Adder, Binary Addition, and subtraction.

For example, we will take two 4-bit binary numbers of 'X' and 'Y' for the operation with digits.

The Binary Adder-Subtractor is a combination of 4 Full-Adder, which is able to perform the addition and subtraction of 4-bit binary numbers. The control line determines whether the operation being performed is either subtraction or addition. This determination is done by the binary values 0 and 1, which is hold by K.

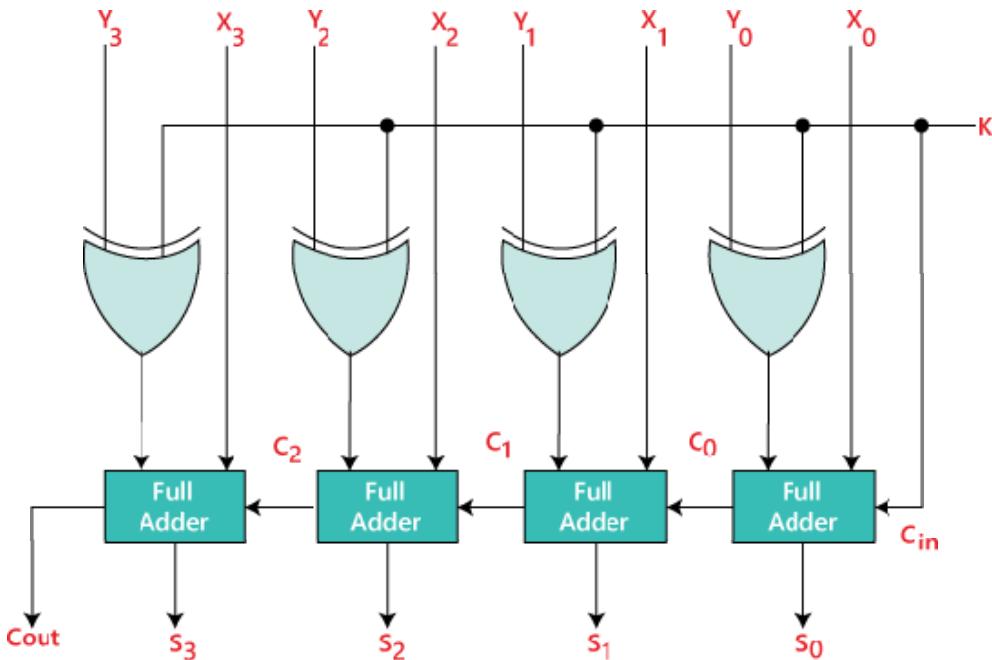

**Figure 6.18 – A Full-Adder-Subtractor**

In the above diagram, the control lines of the first Full-Adder are directly coming as its input (input carry C0). The X0 is the least significant bit of A, which is directly inputted in the Full-Adder. The result produced by performing the XOR operation of Y0 and K is the third input of the Binary Adder-Subtractor. The sum/difference (S0) and carry (C0) are the two outputs produced from the First Full-adder.

When the value of K is set to true or 1, the  $Y_0 \oplus K$  produce the complement of  $Y_0$  as the output. So, the operation would be  $X + Y_0'$ , which is the 2's complement subtraction of X and Y. It means when the value of K is 1; the subtraction operation is performed by the binary Adder-Subtractor. In the same way, when the value of K is set to 0, the  $Y_0 \oplus K$  produce  $Y_0$  as the output. So the operation would be  $X + Y_0$ , which is the binary addition of X and Y. It means when the value of K is 0; the addition operation is performed by the binary Adder-Subtractor.

The carry/borrow C0 is treated as the carry/borrow input for the second Full-Adder. The sum / difference S0 defines the least significant bit of the sum/difference of numbers X and Y.

## Chapter 6


Just like  $X_0$ , the  $X_1$ ,  $X_2$ , and  $X_3$  are faded directly to the 2<sup>nd</sup>, 3<sup>rd</sup>, and 4<sup>th</sup> Full-Adder as an input. The outputs after performing the XOR operation of  $Y_1$ ,  $Y_2$ , and  $Y_3$  inputs with  $K$  are the third inputs for 2<sup>nd</sup>, 3<sup>rd</sup>, and 4<sup>th</sup> Full-Adder. The carry  $C_1$ ,  $C_2$  are passed as the input to the Full-Adder.  $C_{out}$  is the output carry of the sum/difference. To form the final result, the  $S_1$ ,  $S_2$ ,  $S_3$  are recorded with  $s_0$ . We will use  $n$  number of Full-Adder to design the  $n$ -bit binary Adder-Subtractor.

### 6.16 Flip-Flops

There are four types of flipflop

- SR Flip-Flop
- D Flip-Flop
- JK Flip-Flop
- T Flip-Flop

We discuss only T flip flop. T flip-flop is the simplified version of JK flip-flop. It is obtained by connecting the same input 'T' to both inputs of JK flip-flop. It operates with only positive clock transitions or negative clock transitions. The circuit diagram of T flip-flop is shown in the following Figure .

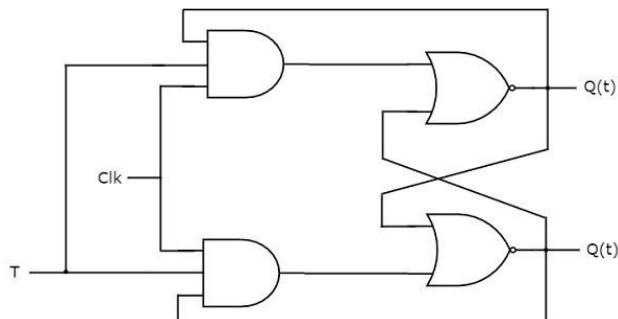

**Figure 6.19 – A T Flip-Flop**

The output of T flip-flop always toggles for every positive transition of the clock signal, when input T remains at logic High 1. Hence, T flip-flop can be used in counters.


### 6.17 Register

We know that one flip-flop can store one-bit of information. In order to store multiple bits of information, we require multiple flip-flops. The group of flip-flops, which are used to hold storestore the binary data is known as register.

If the register is capable of shifting bits either towards right hand side or towards left hand side is known as shift register. An 'N' bit shift register contains 'N' flip-flops. Following are the four types of shift registers based on applying inputs and accessing of outputs.

- Serial In – Serial Out shift register
- Serial In – Parallel Out shift register
- Parallel In – Serial Out shift register
- Parallel In – Parallel Out shift egister Serial In – Serial Out SISOSISO Shift Register

The shift register, which allows serial input and produces serial output is known as Serial In – Serial Out SISO shift register. The block diagram of 3-bit SISO shift register is shown in the following Figure .

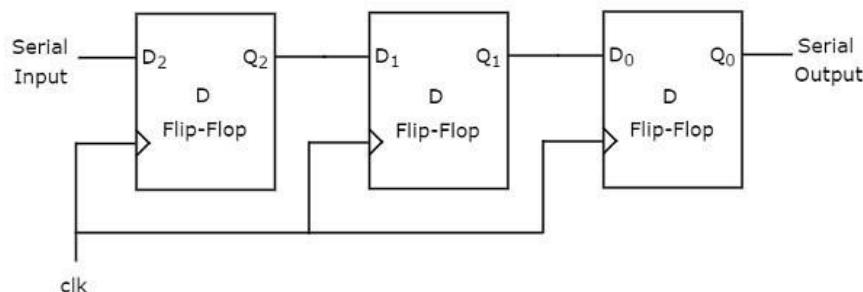

**Figure 6.20 – A SISO Register**

This block diagram consists of three D flip-flops, which are cascaded. That means, output of one D flip-flop is connected as the input of next D flip-flop. All these flip-flops are synchronous with each other since, the same clock signal is applied to each one. In this shift register, we can send the bits serially from the input of left most D flip-flop. Hence, this input is also called as serial input. For every positive edge triggering of clock signal, the data shifts from one stage to the next. So, we can receive the bits serially from the output of right most D flip-flop. Hence, this output is also called as serial output.

## **Chapter 6**

---

- A shift register is used as a Parallel to serial converter, which converts the parallel data into serial data. It is utilized at the transmitter section after Analog to Digital Converter ADC block.
- A Shift register is also used as a Serial to parallel converter, which converts the serial data into parallel data. It is utilized at the receiver section before Digital to Analog Converter DAC block.

### **6.18 Counter**

An ‘N’ bit binary counter consists of ‘N’ T flip-flops. If the counter counts from 0 to  $2^N - 1$ , then it is called as binary up counter. Similarly, if the counter counts down from  $2^N - 1$  to 0, then it is called as binary down counter.

There are two types of counters based on the flip-flops that are connected in synchronous or not.

1. Asynchronous counters
2. Synchronous counters

#### **6.18.1 Asynchronous Counters**

If the flip-flops do not receive the same clock signal, then that counter is called as Asynchronous counter. The output of system clock is applied as clock signal only to first flip-flop. The remaining flip-flops receive the clock signal from output of its previous stage flip-flop. Hence, the outputs of all flip-flops do not change affect at the same time.

There are two types:

1. Asynchronous Binary up counter
2. Asynchronous Binary down counter

#### **6.18.2 Synchronous Counters**

If all the flip-flops receive the same clock signal, then that counter is called as Synchronous counter. Hence, the outputs of all flip-flops change affect at the same time.

There are two types:


1. Synchronous Binary up counter
2. Synchronous Binary down counter

### 6.19 Encoder and Decoder

An Encoder is a combinational circuit that performs the reverse operation of Decoder. It has maximum of  $2^n$  input lines and ‘n’ output lines. It will produce a binary code equivalent to the input, which is active High. Therefore, the encoder encodes  $2^n$  input lines with ‘n’ bits. It is optional to represent the enable signal in encoders.

#### 6.19.1 Basic 4 to 2 Encoder

Let 4 to 2 Encoder has four inputs  $Y_3, Y_2, Y_1$  and  $Y_0$  and two outputs  $A_1$  and  $A_0$ . The block diagram of 4 to 2 Encoder is shown in the following Figure .

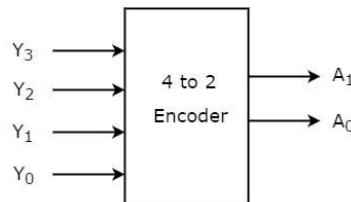

**Figure 6.21 – A Basic Encoder**

At any time, only one of these 4 inputs can be ‘1’ in order to get the respective binary code at the output. The Truth table of 4 to 2 encoder is shown below.

Inputs				Outputs	
$Y_3$	$Y_2$	$Y_1$	$Y_0$	$A_1$	$A_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

From Truth table, we can write the Boolean functions for each output as:

$$A_1 = Y_3 + Y_2 \quad A_1 = Y_3 + Y_2 \quad A_0 = Y_3 + Y_1 \quad A_0 = Y_3 + Y_1$$

Decoder is a combinational circuit that has ‘n’ input lines and maximum of  $2^n$  output lines. One of these outputs will be active High based on the combination of inputs present, when the decoder is enabled. That means decoder detects a particular code.


## Chapter 6

---

The outputs of the decoder are nothing but the min terms of 'n' input variables lines, when it is enabled.

### 6.19.2 2 to 4 Decoder

Let 2 to 4 Decoder has two inputs A1 and A0 and four outputs Y3, Y2, Y1 and Y0. The block diagram of 2 to 4 decoder is shown in the following Figure .

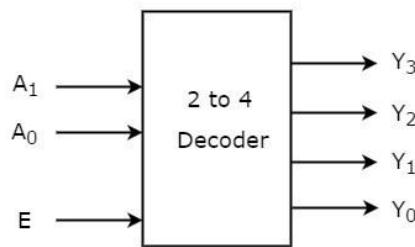

**Figure 6.22 – A 2 to 4 Decoder**

One of these four outputs will be '1' for each combination of inputs when enable, E is '1'. The Truth table of 2 to 4 decoder is shown below.

<b>Enable</b>	<b>Inputs</b>		<b>Outputs</b>			
	<b>E</b>	<b>A1</b>	<b>A0</b>	<b>Y3</b>	<b>Y2</b>	<b>Y1</b>
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

From Truth table, we can write the Boolean functions for each output as

$$Y3=E.A1.A0$$

$$Y2=E.A1.A0'$$

$$Y1=E.A1'.A0$$

$$Y0=E.A1'.A0'$$


Multiplexer is a combinational circuit that has maximum of  $2n$  data inputs, ‘n’ selection lines and single output line. One of these data inputs will be connected to the output based on the values of selection lines.

Since there are ‘n’ selection lines, there will be  $2^n$  possible combinations of zeros and ones.

So, each combination will select only one data input. Multiplexer is also called as Mux.

#### 6.20 Basic 4x1 Multiplexer

4x1 Multiplexer has four data inputs  $I_3, I_2, I_1$  and  $I_0$ , two selection lines  $s_1$  and  $s_0$  and one output  $Y$ . The block diagram of 4x1 Multiplexer is shown in the following Figure .

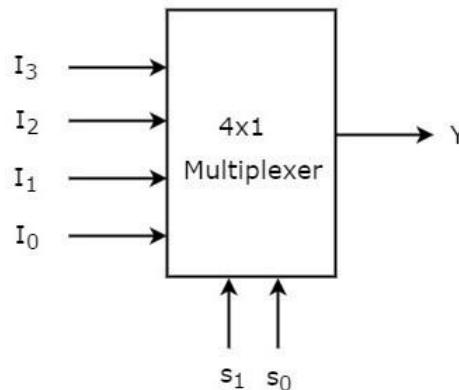

**Figure 6.23 – A 4 to 1 Multiplexer**

One of these 4 inputs will be connected to the output based on the combination of inputs present at these two selection lines. Truth table of 4x1 Multiplexer is shown below.

Selection Lines		Output
S1	S0	Y
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

## **Chapter 6**

---

From the previous truth table, we can directly write the Boolean function for output, Y as  $Y = S_1'S_0'I_0 + S_1'S_0I_1 + S_1S_0'I_2 + S_1S_0I_3$

### **6.21 Semiconductor Memory Technologies**

A semiconductor memory is used in any electronics assembly that uses computer processing technology. Semiconductor memory is the essential electronics component needed for any computer-based PCB assembly.

In addition to this, memory cards have become commonplace items for temporarily storing data - everything from the portable flash memory cards used for transferring files, to semiconductor memory cards used in cameras, mobile phones and the like.

The use of semiconductor memory has grown, and the size of these memory cards has increased as the need for larger and larger amounts of storage is needed.

To meet the growing needs for semiconductor memory, there are many types and technologies that are used. As the demand grows new memory technologies are being introduced and the existing types and technologies are being further developed.

A variety of different memory technologies are available - each one suited to different applications. Names such as ROM, RAM, EPROM, EEPROM, Flash memory, DRAM, SRAM, SDRAM, as well as F-RAM and MRAM are available, and new types are being developed to enable improved performance.

Terms like DDR3, DDR4, DDR5 and many more are seen and these refer to different types of SDRAM semiconductor memory.

In addition to this the semiconductor devices are available in many forms - ICs for printed board assembly, USB memory cards, Compact Flash cards, SD memory cards and even solid-state hard drives. Semiconductor memory is even incorporated into many microprocessor chips as on-board memory.



**Figure 6.24 – Printed circuit board containing computer memory**

#### ***Semiconductor Memory Main Types***

There are two main types or categories that can be used for semiconductor technology. These memory types or categories differentiate the memory to the way in which it operates:

##### ***6.21.1 RAM - Random Access Memory***

As the names suggest, the RAM or random-access memory is a form of semiconductor memory technology that is used for reading and writing data in any order - in other words as it is required by the processor. It is used for such applications as the computer or processor memory where variables and other stored and are required on a random basis. Data is stored and read many times to and from this type of memory. Random access memory is used in huge quantities in computer applications as current day computing and processing technology requires large amounts of memory to enable them to handle the memory hungry applications used today. Many types of RAMs including the SDRAM with its DDR3, DDR4, and soon DDR5 variants are used in huge quantities.

##### ***6.21.2 ROM - Read Only Memory***

A ROM is a form of semiconductor memory technology used where the data is written once and then not changed. In

In view of this it is used where data needs to be stored permanently, even when the power is removed - many memory technologies lose the data once the power is removed.

As a result, this type of semiconductor memory technology is widely used for storing programs and data that must survive when a computer or processor is powered down. For example, the BIOS of a computer will be stored in ROM. As the name implies, data cannot be easily written to ROM.

## **Chapter 6**

---

Depending on the technology used in the ROM, writing the data into the ROM initially may require special hardware. Although it is often possible to change the data, this gain requires special hardware to erase the data ready for new data to be written in.

As can be seen, these two types of memory are very different, and as a result they are used in very different ways.

Each of the semiconductor memory technologies outlined below falls into one of these two types. Each technology offers its own advantages and is used in a particular way, or for a particular application.

### **6.21.3 RAM - Random Access Memory**

As the names suggest, the RAM or random-access memory is a form of semiconductor memory technology that is used for reading and writing data in any order - in other words as it is required by the processor.

It is used for such applications as the computer or processor memory where variables and other stored and are required on a random basis.

Data is stored and read many times to and from this type of memory. Random access memory is used in huge quantities in computer applications as current day computing and processing technology requires large amounts of memory to enable them to handle the memory hungry applications used today. Many types of RAM including SDRAM with its DDR3, DDR4, and soon DDR5 variants are used in huge quantities.

### **6.21.4 ROM - Read Only Memory**

A ROM is a form of semiconductor memory technology used where the data is written once and then not changed. In view of this it is used where data needs to be stored permanently, even when the power is removed - many memory technologies lose the data once the power is removed.

As a result, this type of semiconductor memory technology is widely used for storing programs and data that must survive when a computer or processor is powered down. For example, the BIOS of a computer will be stored in ROM. As the name implies, data cannot be easily written to ROM. Depending on the technology used in the ROM, writing the data into the ROM initially may require special hardware. Although it is often possible to change the data, this gain requires special hardware to erase the data ready for new data to be written in.

As can be seen, these two types of memory are very different, and as a result they are used in very different ways.

Each of the semiconductor memory technologies outlined below falls into one of these two categories. each technology offers its own advantages and is used in a particular way, or for a particular application.

There is a large variety of types of ROM and RAM that are available. Often the overall name for the memory technology includes the initials RAM or ROM and this gives a guide as to the overall type of format for the memory.

With technology moving forwards apace, not only are the established technologies moving forwards with SDRAM technology moving from DDR3 to DDR4 and then to DDR5, but Flash memory used in memory cards is also developing as are the other technologies.

In addition to this, new memory technologies are arriving on the scene and they are starting to make an impact in the market, enabling processor circuits to perform more effectively.

The different memory types or memory technologies are detailed below:

### **6.21.5 DRAM**

Dynamic RAM is a form of random-access memory. DRAM uses a capacitor to store each bit of data, and the level of charge on each capacitor determines whether that bit is a logical 1 or 0. However these capacitors do not hold their charge indefinitely, and therefore the data needs to be refreshed periodically. As a result of this dynamic refreshing, it gains its name of being a dynamic RAM. DRAM is the form of semiconductor memory that is often used in equipment including personal computers and workstations where it forms the main RAM for the computer. The semiconductor devices are normally available as integrated circuits for use in PCB assembly in the form of surface mount devices or less frequently now as leaded components.

### **6.21.6 EEPROM**

This is an Electrically Erasable Programmable Read Only Memory. Data can be written to these semiconductor devices and it can be erased using an electrical voltage.

## **Chapter 6**

---

This is typically applied to an erase pin on the chip. Like other types of PROMS, EEPROM retains the contents of the memory even when the power is turned off. Also, like other types of ROM, EEPROM is not as fast as RAM.

### **6.21.7 EPROM**

This is an Erasable Programmable Read Only Memory. These semiconductor devices can be programmed and then erased at a later time. This is normally achieved by exposing the semiconductor device itself to ultraviolet light. To enable this to happen there is a circular window in the package of the EPROM to enable the light to reach the silicon of the device. When the PROM is in use, this window is normally covered by a label, especially when the data may need to be preserved for an extended period. The PROM stores its data as a charge on a capacitor.

There is a charge storage capacitor for each cell and this can be read repeatedly as required. However, it is found that after many years the charge may leak away and the data may be lost. Nevertheless, this type of semiconductor memory used to be widely used in applications where a form of ROM was required, but where the data needed to be changed periodically, as in a development environment, or where quantities were low.

### **6.21.8 Flash Memory**

Flash memory may be considered as a development of EEPROM technology. Data can be written to it and it can be erased, although only in blocks, but data can be read on an individual cell basis. To erase and re-programme areas of the chip, programming voltages at levels that are available within electronic equipment are used. It is also non-volatile, and this makes it particularly useful. As a result, Flash memory is widely used in many applications including USB memory sticks, compact Flash memory cards, SD memory cards and also now solid-state hard drives for computers and many other applications.

### **6.21.9 F-RAM**

Ferroelectric RAM is a random-access memory technology that has many similarities to the standard DRAM technology. The major difference is that it incorporates a ferroelectric layer instead of the more usual dielectric layer and this provides its non-volatile capability. As it offers a non-volatile capability, F-RAM is a direct competitor to Flash.

#### **6.21.10 M-RAM**

This is Magneto-resistive RAM, or Magnetic RAM. It is a non-volatile RAM memory technology that uses magnetic charges to store data instead of electric charges. Unlike technologies including DRAM, which require a constant flow of electricity to maintain the integrity of the data, MRAM retains data even when the power is removed. An additional advantage is that it only requires low power for active operation. As a result, this technology could become a major player in the electronics industry now that production processes have been developed to enable it to be produced.

#### **6.21.11 P-RAM / PCM**

This type of semiconductor memory is known as Phase change Random Access Memory, P-RAM or just Phase Change memory, PCM. It is based around a phenomenon where a form of chalcogenide glass changes its state or phase between an amorphous state (high resistance) and a polycrystalline state (low resistance).

It is possible to detect the state of an individual cell and hence use this for data storage. Currently this type of memory has not been widely commercialised, but it is expected to be a competitor for flash memory.

#### **6.21.12 PROM**

This stands for Programmable Read Only Memory. It is a semiconductor memory which can only have data written to it once - the data written to it is permanent.

These memories are bought in a blank format and they are programmed using a special PROM programmer. Typically, a PROM will consist of an array of fuseable links some of which are "blown" during the programming process to provide the required data pattern.

#### **6.21.13 SDRAM**

Synchronous DRAM. This form of semiconductor memory can run at faster speeds than conventional DRAM. It is synchronised to the clock of the processor and is capable of keeping two sets of memory addresses open simultaneously. By transferring data alternately from one set of addresses, and then the other, SDRAM cuts down on the delays associated with non-synchronous RAM, which must close one address bank before opening the next. Within the SDRAM family there are several types of memory technologies that are seen.

## **Chapter 6**

---

These are referred to by the letters DDR - Double Data Rate. DDR4 is currently the latest technology, but this is soon to be followed by DDR5 which will offer some significant improvements in performance.

### **6.21.14 SRAM**

Static Random-Access Memory. This form of semiconductor memory gains its name from the fact that, unlike DRAM, the data does not need to be refreshed dynamically. These semiconductor devices are able to support faster read and write times than DRAM (typically 10 ns against 60 ns for DRAM), and in addition its cycle time is much shorter because it does not need to pause between accesses. However, they consume more power, they are less dense and more expensive than DRAM. As a result of this SRAM is normally used for caches, while DRAM is used as the main semiconductor memory technology.

## **6.22 Microprocessor**

A Microprocessor is an important part of a computer architecture without which you will not be able to perform anything on your computer.

It is a programmable device that takes in input perform some arithmetic and logical operations over it and produce desired output. In simple words, a Microprocessor is a digital device on a chip which can fetch instruction from memory, decode and execute them and give results.

Microprocessor consists of an ALU, register array, and a control unit. ALU performs arithmetical and logical operations on the data received from the memory or an input device. Register array consists of registers identified by letters like B, C, D, E, H, L and accumulator. The control unit controls the flow of data and instructions within the computer.

### **6.22.1 Working Principle**

The microprocessor follows a sequence: Fetch, Decode, and then Execute. Initially, the instructions are stored in the memory in a sequential order. The microprocessor fetches those instructions from the memory, then decodes it and executes those instructions till STOP instruction is reached. Later, it sends the result in binary to the output port. Between these processes, the register stores the temporarily data and ALU performs the computing functions.

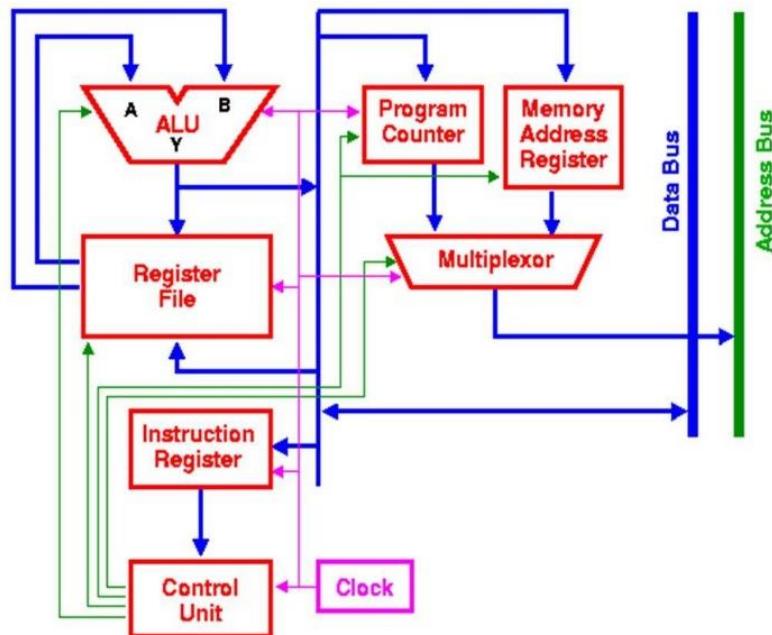


Figure 6.25 – Basic Architecture of a Microprocessor

### 6.22.2 Important Terms Used in a Microprocessor

#### 6.22.2.1 Instruction Set

It is the set of instructions that the microprocessor can understand.

#### 6.22.2.2 Bandwidth

It is the number of bits processed in a single instruction.

#### 6.22.2.3 Clock Speed

It determines the number of operations per second the processor can perform. It is expressed in megahertz (MHz) or gigahertz (GHz). It is also known as Clock Rate.

#### 6.22.2.4 Word Length

It depends upon the width of internal data bus, registers, ALU, etc. An 8-bit microprocessor can process 8-bit data at a time. The word length ranges from 4 bits to 64 bits depending upon the type of the microcomputer.

## **Chapter 6**

---

### **6.22.2.5 Data Types**

The microprocessor has multiple data type formats like binary, BCD, ASCII, signed and unsigned numbers.

### **6.22.3 Functional Parts**

#### **6.22.3.1 ALU**

Arithmetic and logic unit, As the name suggests, it performs arithmetic and logical operations like Addition, Subtraction, AND, OR, etc.

#### **6.22.3.2 Instruction Sets and Registers**

The group of instructions a processor can execute are called its "instruction set." The instruction set determines things such as the type of programs a CPU can work with. Registers are small memory locations that also contain instructions. Unlike regular memory locations, registers are referred to by a name instead of a number. For example, the IP (instruction pointer) contains the location of the next instruction, and the "accumulator" is where the processor stores the next value it plans to work on.

#### **6.22.3.3 Cache Memory**


Cache memory is an area on the CPU where copies of common instructions required to perform functions and run programs are stored temporarily. Since the processor has its own smaller, faster cache memory, it can process data more quickly than reading and writing to the main system memory. Types of microprocessor memory include ROM (read-only) and RAM (random-access).

#### **6.22.3.4 Bus**

Connection lines used to connect the internal parts of the microprocessor chip is called bus. There are three types of buses in a microprocessor. Data bus, address bus, control bus.

#### **6.22.3.5 Input Output Interface**

Input-Output Interface is used as a method which helps in transferring of information between the internal storage devices i.e., memory and the external peripheral device. A peripheral device is that which provide input and output for the computer, it is also called an I/O device e.g., a keyboard and mouse provide Input to the computer are called input devices while a monitor and printer that provide output to the computer are called output devices. Just like the external hard-drives, there is also availability of some peripheral devices which are able to provide both input and output.

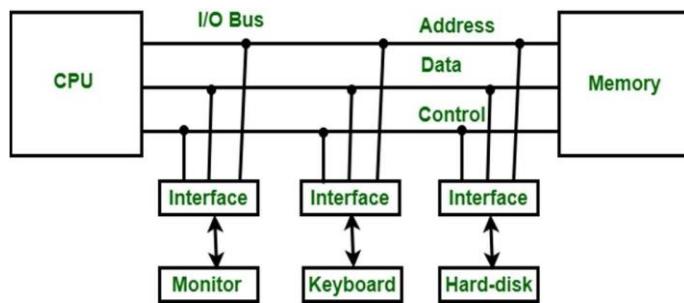

**Figure 6.26 – An Input Output Interface**

#### **6.22.3.6 Functions of Input-Output Interface:**

- It is used to synchronize the operating speed of CPU with respect to input-output devices.
- It selects the input-output device which is appropriate for the interpretation of the input-output device.
- It is capable of providing signals like control and timing signals.
- In this data buffering can be possible through data bus.
- There are various error detectors.
- It converts serial data into parallel data and vice-versa.
- It also converts digital data into analog signal and vice-versa.

### **6.23 Application in Marine Control Systems**


#### **6.23.1 Alarm Monitoring System**

Alarm monitoring follows a similar process in that the measured value is transmitted to the control unit, but in addition it is compared with the set alarm limits. This scanning process is continuous and, where an alarm condition occurs, the channel number and time will be printed out on the printer. Audible and visual Audible and visual alarms are simultaneously given in the machinery space and control room. Alarms are also given on the bridge and in the duty engineer's cabin when the machinery space is unattended. The system is also capable of monitoring itself. An alarm is given if a fault develops in the system. A fault in a particular transducer or channel circuit board does not, however, affect the rest of the system. A separate alarm channel to the bridge and cabin panels indicates the presence of faults in the power supply of the system

## Chapter 6

### 6.23.2 Condition Monitoring of The Main Engine

The conditions within a diesel engine relating to combustion pressure, indicated power, cylinder surface temperatures, condition of piston rings, etc. can be continuously monitored by the use of a microprocessor-based system. Monitoring of these parameters will result in better engine performance, reduced wear and a better overall knowledge of the general state of the engine.

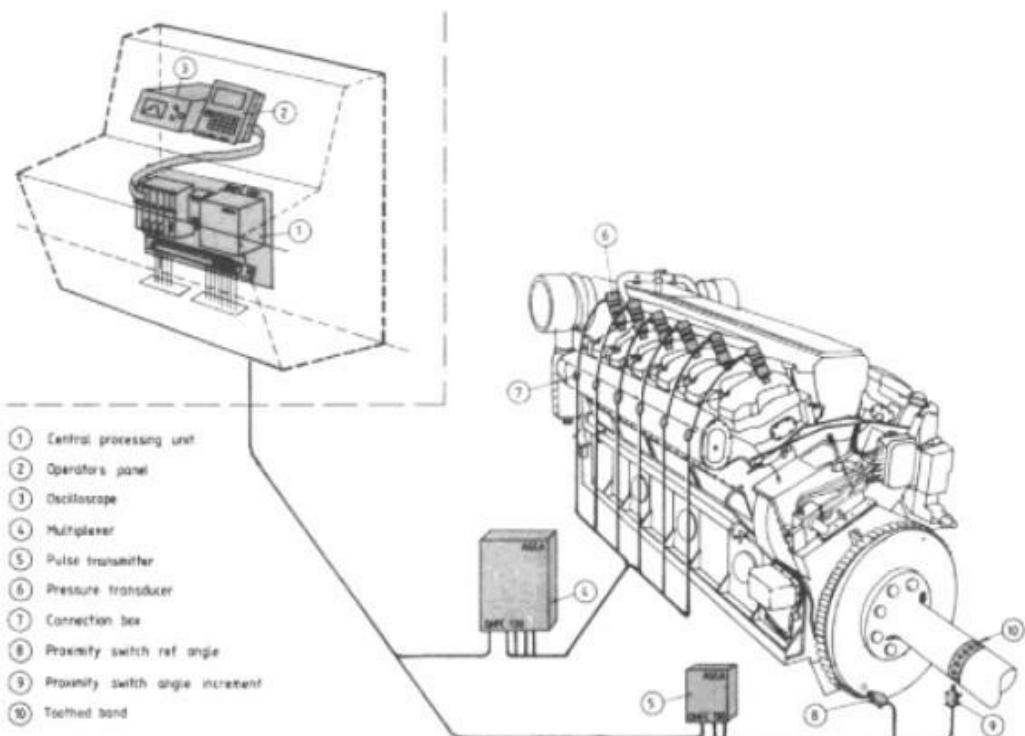

**Figure 6.27 – Microprocessor-based Control of a Main Engine**

A system used for the measurement of combustion conditions is shown in the Figure above. The combustion pressure is measured by a pressure transducer which is connected to the indicator cock of the cylinder.

The transducer produces an electric signal proportional to the pressure applied at any particular instant. This signal is supplied to a module which provides as output the instantaneous pressure, the pressure variation with time and the maximum pressure. Digital output values are provided to a panel and analogue outputs are supplied to an oscilloscope.

The crankshaft rotation angle is measured by two proximity switches. One reads the incremental angle from the flywheel teeth or a toothed band on the shaft. The other is a reference point which is the top dead centre position for the cylinder nearest to the flywheel. The pulses from the proximity switches are passed to a transmitter where they are modified and then pass to the central processing unit.

The multiplexer transmits the pressure signals, cylinder by cylinder, to the central processing unit.

The operator's panel communicates with the central processing unit to enable display, as digital values, of mean indicated combustion pressure, indicated power, engine speed, maximum combustion pressure, compression pressure and ignition angle.

Diagrams can be displayed on the oscilloscope of pressure against crank angle and peak pressure against time. The system incorporates several test and calibration functions which enable simple operation and fault tracing.

For each particular installation, parameters such as firing order, swept volume, connecting rod length and stroke length are pre-programmed into the microcomputer memory.

The program will also contain the appropriate mathematics to generate the output functions from the input data. The fitting of appropriate sensors and suitable programming of the microcomputer will enable many other engine conditions to be monitored. One example is the use of thermoelement surface temperature sensors inserted into cylinder liners. The liner surface temperature can then be continuously monitored.

#### **6.23.3 Generator Plant Control**

- Integrated control
- Integrated bridge control
- Integrated ship instrumentation system
- Cargo control system


### **6.24 The 8085 Microprocessor**

The 8085 microprocessor is pronounced as the "eighty-eighty-five" microprocessor. It is an 8-bit microprocessor designed by Intel in 1977 using NMOS technology. It is a very basic type of microprocessor that is used in washing machines, microwave ovens, mobile phones, etc.

## Chapter 6

---

The pin diagram of the 8085 microprocessor is given as follows:

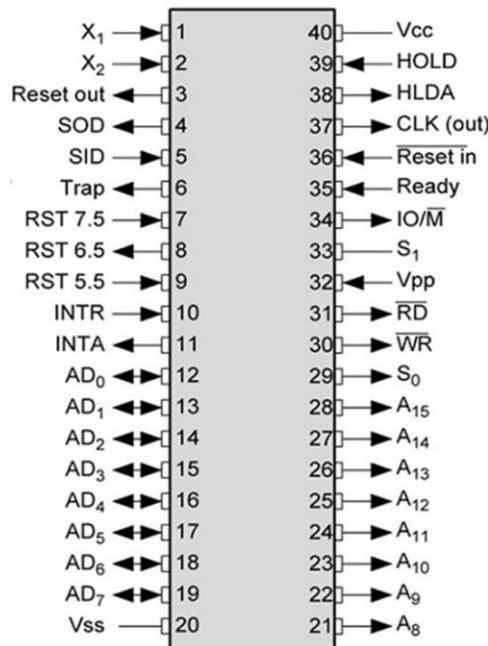

**Figure 6.28 – The 8085 Microprocessor Chip**

The pins of a 8085 microprocessor can be classified into seven groups – Address bus A15-A8, it carries the most significant 8-bits of memory/IO address.

### 6.24.1 Data Bus

AD7-AD0, it carries the least significant 8-bit address and data bus.

### 6.24.2 Control and Status Signals

These signals are used to identify the nature of operation. There are 3 control signal and 3 status signals.

Three control signals are: RD, WR and ALE.

Three status signals are IO/M, S0 and S1.

IO/M This signal is used to differentiate between IO and Memory operations, i.e., when it is high indicates IO operation and when it is low then it indicates memory operation.

#### **6.24.3 SI and S0**

These signals are used to identify the type of current operation.

#### **6.24.4 Power Supply**

There are 2 power supply signals – VCC and VSS. VCC indicates +5v power supply and VSS indicates ground signal.

#### **6.24.5 Clock Signals**

There are 3 clock signals, i.e. X1, X2, CLK OUT.

**6.24.6 X1, X2** – A crystal (RC, LC N/W) is connected at these two pins and is used to set frequency of the internal clock generator. This frequency is internally divided by 2.

**6.24.7 CLK OUT** – This signal is used as the system clock for devices connected with the microprocessor.

#### **6.24.8 Interrupts and Externally Initiated Signals**

Interrupts are the signals generated by external devices to request the microprocessor to perform a task. There are 5 interrupt signals, i.e. TRAP, RST 7.5, RST 6.5, RST 5.5, and INTR. We will discuss interrupts in detail in interrupts section.

**6.24.9 INTA** – It is an interrupt acknowledgment signal.

**6.24.10 RESET IN** – This signal is used to reset the microprocessor by setting the program counter to zero.

**6.24.11 RESET OUT** – This signal is used to reset all the connected devices when the microprocessor is reset.

**6.24.12 READY** – This signal indicates that the device is ready to send or receive data. If READY is low, then the CPU has to wait for READY to go high.

**6.24.13 HOLD** – This signal indicates that another master is requesting the use of the address and data buses.

**6.24.14 HLDA (HOLD Acknowledge)** – It indicates that the CPU has received the HOLD request and it will relinquish the bus in the next clock cycle. HLDA is set to low after the HOLD signal is removed.

## **Chapter 6**

---

### **6.24.15 Serial I/O Signals**

There are 2 serial signals, i.e. SID and SOD and these signals are used for serial communication.

**6.24.16 SOD (Serial output data line)** – The output SOD is set/reset as specified by the SIM instruction.

**6.24.17 SID (Serial input data line)** – The data on this line is loaded into accumulator whenever a RIM instruction is executed.

### **6.24.18 Input - Output Interface**

Input Output Interface provides a method for transferring information between internal storage and external I/O devices. Peripherals connected to a computer need special communication links for interfacing them with the central processing unit. The purpose of communication link is to resolve the differences that exist between the central computer and each peripheral.


The Major Differences are:

- Peripherals are electromechanical and electromagnetic devices and CPU and memory are electronic devices. Therefore, a conversion of signal values may be needed.
- The data transfer rate of peripherals is usually slower than the transfer rate of CPU and consequently, a synchronization mechanism may be needed.
- Data codes and formats in the peripherals differ from the word format in the CPU and memory. 2 UNIT-V
- The operating modes of peripherals are different from each other and must be controlled so as not to disturb the operation of other peripherals connected to the cpu.

### **6.24.19 I/O BUS and Interface Module**

- It defines the typical link between the processor and several peripherals. The I/O Bus consists of data lines, address lines and control lines.
- The I/O bus from the processor is attached to all peripherals interface.
- To communicate with a particular device, the processor places a device address on address lines.
- Each Interface decodes the address and control received from the I/O bus, interprets them for peripherals and provides signals for the peripheral controller.

- It also synchronizes the data flow and supervises the transfer between peripheral and processor.

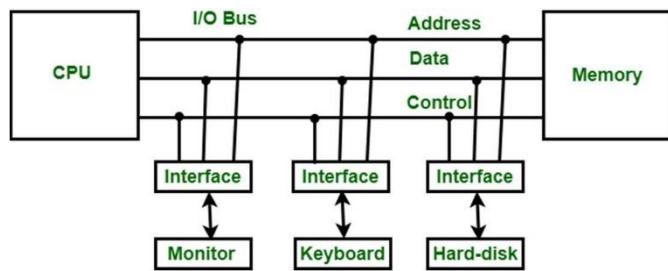

**Figure 6.29 – I/O BUS and Interface Module**

### 6.25 One-Time-Programmable Memory (OTP)

While the memory contents for a ROM are set at design/manufacturing time, Programmable Read Only memories (PROM) and more recently One-Time Programmable (OTP) devices can be programmed after manufacturing making them a lot more flexible. Once programmed, or blown, the contents cannot be changed and the contents are retained after power is removed.

The term “blown” is a historical term related to the programming mechanism of PROMs.

Contents were written by using a high voltage to burn out interconnection fuses. These PROMs were blown on special devices called PROM Programmers.

The PROM was originally developed as part of a military program related to ICBMs in 1956. The invention is attributed to Wen Tsing Chow who was working for American Bosch Arma Corporation. Commercial devices became available in the late 1960s.

The integration of PROM technology into a standard CMOS process is attributed to Kilopass Technology Inc. Kilopass has 1T, 2T and 3.5T antifuse bit cells and have been available since 2001. In 2005, Sidense developed a split channel antifuse 1T device. Synopsys has since acquired both Sidense and Kilopass.

### 6.26 NOR Flash Memory

Flash memory is NON volatile memory and currently very popular. Two the most popular types are: NOR and NAND flash memory.

## **Chapter 6**

---

NOR memory is used for storing code and execution. Allows quick random access to any location in memory array.

NAND memory is used for data storage. Requires relatively long random access.

Programming and erasing is easier than in NAND memory. Cost of bit of NAND memory is cheaper than NOR memory.

Flash memory architecture based on floating gate technology. In NOR flash memory every memory cell is connected to the floating gate. In NAND flash memory, several memory cells are connected in parallel.

NOR flash memory works on bit level. Due to the accessibility of every single bits in NOR flash memory, it is slow comparatively. It is normally used for ROM memory. It is comparatively expensive than NAND memory.

### **6.27 GPIO**

A GPIO is a signal pin on an integrated circuit or board that can be used to perform digital input or output functions. By design it has no predefined purpose and can be used by the hardware or software developer to perform the functions they choose.

Typical applications include controlling LEDs, reading switches and controlling various types of sensors.

The most common functions of GPIO pins include:

- Being configurable in software to be input or output
- Being enabled or disabled
- Setting the value of a digital output
- Reading the value of a digital output
- Generating an interrupt when the input changes value

GPIO pins are digital, meaning they only support high/low or on/off levels. They generally don't support analog input or output with many discrete voltage levels.

### **6.27.1 Objectives**

General Purpose I/O (GPIO) pins are single need to be provided to be versatile to digital and analog signals for ADC conversions. To provide efficiency the signals must be signals individually controllable on a particular chip board. Each GPIO should be able to define either an input mode or an output mode for individual pins on the chip.

Finally, the pins must be extendable for a wide array of applications and functional uses that define its generality in use.

### **6.27.2 GPIO on the LM3S89**

On the LM3S8962 the GPIO modules consist of seven separate blocks, each of these blocks will corresponding to individual ports on the GPIO interface, the ports in order are: (Port A, Port B, Port C, Port D, Port E, Port F, Port G). The GPIO module on this board supports up to 42 programmable input or output pins depending on the specific configuration being chosen.

Some of the features of the ports include: a standard logic tolerance of up to 5-V on both input and output, specific programmable control for GPIO interrupts which include interrupt generation masking, ADC sampling, programmable control for GPIO pad, digital input enables and open drain enables.

On the 8962 the data control registers allow software to conFigure the separate programmable modes on the GPIOs. This is done by configuring the data direction registers on the pins as either input or output for the lines. The data registers themselves will contain information to be driven out of the system or new data that's entered the system. An example of the seven physical blocks of the GPIO is illustrated below:

## Chapter 6

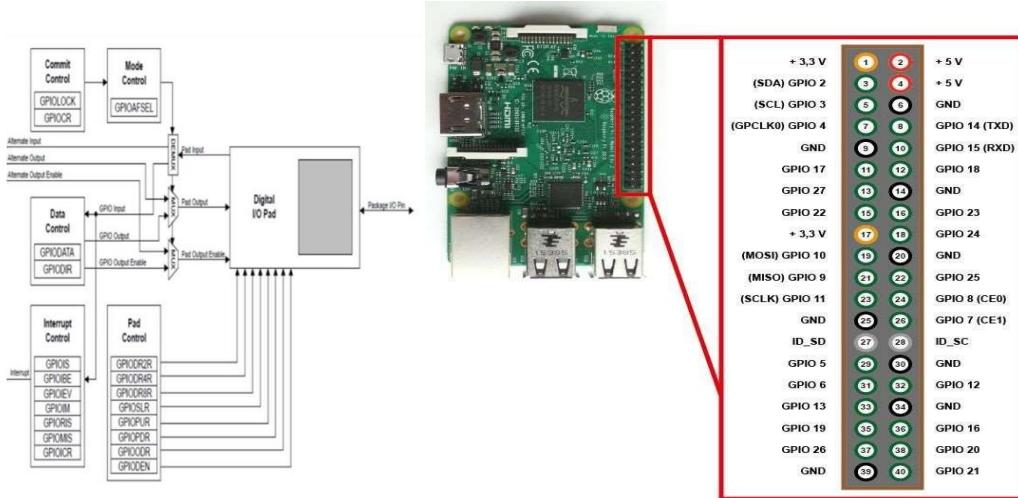


Figure 6.30 – GPIO on the LM3S8962

The reason we need pins that provide general purpose use is to provide an interface that can be controlled by various devices and similarly be used to control the behavior of other devices. As an example, a USB or Serial I/O interface can be programmed to control lines on the GPIO through register setup, these in turn can be programmed to control LEDs or switches on external devices through limited rearrangement of the pins on the board.


The ability to program directionality for individual applications and the functionality to handle interrupts and analog signals make application code developed for one purpose easily extendable to other applications through limited editing.

Time and efficiency for repetitive modes are the highest priority when using GPIOs and variability of modern processors certainly provide these required responsibilities.

### 6.28 3-bit Analogue-to-Digital Converter

The parallel ADC above converts the analogue input voltage in the range from 0 to over 3 volts to produce a 2-bit binary code. Since a 3-bit digital logic system can generate  $2^3 = 8$  different digital outputs, the analogue input voltage can therefore be compared against eight reference voltage levels with each voltage level being equal to one eighth (V/8) of the reference voltage. Thus, we could now measure a resolution of 0.5 (4/8) volts and would require  $2^3 - 1$  comparator for a 3-bit binary code output between 000 (0) and 111 (7) as shown.

**6.29 3-bit Analogue to Digital Converter Circuit (Flash Type)**

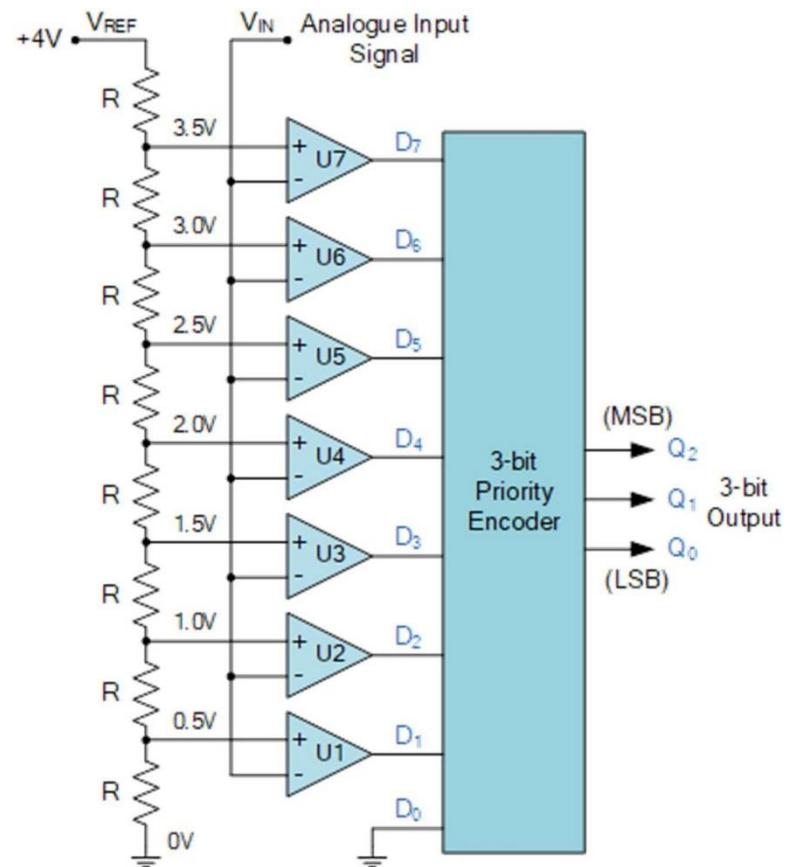

**Figure 6.31 – A Flash-type ADC**

## Chapter 6

### 6.30 ADC0808 (A to D converter IC)

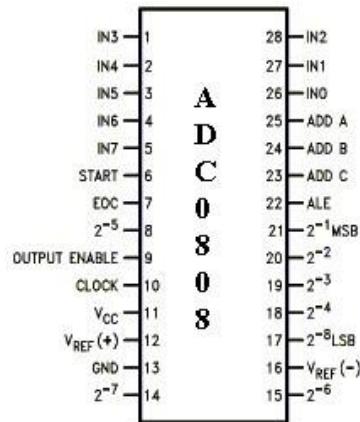


Figure 6.32 – ADC0808


ADC0808 is a converter that has 8 analog inputs and 8 digital outputs. ADC0808 allows us to monitor up to 8 different transducers using only a single chip. This eliminates the need for external zero and full-scale adjustments.

#### ADC0808 IC

ADC0808 is a monolithic CMOS device, offers high speed, high accuracy, minimal temperature dependence, excellent long-term accuracy and repeatability and consumes minimal power. These features make this device ideally suited to applications from process and machine control to consumer and automotive applications. The pin diagram of ADC0808 is shown in the Figure
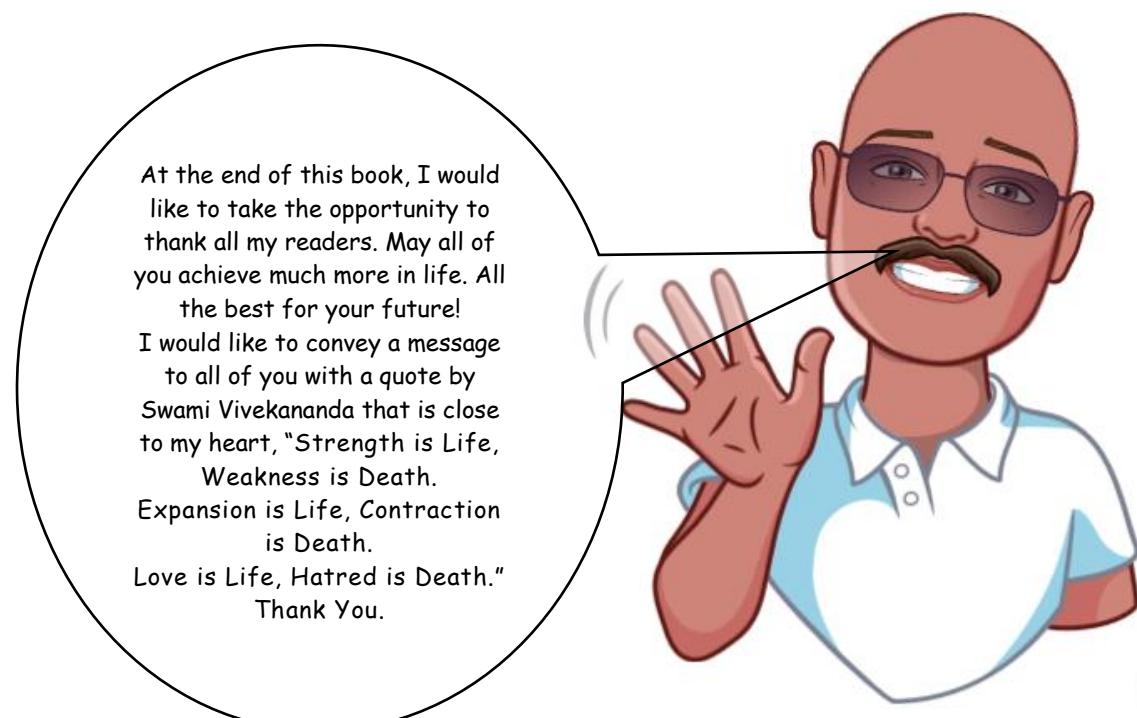
#### 6.30.1 Features

- The main features of ADC0808 include the following.
  - Easy interface to all microprocessors
  - No zero or full-scale adjust required
  - 8-channel multiplexer with address logic
  - 0V to 5V input range with single 5V power supply
  - Outputs meet TTL voltage level specifications
  - Carrier chip package with 28-pin


















## ***Chapter 6***

---



### **Sources**

- [www.elprocus.com/](http://www.elprocus.com/)
- [www.electronics-tutorials.ws](http://www.electronics-tutorials.ws)
- <https://www.electronics-notes.com/>
- [www.techwalla.com](http://www.techwalla.com)
- [www.t](http://www.t) <https://www.geeksforgeeks.org>
- <https://www.tutorialspoint.com>
- <http://www.pvpsiddhartha.ac.in/>
- Marine Control Practice by DA Taylor
- [www.marineeto.we.bs](http://www.marineeto.we.bs)
- [www.fierceelectronics.com](http://www.fierceelectronics.com)
- <https://www.electronics-tutorials.ws>
- <https://www.omega.com/>
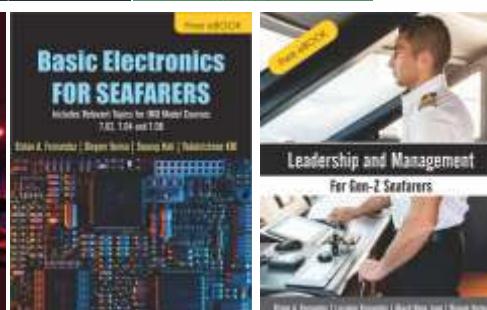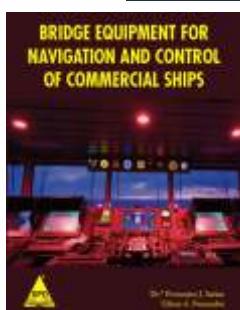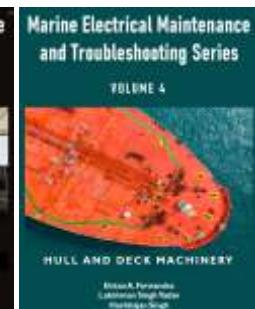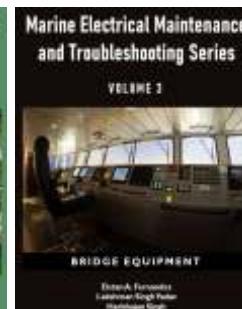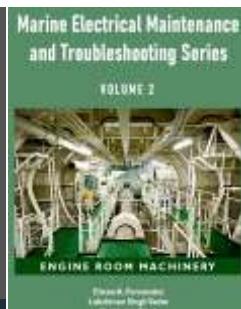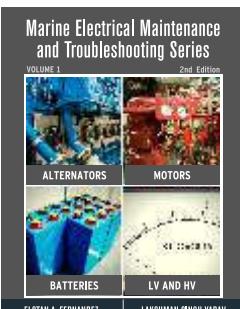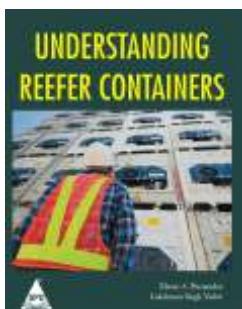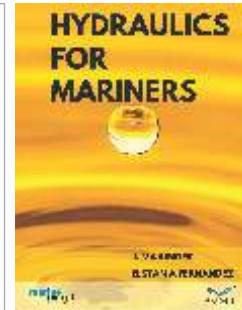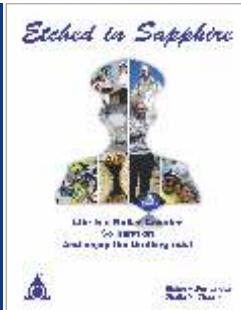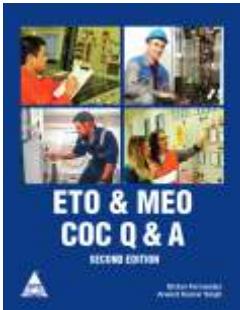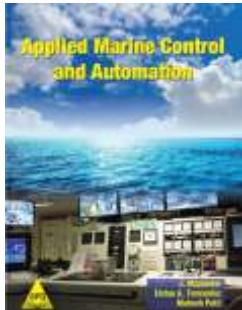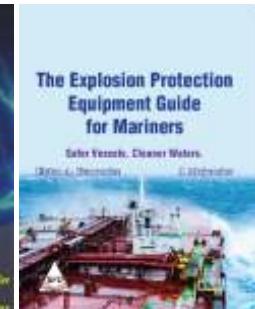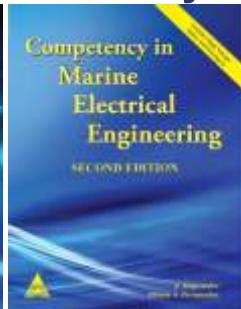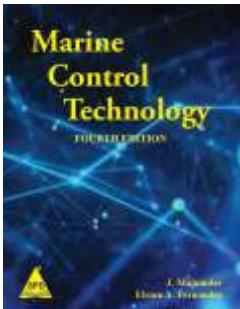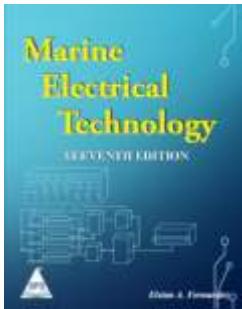
# Maritime Books Published by Our Team of Authors



## Forthcoming Books

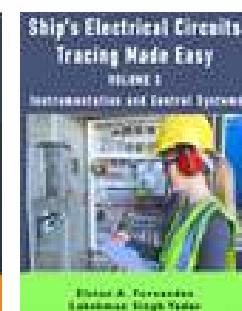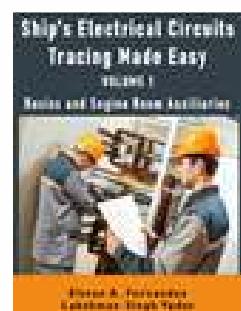

## Forthcoming Books



# ABOUT THE BOOK

This book is compiled to help both pre-sea cadets and officers of post sea courses get a clear understanding of Basic Electronics, which is so important in the shipping industry these days. Efforts have been made to align the topics to the requirements of the IMO Model Courses for Marine Engineers at the Management and Operation Level and also for Electro Technical Officers.

The chapters within are :

**Chapter No.      Title**

1	Electron Theory
2	Semiconductors
3	Silicon Controlled Rectifiers
4	Power Electronics
5	ICs and LSI
6	Digital Techniques

Brought to you by:



Free eBooks Available with:



[www.marineinsight.com](http://www.marineinsight.com)



[marineelectricity.com](http://marineelectricity.com)

Printed By: SSIA Graphics, Pune.